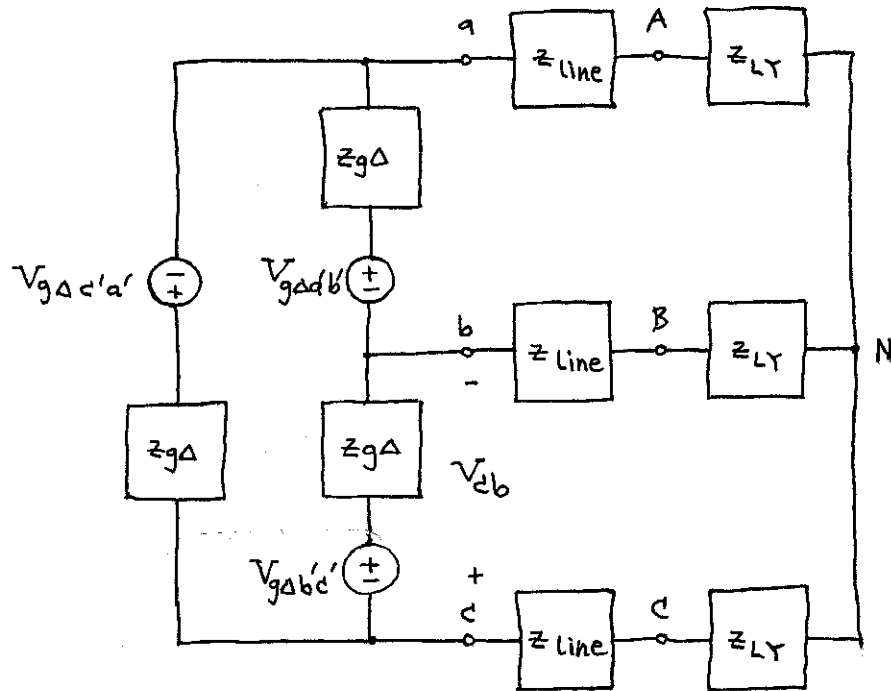


2.1



$$V_{g\Delta a'b'} = 116 \angle 0^\circ \text{ V} \quad z_{g\Delta} = 4.5 + j6 \ \Omega$$

$$V_{g\Delta b'c'} = 116 \angle -120^\circ \text{ V} \quad z_{line} = 1.2 + j7.7 \ \Omega$$

$$V_{g\Delta c'a'} = 116 \angle +120^\circ \text{ V} \quad z_{LY} = 4 - j3 \ \Omega$$

- Draw a single-phase equivalent circuit
- Find  $V_{cb}$

sol'n: a) We convert the circuit to a Y-Y config.

For the generator, we have a  $\Delta$  that we convert to a Y configuration.


For  $\Delta$ -to- $Y$  transformation, we have

$$z_{gY} = \frac{z_{g\Delta}}{3} = \frac{4.5 + j6 \Omega}{3}$$


or  $z_{gY} = 1.5 + j2 \Omega$

For the voltage sources, we assume  $\epsilon_{gY} = 0 = z_{g\Delta}$  and find equivalent voltages for  $\Delta$  and  $Y$ .

$\Delta$  config:

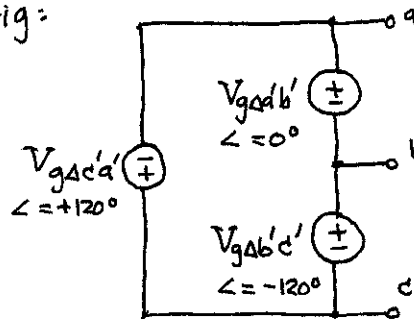

$Y$  config:

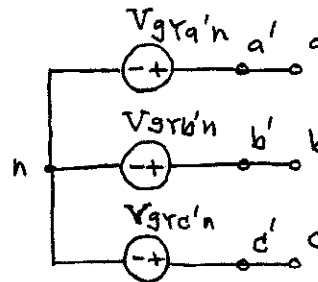

For  $V_{ab}$  to be the same for both diagrams, we have


$$V_{g\Delta a'b'} = V_{gYa'n} - V_{gYb'n}$$

where  $V_{gYb'n} = V_{gYa'n} \angle -120^\circ$

Thus,

$$V_{g\Delta a'b'} = V_{g r a'n} (1 - \angle -120^\circ)$$

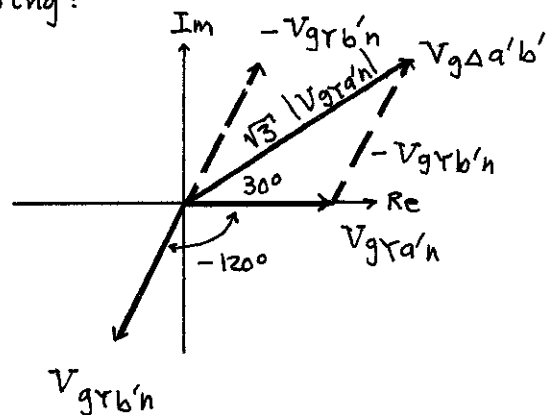Using a phasor diagram, we have the following:



Note: We treat  $V_{g r a'n}$  as though it has  $\angle = 0^\circ$ . This works because we are only looking for the relative value of  $V_{g \Delta a'b'}$  given  $V_{g r a'n}$ . In other words, the eq'n we derive from the diagram is valid.


$$V_{g \Delta a'b'} = V_{g r a'n} \cdot \sqrt{3} \angle 30^\circ$$

$$\text{or } V_{g r a'n} = V_{g \Delta a'b'} \cdot \frac{1}{\sqrt{3}} \angle -30^\circ$$

$$\text{or } V_{g r a'n} = 116 \angle 0^\circ \cdot \frac{1}{\sqrt{3}} \angle -30^\circ \text{ V}$$

$$V_{g r a'n} = 67 \angle -30^\circ \text{ V}$$

Single-phase equivalent:

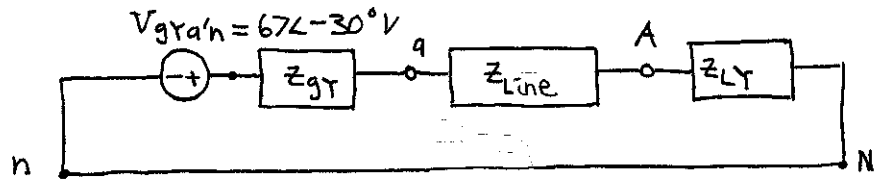

$$z_{gY} = 1.5 + j2 \Omega$$

$$z_{Line} = 1.2 + j7.7 \Omega$$

$$z_{LY} = 4 - j3 \Omega$$

b) To find  $V_{cb}$ , we determine  $V_{an}$  and

use a phasor diagram to relate  $V_{an}$  to  $V_{ab}$ . (But this is the same as the phasor diagram used in part (a).)

$$V_{ab} = V_{an} \cdot \sqrt{3} \angle 30^\circ$$

Given  $V_{ab}$ , we have  $V_{bc} = V_{ab} \cdot 1 \angle -120^\circ$

$$\text{and } V_{cb} = -V_{bc} = V_{bc} \cdot 1 \angle \pm 180^\circ$$

Combining eq's, we have the following result:

$$V_{cb} = V_{an} \cdot \sqrt{3} \angle 30^\circ \cdot 1 \angle -120^\circ \cdot 1 \angle 180^\circ$$

$$V_{cb} = V_{an} \sqrt{3} \angle 90^\circ$$

What remains is to find  $V_{an}$  from the single-phase equivalent. We have a V-divider:

$$V_{an} = V_{aN} = V_{gr'a'n} \cdot \frac{z_{Line} + z_{LY}}{z_{gY} + z_{Line} + z_{LY}}$$

$$\text{or } V_{an} = 67 \angle -30^\circ \text{ V} \cdot \frac{1.2 + j7.7 + 4 - j3 \Omega}{1.5 + j2 \Omega + 1.2 + j7.7 + 4 - j3 \Omega}$$

$$= 67 \angle -30^\circ \text{ V} \frac{5.2 + j4.7}{6.7 + j6.7}$$

$$= 67 \angle -30^\circ \text{ V} \frac{5.2 + j4.7}{6.7(1+j)}$$

$$= 67 \angle -30^\circ \text{ V} \cdot \frac{7 \angle 42^\circ}{6.7(\sqrt{2}) \angle 45^\circ}$$

$$= \frac{70}{\sqrt{2}} \angle -33^\circ \text{ V}$$

Substituting into  $V_{cb} = V_{an} \sqrt{3} \angle 90^\circ$  yields

$$V_{cb} = \frac{70}{\sqrt{2}} \angle -33^\circ \text{ V} \cdot \sqrt{3} \angle 90^\circ$$

$$V_{cb} = 85.7 \angle 57^\circ \text{ V} \text{ or } 70 \sqrt{\frac{3}{2}} \angle 57^\circ \text{ V}$$

$$\text{or } V_{cb} = 51.4 + j68.6 \text{ V}$$