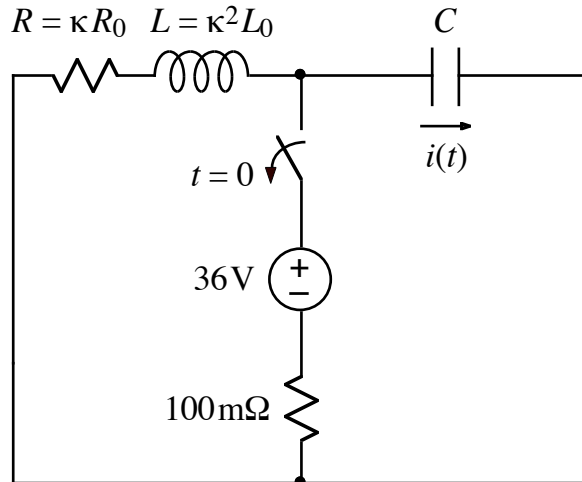


1.



After being closed for a long time, the switch opens at  $t = 0$ .

The inductance and resistance in the above circuit form the model of a coil that is made by winding a piece of wire around a plastic rod. The coil has  $\kappa$  turns of wire. One turn of wire would give rise to the following resistance and inductance:

$$R_0 = 30 \text{ m}\Omega \quad L_0 = 100 \text{ nH}$$

Since resistance is proportional to wire length, the resistance of the coil is proportional to the number of turns:

$$R = \kappa R_0.$$



The inductance of the coil, however, is proportional to the number of turns *squared*:

$$L = \kappa^2 L_0.$$

Find the number of turns,  $\kappa$ , and the value of  $C$  that make the circuit critically damped with a characteristic root  $s = -5\text{k rad/s}$ .

2. Using the component values from problem 1, find a numerical expression for  $i(t)$  for  $t > 0$ .

3.

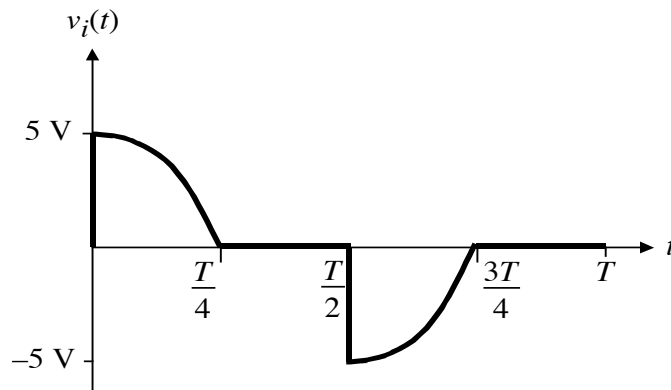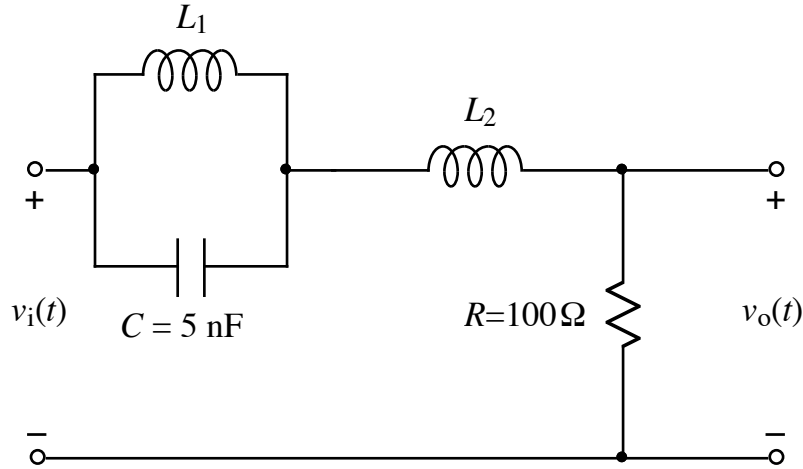

$T = \text{one period of } v_i(t) = 0.8 \cdot \pi \text{ } \mu\text{s}$

$$v_i(t) = \begin{cases} 5 \cos(\omega_0 t) \text{ V} & 0 < t \leq T/4 \\ 0 \text{ V} & T/4 < t \leq T/2 \\ 5 \cos(\omega_0 t) \text{ V} & T/2 < t \leq 3T/4 \\ 0 \text{ V} & 3T/4 < t \leq T \end{cases}$$

Find values of  $L_1 \neq 0$  and  $L_2 \neq 0$  for the above filter circuit such that the transfer function equals zero for the fourth harmonic and one for the eighth harmonic of  $v_i(t)$ , also shown above.

4. Find numerical values of coefficients  $a_v$ ,  $a_1$ ,  $a_2$ ,  $b_1$ , and  $b_2$  for the Fourier series for  $v_i(t)$  from problem 3:

$$v_i(t) = a_v + \sum_{k=1}^{\infty} a_k \cos(k\omega_0 t) + b_k \sin(k\omega_0 t)$$