

1.  $i_L(0^-) = i_g$  and  $v_L(0^+) = 0$  V
2.  $0 < L < 100$  mH
3. a)  $\frac{dv_1}{dt} = \frac{i_C}{C} = \frac{i_1 + i_2 + (v_o - v_1)/R_1}{C}$   
b)  $v_1(0^-) = v_g = -v_o$
4. a) critically damped  
b)  $i(t) = A_1 e^{-\alpha t} + A_2 t e^{-\alpha t} + A_3$  where  $\alpha = \frac{100 \text{ kr/s}}{6}$   
 $\left. \frac{di(t)}{dt} \right|_{t=0^+} = \frac{v_L(0^+)}{L} = \frac{6 \text{ V}}{3 \mu\text{H}} = 2 \text{ MA/s} = -\alpha A_1 + A_2$