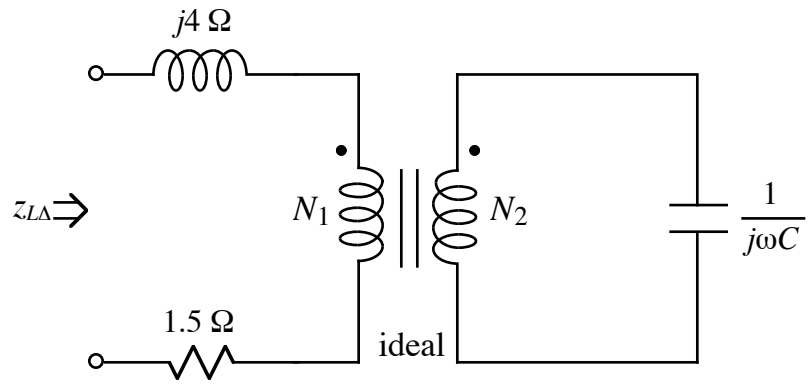


Ex:



Given $\omega = 300 \text{ rad/s}$ and $N_1/N_2 = 10$, find the value of C that makes $z_{L\Delta} = 1.5 \Omega$.
Note that $z_{L\Delta}$ is the equivalent impedance of the entire circuit.


sol'n:

For an ideal transformer, the reflected impedance is

$$z_r = \left(\frac{N_1}{N_2} \right)^2 z_{L\Delta} = 10^2 \cdot z_L$$

$$\text{where } z_{L\Delta} \equiv \text{load on secondary} = \frac{1}{j\omega C}$$

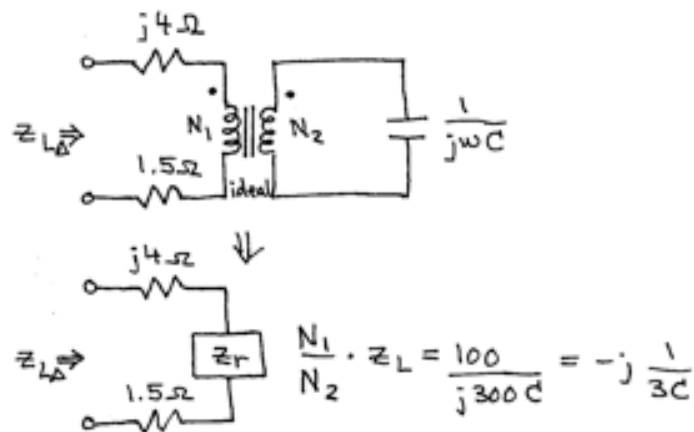We replace the entire transformer and load impedance with the reflected impedance, z_r :



$$\text{Now we have } z_{L\Delta} = j4\Omega - j \frac{1}{3C} + 1.5\Omega.$$

$$\text{We want } z_{L\Delta} = 1.5\Omega.$$

$$\text{Thus, } j4\Omega - j \frac{1}{3C} = 0\Omega.$$

$$\text{or } j \frac{1}{3C} = j4\Omega$$

$$\text{or } 3C = \frac{1}{4}$$

$$\text{or } C = \frac{1}{12} \text{ F} = 83.3 \text{ mF}.$$