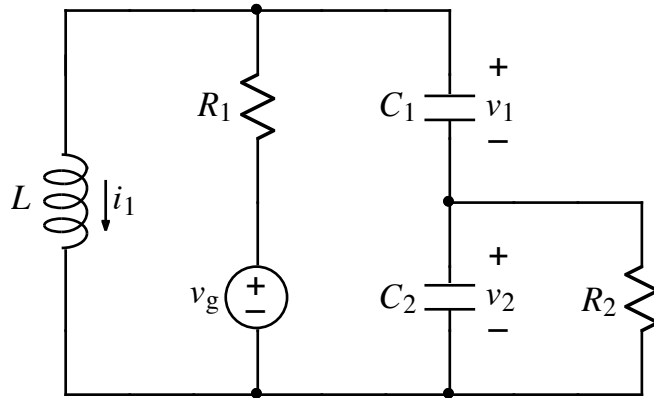


Ex:



At $t = 0$, $v_g(t)$ switches instantly from $-v_0$ to v_0 .

- a) Write the state-variable equations for the circuit in terms of the state vector:

$$\bar{x} = \begin{bmatrix} i_1 \\ v_1 \\ v_2 \end{bmatrix}$$

- b) Evaluate the state vector at $t = 0^+$.

SOL'N:

- a) We have first derivatives of state vars on the left, and we first equate these to non-derivatives:


$$\frac{di_1}{dt} = \frac{di_L}{dt} = \frac{v_L}{L}$$

$$\frac{dv_1}{dt} = \frac{dv_{C1}}{dt} = \frac{i_{C1}}{C_1}$$

$$\frac{dv_2}{dt} = \frac{dv_{C2}}{dt} = \frac{i_{C2}}{C_2}$$

We now write the variables on the right in terms of only state vars i_1 , v_2 , and v_3 , (and components and sources).

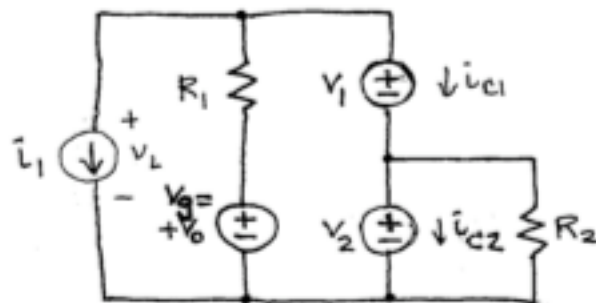
This problem of writing i 's and v 's in terms of state var's is easier to solve if we redraw the circuit with i_c 's and v_c 's shown as sources:



Note: we use $v_g = +V_0$ for $t > 0$.

Using superposition, we turn on one source at a time.

I. i_1 on

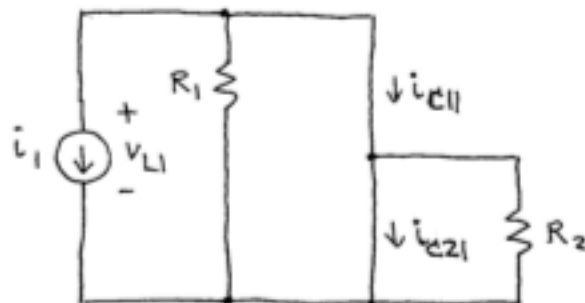


$$v_{L1} = 0V \quad (c_1, c_2 \text{ form wire, short})$$

$$i_{c1} = -i_1 \quad (\text{all of } i_1 \text{ flows in short})$$

$$i_{c2} = -i_1 \quad (\text{all of } i_1 \text{ flows in short})$$

II. $v_g = v_o$ on

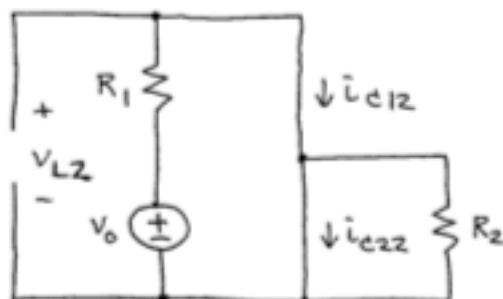


$$v_{L2} = 0V \quad (\text{shorted by } C_1, C_2)$$

$$i_{c12} = \frac{v_o}{R_1} \quad (\text{middle loop carries all of the current})$$

$$i_{c22} = \frac{v_o}{R_1} \quad (\text{ditto, } R_2 \text{ shorted})$$

III. v_i on

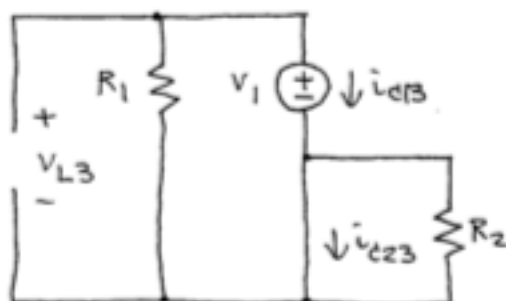


$$v_{L3} = v_i \quad (L \text{ is connected across } v_i)$$

$$i_{c13} = -\frac{v_i}{R_1} \quad (\text{all current is in middle loop})$$

$$i_{c23} = i_{c13} = -\frac{v_i}{R_1}$$

IV. V_2 on

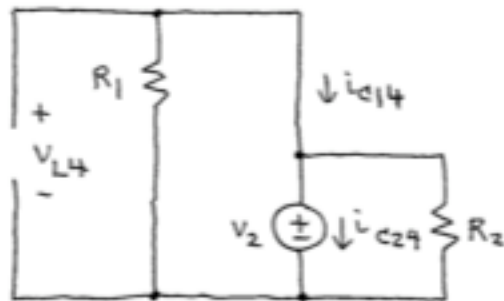

$$V_{L4} = V_2 \quad (\text{L is across } V_2)$$

$$i_{L4} = -\frac{V_2}{R_1} \quad (\text{i flows around middle loop})$$

$$i_{C24} = -\frac{V_2}{R_1 \parallel R_2} = -\frac{V_2}{R_1} - \frac{V_2}{R_2} \quad (\text{i in } R_1 \text{ \& } R_2 \text{ from Ohm's law})$$

Combining results:


$$\frac{di_L}{dt} = \frac{V_1 + V_2}{L}$$

$$\frac{dv_1}{dt} = \frac{-i_1 - \frac{V_1}{R_1} - \frac{V_2}{R_1} + \frac{V_0}{R_1}}{C_1}$$

$$\frac{dv_2}{dt} = \frac{-i_1 - \frac{V_1}{R_1} - \frac{V_2}{R_1} - \frac{V_2}{R_2} + \frac{V_0}{R_1}}{C_2}$$

b)

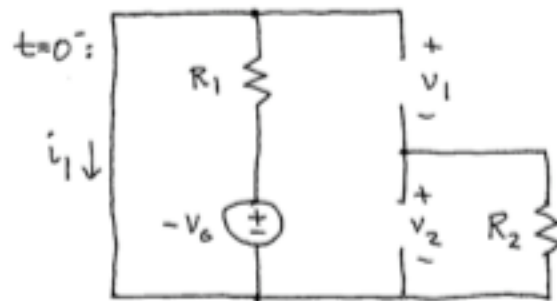For initial conditions, we use the circuit at $t=0^-$, since $i_L(0^+) = i_L(0^-)$ and $v_C(0^+) = v_C(0^-)$. At $t=0^-$, $L = \text{wire}$, $C = \text{open}$, and $V_g = -V_0$.



From loop on left, $i_1(0^-) = -\frac{V_0}{R_1}$.

Note: no current flows on right side.

No current R_2 , so $v_2(0^-) = 0V$ is v -drop across R_2 .

Short on left side and no v -drop for R_2 give $v_1 = 0V$ from outer v -loop.

$$i_1(0^+) = -\frac{V_0}{R_1} \quad (\text{same values as at } t=0^-)$$

$$v_1(0^+) = 0V$$

$$v_2(0^+) = 0V$$