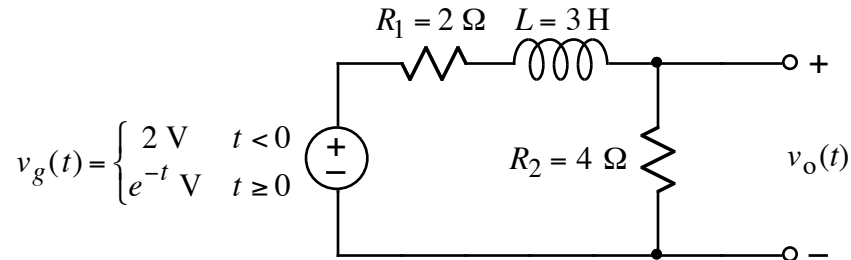


Ex:




- Write the Laplace transform $V_g(s)$ of $v_g(t)$.
- Write the Laplace transform $V_o(s)$ of $v_o(t)$. Be sure to include the effects of initial conditions, if they are nonzero.
- Write a numerical time-domain expression for $v_o(t)$ where $t \geq 0$.

SOL'N: a) The Laplace transform depends only on what the input signal is from time 0 to ∞ .

$$\mathcal{L}\{v_g(t)\} = \mathcal{L}\{e^{-t}\}V = \frac{1}{s+1}V$$

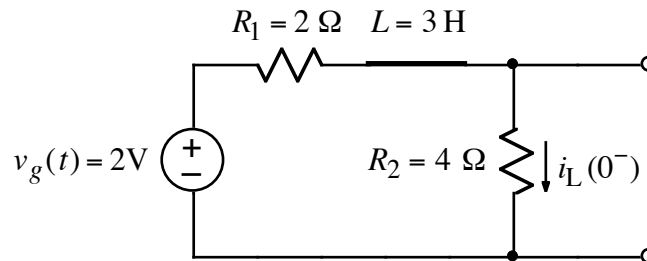
- We find initial conditions by considering circuit at $t = 0^-$. The circuit has a 2 V input and has reached equilibrium. Thus, the L acts like a wire.



We use Ohm's Law to obtain the initial inductor current:

$$i_L(0^-) = \frac{2\text{ V}}{2\ \Omega + 4\ \Omega} = \frac{1}{3}\text{ A}$$

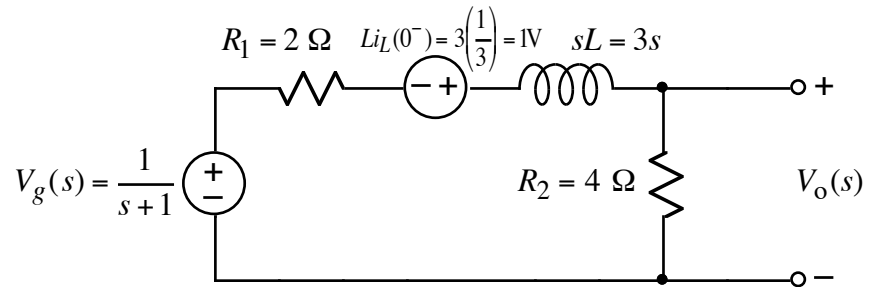Our circuit model includes initial conditions for the L :



The output voltage is found by summing the input voltages and using a voltage divider formula:

$$\begin{aligned}
 V_o(s) &= \left[\frac{1}{s+1} + Li_L(0^-) \right] \frac{R_2}{R_1 + sL + R_2} = \left[\frac{1}{s+1} + 3\left(\frac{1}{3}\right) \right] \frac{4}{2 + 3s + 4} \\
 &= \left[\frac{1}{s+1} + 1 \right] \frac{4}{3(s+2)} = \frac{4}{3} \frac{s+2}{(s+1)(s+2)} \\
 &= \frac{4}{3} \frac{1}{s+1} \text{ V}
 \end{aligned}$$

c) The output voltage versus time is the inverse Laplace transform of $V_o(s)$:

$$v_o(t \geq 0) = \frac{4}{3} e^{-t} u(t) \text{ V}$$

NOTE: We could omit the $u(t)$, but it reminds us that our answer only applies to $t \geq 0$.