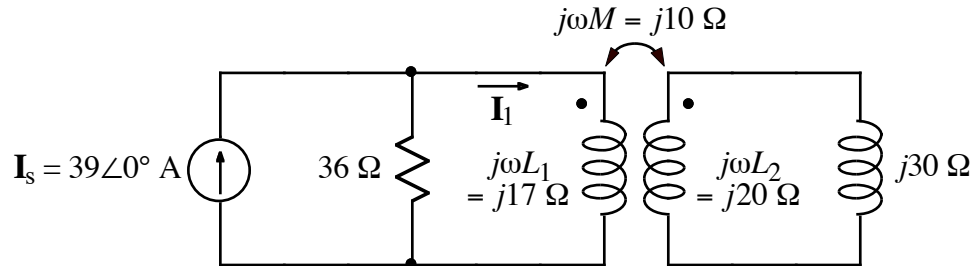


Ex:




Calculate the numerical value of phasor current I_1 for the above circuit. Note: the transformer is linear.

SOL'N:

$$\text{Use } z_r = \frac{(\omega M)^2}{z_{\text{secondary}}} = \frac{10^2 \Omega^2}{j20 + j30 \Omega}$$

$$z_r = \frac{100 \Omega^2}{j50 \Omega} = -j2 \Omega$$

Equiv circuit:

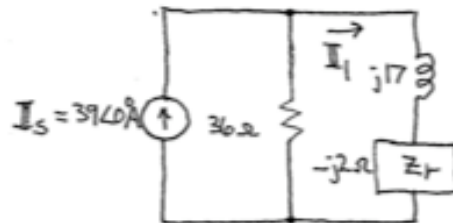

This is a current divider.

$$\begin{aligned} I_1 &= I_s \frac{36 \Omega}{36 \Omega + j17 \Omega - j2 \Omega} \\ &= I_s \frac{36 \Omega}{36 \Omega + j15 \Omega} = I_s \frac{12 \Omega}{12 \Omega + j5 \Omega} \end{aligned}$$

$$= I_s \frac{12}{13 \angle 22.6^\circ} = \frac{39 \cdot 12}{13 \angle 22.6^\circ} \text{ A}$$

$$I_1 = 36 \angle -22.6^\circ \text{ A}$$