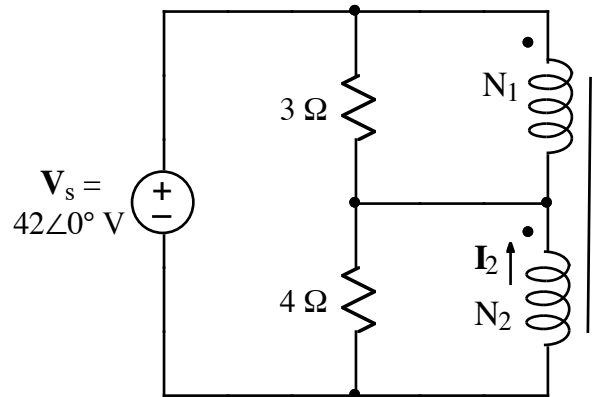


Ex:




Given $N_1/N_2 = 1/6$, calculate the phasor current, I_2 , flowing upward in the bottom coil of the transformer. Note: the transformer is ideal.

SOL'N:

Ideal transformer relationships:

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = N, \quad \frac{I_2}{I_1} = \frac{N_1}{N_2} = N$$

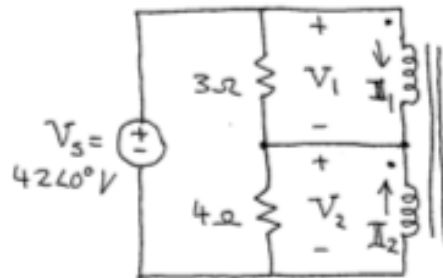We draw the circuit and label I 's and V 's.



From an outside V -loop, we have


$$V_3 = V_1 + V_2 = N V_2 + V_2 = (1+N) V_2$$

$$\text{or } 42\angle 0^\circ V = \left(1 + \frac{1}{6}\right) V_2 \quad \text{or } V_2 = 42\angle 0^\circ V \cdot \frac{6}{7}$$

$$\text{or } V_2 = 36\angle 0^\circ V$$

$$\text{Then } V_1 = N V_2 = \frac{1}{6} \cdot 36 \angle 0^\circ \text{ V} = 6 \angle 0^\circ \text{ V}$$

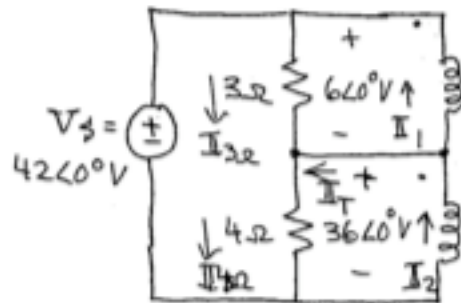Adding these voltages to our diagram allows us to calculate currents in R 's.



$$I_{3\Omega} = \frac{V_1}{3\Omega} = \frac{6 \angle 0^\circ \text{ V}}{3\Omega} = 2 \angle 0^\circ \text{ A}$$

$$I_{4\Omega} = \frac{V_2}{4\Omega} = \frac{36 \angle 0^\circ \text{ V}}{4\Omega} = 9 \angle 0^\circ \text{ A}$$

Now consider I_T flowing in the wire between the transformer coils toward the R 's.

$$I_T = I_1 + I_2 = \frac{I_2}{N} + I_2 = \left(1 + \frac{1}{N}\right) I_2 = 7I_2$$

$$\text{and } I_T + I_{3\Omega} = I_{4\Omega} \text{ or } I_T = 9\text{A} - 2\text{A} = 7\text{A } \angle 0^\circ$$

$$\therefore 7I_2 = 7\text{A } \angle 0^\circ$$

$$\text{or } I_2 = 1\text{A } \angle 0^\circ$$