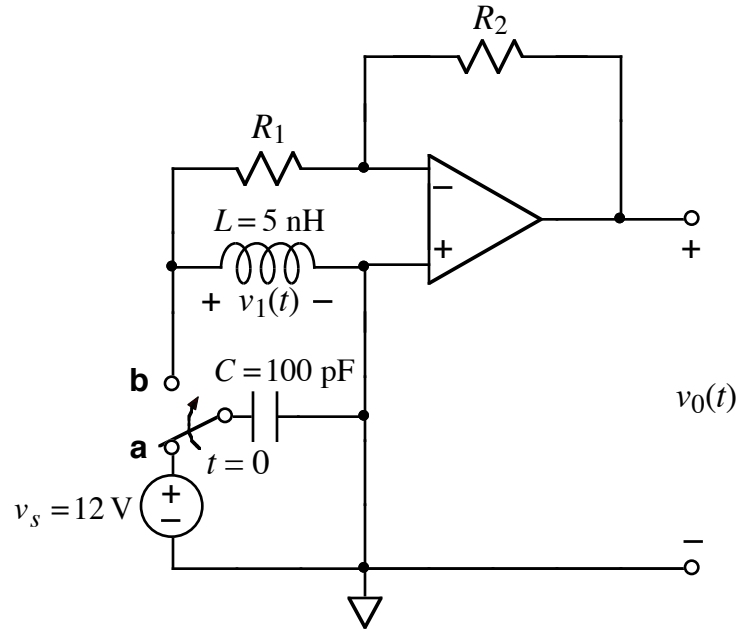




1.



After being in position **a** for a long time, the switch moves to position **b** at time $t = 0$.

Find a symbolic expression for the Laplace-transformed output, $\mathbf{V}_o(s)$, in terms of not more than R_1 , R_2 , L , C , and values of sources or constants.

2.

Choose a numerical value for R_1 to make


$$v_1(t) = v_m e^{-\alpha t} [\cos(\beta t) - \sin(\beta t)]$$

where v_m , α , and β are real-valued constants.

Hint: R_1 behaves as though it is in parallel with L and C .


Hint: $s = s + \alpha - \alpha$.

3.

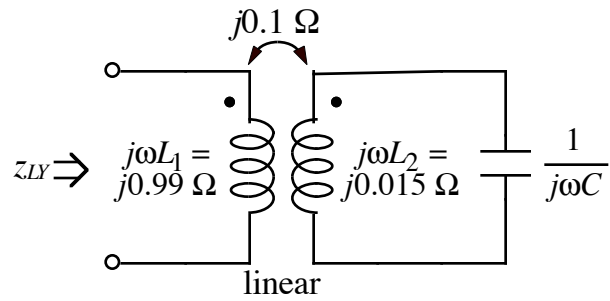

Given $\omega = 1\text{Mrad/s}$, find the value of C that makes $z_{LY} = -j1.01\ \Omega$. Note that z_{LY} is the equivalent impedance of the entire circuit.

4.

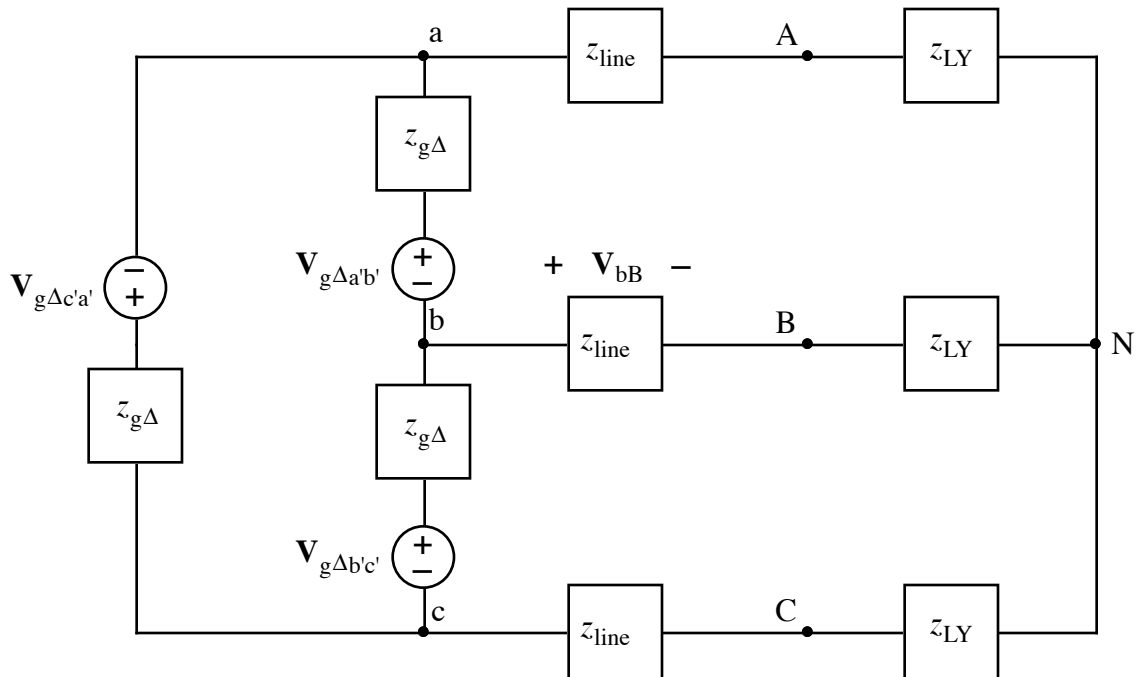

$$V_{g\Delta a'b'} = 168\angle 0^\circ\ \text{V}$$

$$z_{g\Delta} = j0.9\ \Omega$$

$$V_{g\Delta b'c'} = 168\angle -120^\circ\ \text{V}$$

$$z_{\text{line}} = j1.68\ \Omega$$

$$V_{g\Delta c'a'} = 168\angle +120^\circ\ \text{V}$$

$$z_{LY} = -j1.01\ \Omega$$

For the above 3-phase balanced circuit, find the single-phase equivalent model.

5.

For the above 3-phase balanced circuit, find the numerical value of the phasor voltage V_{bB} .