
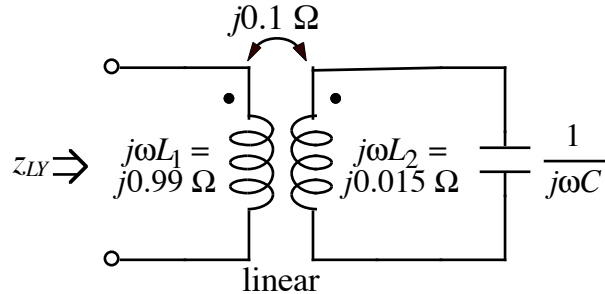


Ex:

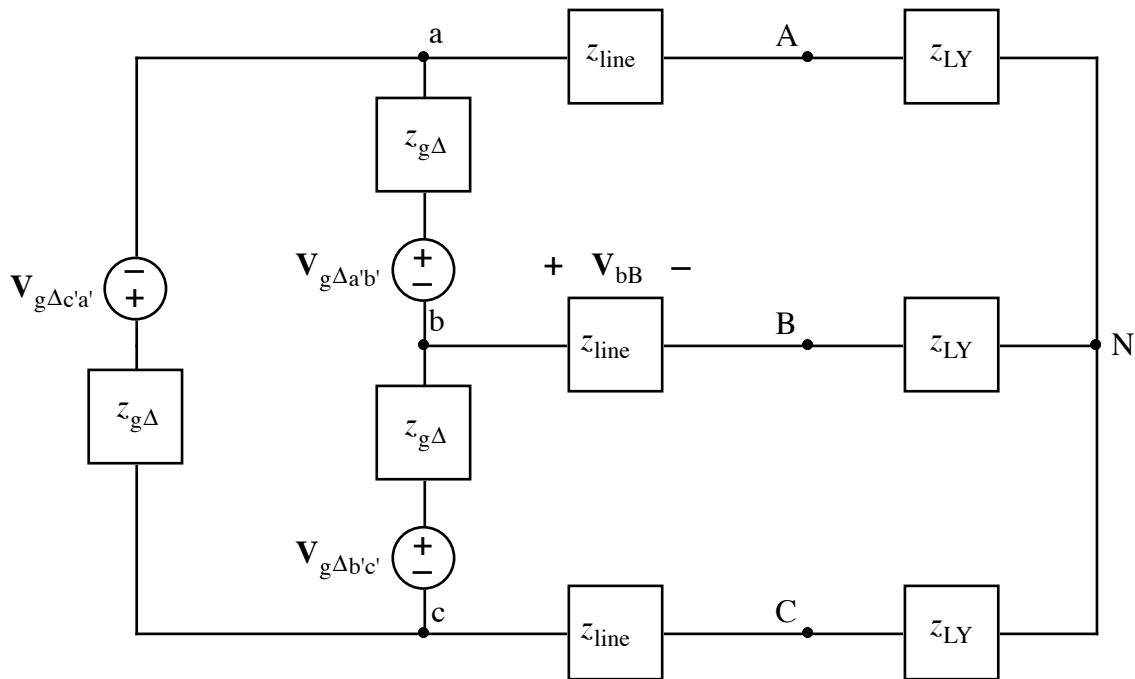

- a) Given  $\omega = 1\text{M rad/s}$ , find the value of  $C$  that makes  $z_{LY} = -j1.01 \Omega$ . Note that  $z_{LY}$  is the equivalent impedance of the entire circuit.




$$\begin{aligned} V_{g\Delta a'b'} &= 168\angle 0^\circ \text{ V} & z_{g\Delta} &= j0.9 \Omega \\ V_{g\Delta b'c'} &= 168\angle -120^\circ \text{ V} & z_{line} &= j1.68 \Omega \\ V_{g\Delta c'a'} &= 168\angle +120^\circ \text{ V} & z_{LY} &= -j1.01 \Omega \end{aligned}$$

- b) For the above 3-phase balanced circuit, find the numerical value of the phasor voltage  $V_{bB}$ .

sol'n: a) We replace the secondary with reflected impedance,  $z_r$ :

$$z_r = \frac{(\omega M)^2}{z_{\text{secondary tot}}} = \frac{(0.1)^2}{j0.015 + \frac{1}{j\omega C}}$$

model:

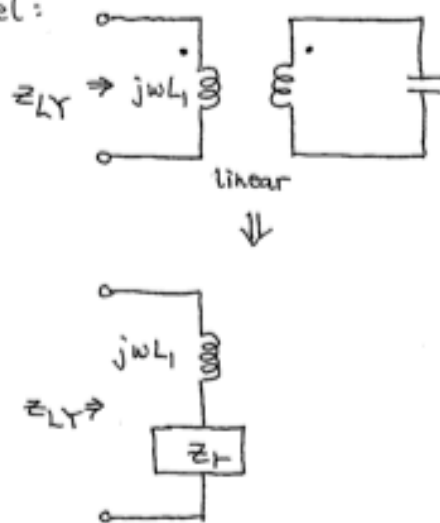

$$\text{Thus, } z_{LY} = j\omega L_1 + z_r = -j1.01\Omega$$

$$\text{or } z_r = -j2\Omega$$

$$\text{or } \frac{(0.1)^2}{j0.015 + \frac{1}{j\omega C}} = -j2\Omega$$

$$\text{or } \frac{1}{j0.015 + \frac{1}{j\omega C}} = -j200\Omega$$

$$\text{or } j0.015 + \frac{1}{j\omega C} = \frac{1}{-j200\Omega}$$

$$\text{or } 0.015 + \frac{-1}{\omega C} = \frac{1}{200\Omega}$$

$$\text{or } -\frac{1}{\omega C} = 0.005 - 0.015 = -0.01$$


$$\text{or } \omega C = 100$$

$$\text{or } C = \frac{100}{\omega} = \frac{100}{1 \text{ Mr/s}}$$

$$\text{or } C = 100 \mu\text{F}$$

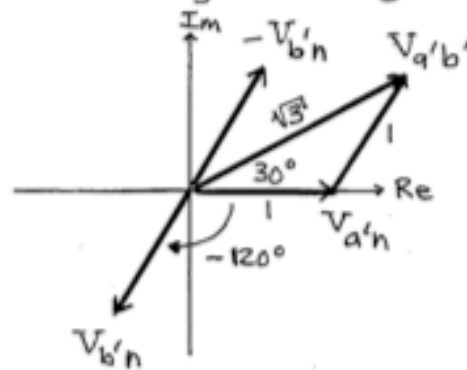b) We first transform the delta generator to a  $\Upsilon$  configuration.

$$Z_{g\Upsilon} = \frac{Z_{g\Delta}}{3} = j\frac{0.9}{3} \Omega = j0.3 \Omega$$



$$V_{a'b'} = V_{a'n} - V_{b'n} = V_{a'n} - V_{a'n} \angle -120^\circ$$


$$\text{or } V_{a'b'} = V_{a'n} (1 - \angle -120^\circ)$$

$$\text{or } V_{a'b'} = V_{a'n} \sqrt{3} \angle 30^\circ \quad (\text{from diagram})$$

$$\text{or } V_{a'n} = V_{a'b'} \frac{1}{\sqrt{3}} \angle -30^\circ = \frac{168}{\sqrt{3}} \angle -30^\circ$$

$$V_{a'n} = 97 \angle -30^\circ \text{ V}$$

single-phase model:

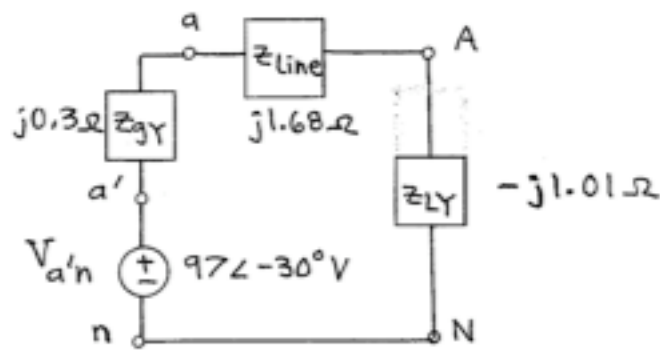

We find  $V_{bB}$  by shifting  $V_{aA}$  by  $-120^\circ$ .

$$V_{aA} = V_{a'n} \cdot \frac{z_{Line}}{z_{gY} + z_{Line} + z_{LY}}$$

or

$$V_{aA} = 97 \angle -30^\circ V \cdot \frac{j 1.68 \Omega}{j0.3 + j1.68 \Omega - j1.01 \Omega}$$

or

$$V_{aA} = 97 \angle -30^\circ V \frac{1.68}{0.97}$$

or

$$V_{aA} = 100 (1.68) \angle -30^\circ V$$

$$V_{aA} = 168 \angle -30^\circ V$$

We shift  $V_{aA}$  by  $-120^\circ$  to obtain  $V_{bB}$ :

$$V_{bB} = 168 \angle -150^\circ V$$

(This illustrates that the voltage on the line may be as large as the generator voltage.)