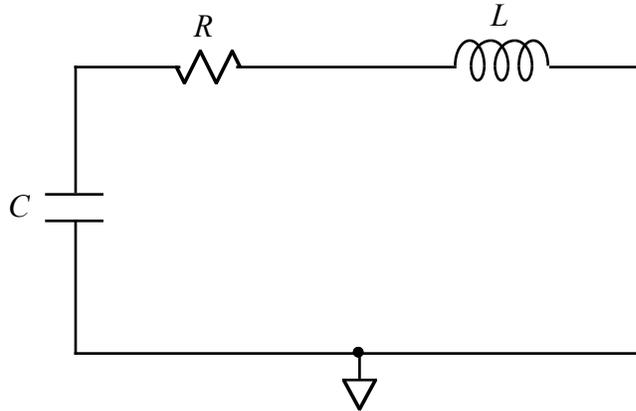


Ex:



$$L = 100 \mu\text{H} \quad C = 400 \mu\text{F}$$

The above circuit may be used to generate a note for an electronic synthesizer.

- Find the value of R that will make the circuit oscillate at 440 Hz, (corresponding to an 'A' note). Remember to convert Hz to rad/s.
- Find the value of the damping factor, α , for your circuit.

SOL'N: a) The oscillation referred to in the problem must be the oscillation seen in under-damped RLC circuits, since over- and critically-damped circuits have only non-oscillatory solutions. The rate of oscillation in under-damped circuits is the damping frequency, ω_d . We convert the damping frequency, f_d , given in the problem statement in units of Hertz (or cycles per second) to the damping frequency, ω_d , in units of radians per second:

$$\omega_d = 440 \text{ Hz} \cdot 2\pi \approx 2764.6 \text{ r/s}$$

The formula for the damping frequency, in terms of damping factor, α , and resonant frequency, ω_o , is the same for both series and parallel RLC circuits:

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$$

Using our value for ω_d , we obtain the following equation:

$$\sqrt{\omega_o^2 - \alpha^2} = 2764.6 \text{ or } \omega_o^2 - \alpha^2 = 2764.6^2 \approx 7.643 \text{ Mr}^2/\text{s}^2$$

The value of the resonant frequency, ω_o , is always given by the following formula:

$$\omega_0^2 = \frac{1}{LC}$$

or

$$\omega_0^2 = \frac{1}{100\mu \cdot 400\mu} = \left(\frac{1}{200\mu}\right)^2 (\text{r/s})^2 = (5\text{k})^2 (\text{r/s})^2 = 25 \text{ M } (\text{r/s})^2$$

Using the prior equations, we solve for α^2 :

$$\alpha^2 = \omega_0^2 - 7.643 \text{ Mr}^2/\text{s}^2 = 25 \text{ M} - 7.643 \text{ Mr}^2/\text{s}^2 \approx 17.357 \text{ Mr}^2/\text{s}^2$$

or

$$\alpha \approx 4.166 \text{ kr/s}$$

For a series RLC circuit, α is one-half the inverse of the L/R time constant:

$$\alpha = \frac{R}{2L}$$

Now we can solve for R :

$$R = 2\alpha L = 2(4.166 \text{ k})100\mu \Omega = 833 \text{ m}\Omega$$

SOL'N: b) The value of α was found in the solution to part (a):

$$\alpha \approx 4.166 \text{ kr/s}$$