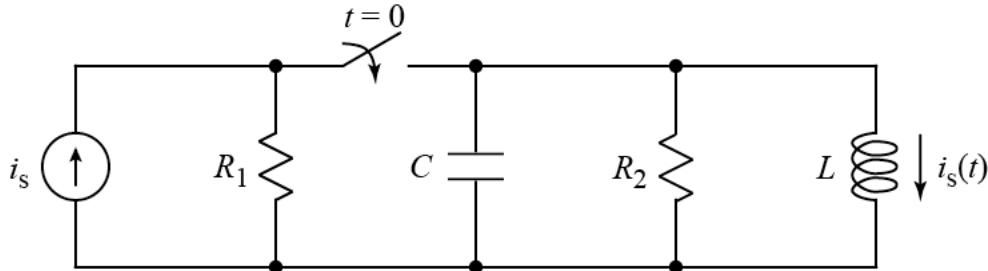


Ex:



After being open for a long time, the switch closes at $t = 0$.

$$i_s = 4 \text{ mA} \quad C = 2 \text{ } \mu\text{F} \quad R_1 = 200 \text{ } \Omega \quad R_2 = 200 \text{ } \Omega$$

- If $L = 125 \text{ mH}$, find the characteristic roots, s_1 and s_2 , for the above circuit.
- If $L = 11.834 \text{ mH}$, find the damping frequency, ω_d .
- Find the value of L that makes the circuit critically-damped, and find $i_L(t)$ for that value of L .

SOL'N: a) Because the switch closes at $t = 0$, all of the components are in the circuit that we use to calculate the characteristic roots. All the components are in parallel, so we have a parallel RLC circuit, with the two R 's in parallel acting as the following equivalent R :

$$R = R_1 \parallel R_2 = 200 \text{ } \Omega \parallel 200 \text{ } \Omega = 100 \text{ } \Omega$$

For a parallel RLC circuit, α is found as

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 100 \text{ } \Omega \cdot 2 \text{ } \mu\text{F}} = 2.5 \text{ k/s}$$

The resonant frequency squared is always $1/LC$:

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{125 \text{ mH} \cdot 2 \text{ } \mu\text{F}} = (2 \text{ kr/s})^2$$

The formula for the characteristic roots is always as follows:

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Using our circuit, we obtain the roots:

$$s_{1,2} = -2.5 \text{ k} \pm \sqrt{(2.5 \text{ k})^2 - (2 \text{ k})^2} \text{ r/s} = -2.5 \text{ k} \pm 1.5 \text{ k r/s}$$

or

$$s_{1,2} = -1\text{kr/s and } -4\text{kr/s}$$

SOL'N: b) Repeating the calculations from part (a) with the new value of L yields the following results, (α is unchanged):

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{11.834\text{mH} \cdot 2\mu\text{F}} \approx (6\text{kr/s})^2$$

$$s_{1,2} = -2.5\text{k} \pm \sqrt{(2.5\text{k})^2 - (6.5\text{k})^2} \text{ r/s} \approx -2.5\text{k} \pm j6\text{kr/s}$$

The damping frequency is the imaginary part of the roots, which may also be found by taking the negative of the quantity under the square root (so as to obtain a positive value):

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \approx \sqrt{(6.5\text{k})^2 - (2.5\text{k})^2} = 6 \text{ kr/s}$$

SOL'N: c) Critical damping occurs when $\alpha = \omega_0$. Repeating the calculations from part (a) with the new value of L yields the following results, (α is unchanged):

$$\alpha = \frac{1}{2RC} = \omega_0 = \frac{1}{\sqrt{LC}}$$

If we invert both sides of the equation, we have the following result:

$$2RC = \sqrt{LC}$$

Using this equation, we solve for L :

$$L = 4R^2C = 4(100\Omega)^2 2\mu\text{F} = 80\text{mH}$$


The value of α was found in part (a) and is minus the value of the repeated root:

$$s_{1,2} = -\alpha = -2.5\text{kr/s}$$

For critical damping, we use the following form of solution:


$$i_L(t) = A_1 e^{-\alpha t} + A_2 t e^{-\alpha t} + A_3$$

Now we start the circuit analysis.

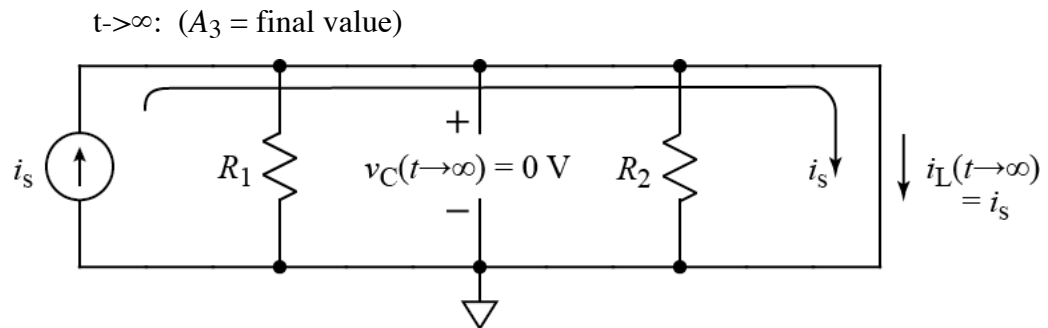

All of i_s will flow through the short formed by the L as time approaches infinity, so the final value of i_L and the value of A_3 will be zero.

$$A_3 = i_s = 4 \text{ mA}$$

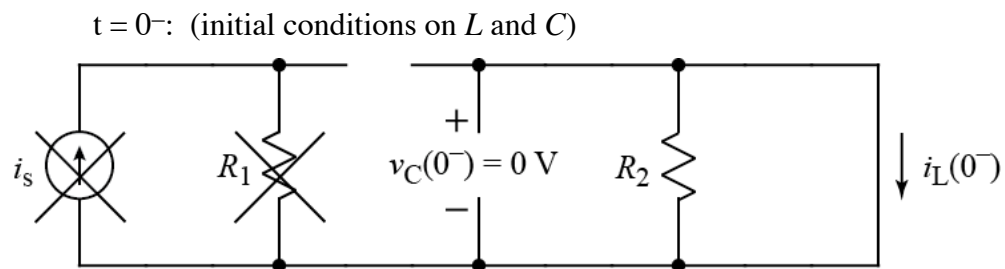

The initial conditions on the L and C will be zero, since there is no source in the circuit for $t < 0$. We match this to the critically damped symbolic solution at $t = 0^+$:

$$i_L(0^+) = 0 \text{ A} = A_1 + A_3 = A_1 + 4 \text{ mA}$$

or

$$A_1 = -4 \text{ mA}$$

Now we match the derivative of the inductor current found from the circuit to the symbolic solution at $t = 0^+$:

$$\left. \frac{di_L(t)}{dt} \right|_{t=0^+} = -\alpha A_1 + A_2 = \frac{v_L(0^+)}{L} = \frac{v_C(0^+)}{L} = 0 \text{ A/s}$$

or

$$A_2 = \alpha A_1 = 2.5\text{k}(-4 \text{ m}) \text{ A/s} = -10 \text{ A/s}$$

$$\text{Thus, } i_L(t) = -4 \text{ mA} \cdot e^{-2.5\text{k}t} - 10 \text{ A} t e^{-2.5\text{k}t} + 4 \text{ mA}.$$