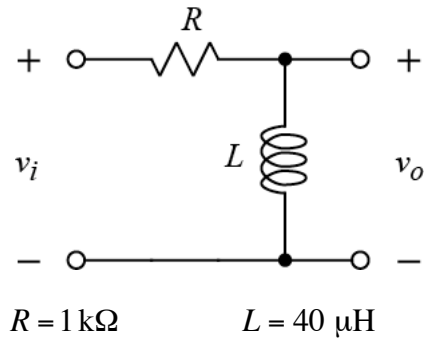





1.




- Determine the transfer function  $V_o/V_i$ .
- Plot  $|V_o/V_i|$  versus  $\omega$ .
- Find the cutoff frequency,  $\omega_c$ .

2.

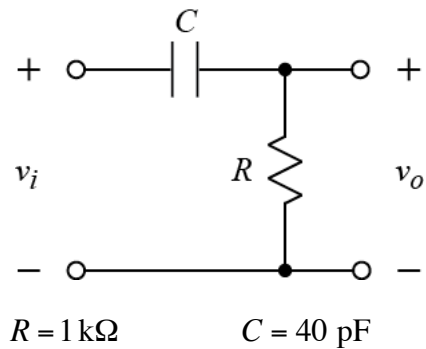


- Determine the transfer function  $V_o/V_i$ .
- Plot  $|V_o/V_i|$  versus  $\omega$ .
- Find the cutoff frequency,  $\omega_c$ .

3.

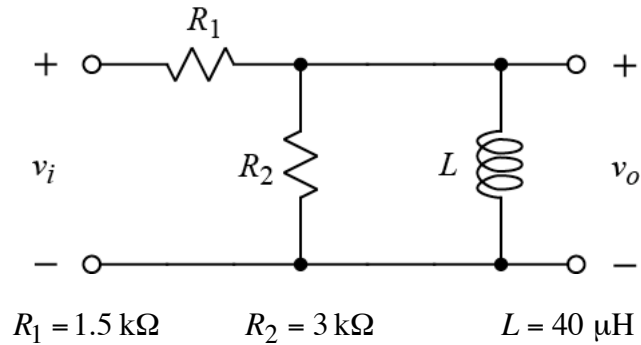

- a) Determine the transfer function  $V_o/V_i$ . **Hint:** use a Thevenin equivalent on the left side.
- b) Plot  $|V_o/V_i|$  versus  $\omega$ .
- c) Find the cutoff frequency,  $\omega_c$ .


4.

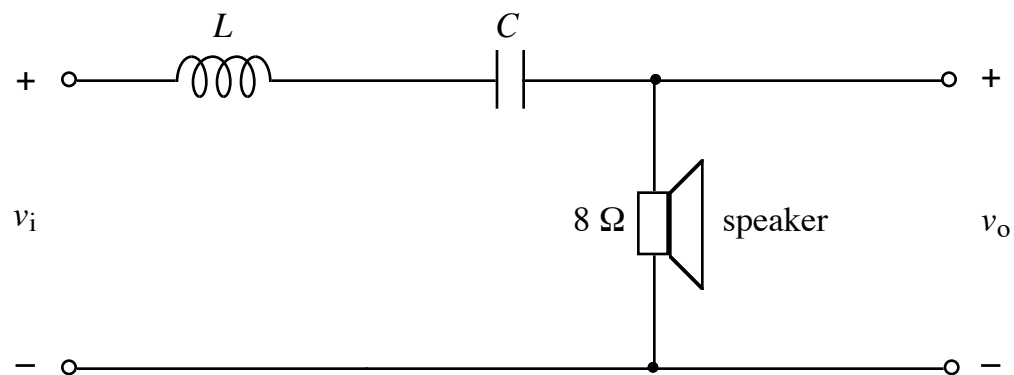

The above circuit is part of a simple crossover network for driving a midrange speaker having an impedance of  $8\Omega$ . The circuit is described at the following web site: <http://www.termpro.com/articles/xover2.html>. A more in-depth discussion of crossover networks may be found at <http://sound.westhost.com/lr-passive.htm>.

- a) The web site describing the above bandpass filter suggests using cutoff frequencies of  $f_{C1} = 130 \text{ Hz}$  and  $f_{C2} = 4 \text{ kHz}$ . Determine the  $L$  and  $C$  values that yield these cutoff frequencies.
- b) Plot  $|V_o/V_i|$  versus  $\omega$ .

5.

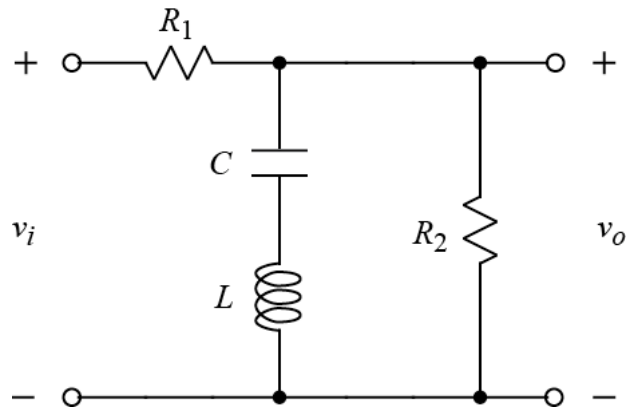

$$R_1 = 18 \Omega$$

$$R_2 = 36 \Omega$$

$$C = 31.25 \mu\text{F} \quad L = 2 \text{ mH}$$

- For the band-reject filter shown above, determine the transfer function  $V_o/V_i$ . **Hint:** move  $R_2$  to the left of  $L$  and  $C$ , and use a Thevenin equivalent.
- Find  $\omega_o$
- Find  $\omega_{C1}$  and  $\omega_{C2}$
- Find  $\beta$  and  $Q$