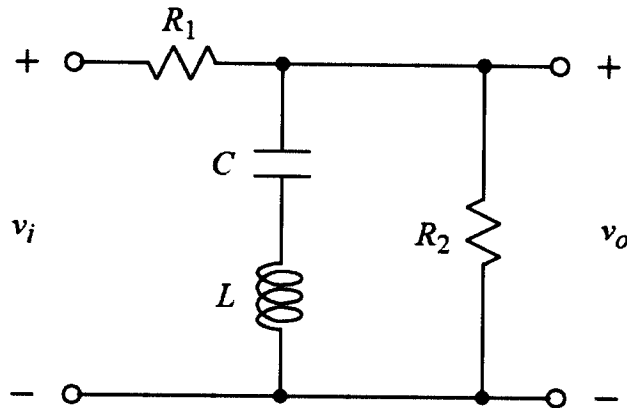



Ex:



$$R_1 = 18 \Omega \quad R_2 = 36 \Omega \quad C = 31.25 \mu\text{F} \quad L = 2 \text{ mH}$$

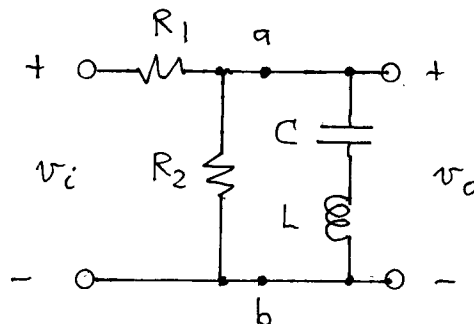- a) For the band-reject filter shown above, determine the transfer function  $V_o/V_i$ .  
**Hint:** move  $R_2$  to the left of  $L$  and  $C$ , and use a Thevenin equivalent.
- b) Find  $\omega_0$
- c) Find  $\omega_{C1}$  and  $\omega_{C2}$
- d) Find  $\beta$  and  $Q$

sol'n: a) We redraw the circuit with  $R_2$  to the left of  $L$  and  $C$ :



We remove  $L$  and  $C$  to find the Thevenin equivalent of  $v_i$ ,  $R_1$ , and  $R_2$ . We then measure the voltage across  $R_2$ . The voltage-divider formula yields the answer:

$$b) \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2m \cdot 31.25 \mu}} \text{ r/s}$$

$$\omega_0 = 4 \text{ k r/s}$$

c) To find  $\omega_{c1}$  and  $\omega_{c2}$ , we solve

$$|H| = \frac{1}{\sqrt{2}} \max_{\omega} |H|$$

The  $\max |H|$  will occur when the imaginary part in the denominator is zero. This occurs when  $\omega = 0$  or  $\omega \rightarrow \infty$ . The value we get is

$$\max_{\omega} |H| = \frac{R_2}{R_1 + R_2}$$

So we solve

$$|H| = \left| \frac{\cancel{R_2}}{R_1 + R_2} \right| \left| \frac{1}{1 - j \frac{R_{Th}}{\omega L - \frac{1}{\omega C}}} \right| = \frac{\cancel{R_1}}{R_1 + R_2} \cdot \frac{1}{\sqrt{2}}$$

The sol'n will occur when

$$\left| 1 - j \frac{R_{Th}}{\omega L - \frac{1}{\omega C}} \right| = \sqrt{2}$$

$$\text{Since } |a + jb| = \sqrt{a^2 + b^2}$$


$$\text{we must have } \frac{R_{Th}}{\omega L - \frac{1}{\omega C}} = \pm 1.$$

$$v_{TH} = v_i \frac{R_2}{R_1 + R_2}$$

To find  $R_{TH}$ , we turn off  $v_i$ , which becomes a wire, and look in from a, b. We see  $R_{TH} = R_1 \parallel R_2$ .

$$R_{TH} = R_1 \parallel R_2$$

Our new circuit model = (freq. domain)

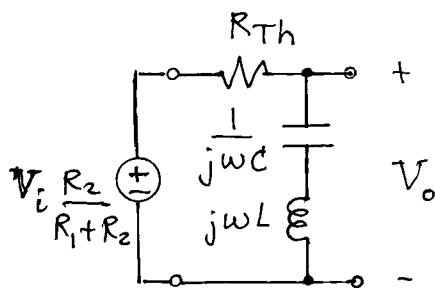

Our transfer function is

$$H(j\omega) = \frac{V_o}{V_i} = \frac{j\omega C + j\omega L}{R_{TH} + \frac{1}{j\omega C} + j\omega L} \cdot \frac{v_i R_2}{R_1 + R_2}$$

$$= \frac{R_2}{R_1 + R_2} \frac{j(\omega L - \frac{1}{\omega C})}{R_{TH} + j(\omega L - \frac{1}{\omega C})}$$

Dividing top and bottom by  $j(\omega L - \frac{1}{\omega C})$  yields a cleaner form:

$$H(j\omega) = \frac{R_2}{R_1 + R_2} \frac{1}{1 - j \frac{R_{TH}}{\omega L - \frac{1}{\omega C}}} = \frac{2/3}{1 - j \frac{12}{\omega \cdot 2m - \frac{1}{3125\mu F}}}$$

$$\text{or } R_{Th} = \pm \left( \omega L - \frac{1}{\omega C} \right)$$

$$\text{or } \pm R_{Th} = \omega L - \frac{1}{\omega C}$$

$$\text{or } \pm R_{Th} \omega = \omega^2 L - \frac{1}{C}$$

$$\text{or } \omega^2 L \pm R_{Th} \omega - \frac{1}{C} = 0$$

$$\text{or } \omega^2 \pm \frac{R_{Th}}{L} \omega - \frac{1}{LC} = 0$$

$$\text{or } \omega_{c1,2} = \pm \frac{R_{Th}}{2L} \pm \sqrt{\left( \frac{R_{Th}}{2L} \right)^2 + \frac{1}{LC}}$$

We use the  $\omega > 0$  roots:

$$\omega_{c1,2} = \pm \frac{R_{Th}}{2L} + \sqrt{\left( \frac{R_{Th}}{2L} \right)^2 + \frac{1}{LC}}$$

$$\frac{R_{Th}}{2L} = \frac{12 \Omega}{2(2 \text{ mH})} = 3 \text{ k r/s}$$

$$\frac{1}{LC} = (4 \text{ k})^2 (\text{r/s})^2 = \omega_0^2 \text{ (above)}$$

$$\omega_{c1,2} = \pm 3 \text{ k} + \sqrt{(3 \text{ k})^2 + (4 \text{ k})^2} \text{ r/s} = \pm 3 \text{ k} + 5 \text{ k r/s}$$

$$\omega_{c1,2} = 2 \text{ k r/s} \text{ and } 8 \text{ k r/s}$$

$$\text{d) } \beta \equiv \omega_{c2} - \omega_{c1} = \frac{R_{Th}}{L} = \frac{12 \Omega}{2 \text{ mH}} = 6 \text{ k r/s}$$

$$Q \equiv \frac{\omega_0}{\beta} = \frac{4 \text{ k r/s}}{6 \text{ k r/s}} = \frac{2}{3}$$