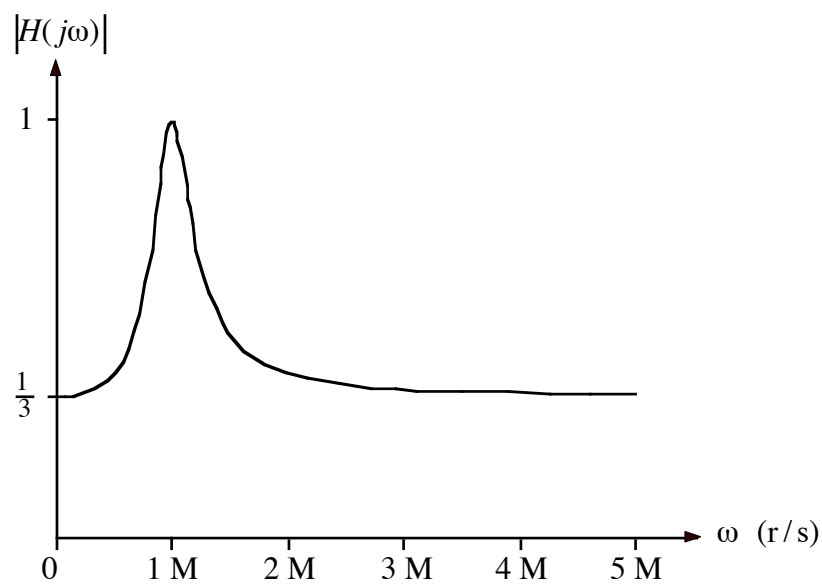


Ex:



Given the resistor connected as shown and using not more than one each R, L, and C in the dashed-line box, design a circuit to go in the dashed-line box that will produce the **band-pass**  $|H(j\omega)|$  vs.  $\omega$  shown above. That is:

$$\max_{\omega} |H(j\omega)| = 1 \text{ and occurs at } \omega_0 = 1 \text{ M r/s}$$

$$|H(j\omega)| = \frac{1}{3} \text{ at } \omega = 0 \quad \text{and} \quad \lim_{\omega \rightarrow \infty} |H(j\omega)| = \frac{1}{3}$$

If you use a C in your solution, use  $C = 0.5 \text{ nF}$ .


sol'n: To achieve a gain of one, i.e.,  $|H|=1$ , at  $\omega_0 = 1\text{Mr/s}$  we need to satisfy one of two following conditions:

- 1) There is an open circuit from the top rail to the bottom rail when  $\omega = \omega_0$ ,
- or 2) There is a short circuit in the top rail connecting the input directly to the output when  $\omega = \omega_0$ .

Given the  $1\text{k}\Omega$  resistor on the right side, only condition (2) is possible.

To achieve the short circuit at  $\omega_0 = 1\text{Mr/s}$ , we use a series L and C.

The circuit thus far:

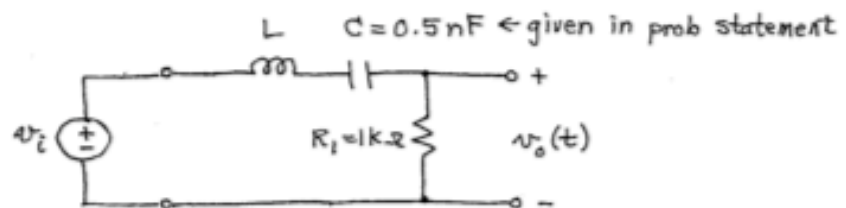


To find L, we have  $\omega_0^2 = \frac{1}{LC} \Rightarrow L = \frac{1}{\omega_0^2 C}$

$$L = \frac{1}{(1\text{M})^2 \frac{1}{2}\text{n}} \text{ H} = 2 \text{ mH}$$

The above circuit is incomplete, as  $H(j\omega)$  will be zero at  $\omega = 0$ , (when the C becomes an open circuit), and  $H(j\omega)$  will be zero as  $\omega \rightarrow \infty$ , (when the L becomes an open circuit).

To achieve a gain of  $1/3$ , i.e.  $|H| = \frac{1}{3}$ , at  $\omega = 0$  and  $\omega \rightarrow \infty$  the L and C must be bypassed by a resistor.

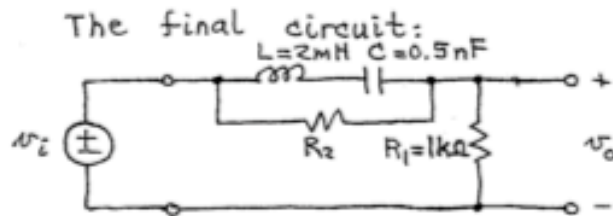

At  $\omega=0$  and  $\omega\rightarrow\infty$ , the circuit effectively consists of the  $v_i$  source and the two  $R$ 's. Using the voltage-divider formula, we have (for  $\omega=0$  or  $\omega\rightarrow\infty$ )

$$|H(j\omega)| = \frac{1}{3} = \frac{R_1}{R_1 + R_2}.$$

This means  $R_1$  is  $\frac{1}{3}$  of the total of  $R_1 + R_2$ .

In other words, the ratio of  $R_1$  to the total of  $R_1 + R_2$  is 1 to 3. It follows that  $R_1 + R_2 = 3\text{k}\Omega$ , since  $R_1 = 1\text{k}\Omega$ .

Thus,  $R_2 = 2\text{k}\Omega$ .

Note: Does  $R_2$  alter the circuit's behavior at  $\omega_0 = 1/\text{Mr/s}$ ? Because the  $L$  and  $C$  act like a short circuit at  $\omega_0$ ,  $R_2$  is bypassed and leaves the circuit response unaltered at  $\omega_0$ .

Note: Finding the cutoff frequencies for this circuit is difficult owing to the  $R$ 's from the  $L$  and  $C$  in the expression for  $H(j\omega)$ .