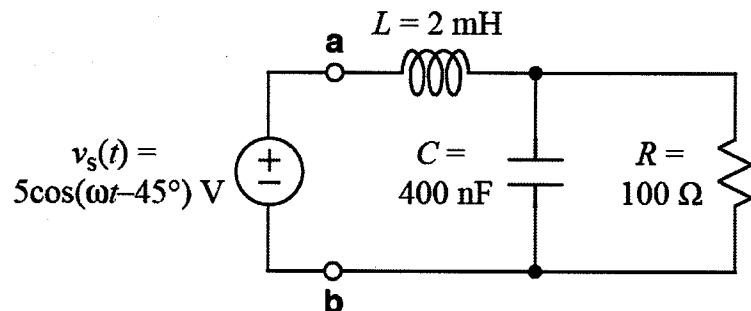


Ex:

Note: $\omega = 25 \text{ k r/s.}$ Do the following for the impedance to the right of the a, b terminals:

- Calculate complex power $S = P + jQ$.
- Calculate average (or DC) power.
- Calculate maximum instantaneous power.
- Sketch the power waveform, $p(t)$.

sol'n: a) We calculate total impedance to right of a, b so we can use the following formula for S :

$$S = \frac{|V|^2}{Z} \quad \text{where } V = V_S$$

Total Z :

$$Z = j\omega L + R \parallel \frac{1}{j\omega C}$$

$$j\omega L = j 25k \cdot 2m\Omega = j 50\Omega$$

$$\frac{1}{j\omega C} = \frac{-j}{25k \cdot 400n} = \frac{-j}{10kkn} = -j100\Omega$$

$$Z = j 50\Omega + 100 \parallel -j 100\Omega$$

$$= j 50\Omega + 100 \cdot 1 \parallel -j$$

$$= j 50\Omega + 100 \cdot \frac{-j}{1-j}$$

$$z = j50\Omega + 100 \cdot \frac{-j}{1-j} \frac{1+j}{1+j} \Omega$$

$$= j50\Omega + 100 \frac{1-j}{2} \Omega$$

$$= j50\Omega + 50\Omega - j50\Omega$$

$$z = 50\Omega$$

Thus, $S = \frac{|V_S|^2}{2 \cdot z^*} = \frac{5^2}{(2)50\Omega} = \frac{1}{4} \text{ VA}$

Note: Because z is real, $z^* = z$ and S is real.

b) $S = P + jQ$ so $P = \text{Re}[S]$, $Q = \text{Im}[S]$.

$$P = \frac{1}{4} \text{ W} \quad \text{Note: } Q = 0 \text{ here.}$$

c) The max instantaneous power is the DC power level, P , plus the magnitude of the sinusoidal part of the power waveform, $|S|$.

$$\max_t p(t) = P + |S| = P + P = \frac{1}{2} \text{ W}$$

d) Since $S = P$ is real, the phase shift of the sinusoidal part of $p(t)$ has zero phase shift.

