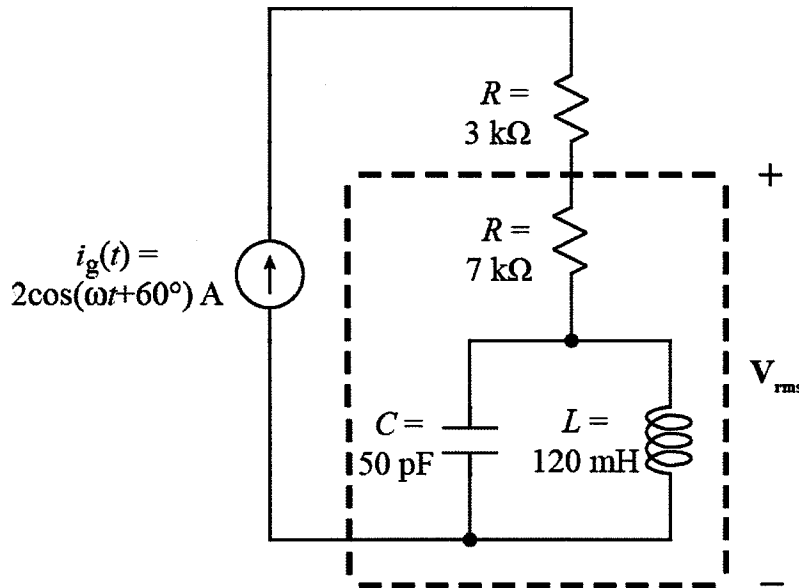


Ex:



- Calculate  $V_{\text{rms}}$ . Note:  $\omega = 1 \text{ Mr/s}$ .
- Calculate the complex power,  $S$ , for the components inside the box.

sol'n a) If we convert the current source to rms units, then a calculation of  $V_{\text{rms}}$  is accomplished by using Ohm's law:

$$V_{\text{rms}} = I_{\text{rms}} \cdot Z_{\text{box}}$$

where

$$Z_{\text{box}} = R + j\omega L \parallel \frac{1}{j\omega C}$$

We have

$$j\omega L = j1\text{M} \cdot 120\text{m}\Omega = j120\text{k}\Omega$$

$$\frac{1}{j\omega C} = \frac{1 \Omega}{j1\text{M} \cdot 50\text{p}} = -j20\text{k}\Omega$$

$$j\omega L \parallel \frac{1}{j\omega C} = j20\text{k} \cdot 6 \parallel -1 = j20\text{k} \left( \frac{-6}{5} \right)$$

$$\parallel = -j24\text{k}\Omega$$

$$\text{Thus, } z_{\text{box}} = 7k\Omega - j24k\Omega.$$

For the current source, the current in rms is the phasor current divided by  $\sqrt{2}$ :

$$I_{g\text{rms}} = \frac{I_g}{\sqrt{2}} = \frac{2\angle 60^\circ}{\sqrt{2}} = \sqrt{2}\angle 60^\circ A_{\text{rms}}$$

$$\begin{aligned}\text{Thus, } V_{\text{rms}} &= I_{g\text{rms}} z_{\text{box}} \\ &= \sqrt{2}\angle 60^\circ A_{\text{rms}} \cdot (7k - j24k)\Omega \\ &= \sqrt{2}\angle 60^\circ A_{\text{rms}} \cdot 25k\Omega\angle -73.7^\circ\end{aligned}$$

$$V_{\text{rms}} = 25\sqrt{2}kV_{\text{rms}}\angle -13.7^\circ$$

$$\text{or } V_{\text{rms}} = 9.6k - j8.1k V_{\text{rms}}$$

b) It is convenient here to use the following formula for  $S$ :

$$\begin{aligned}S &= |I_{\text{rms}}|^2 z \\ &= 2^2 (7k - j24k)\Omega\end{aligned}$$

$$S = 28 - j96 \text{ kVA}$$

$$\text{or } S = 100\angle -73.7^\circ \text{ kVA}$$