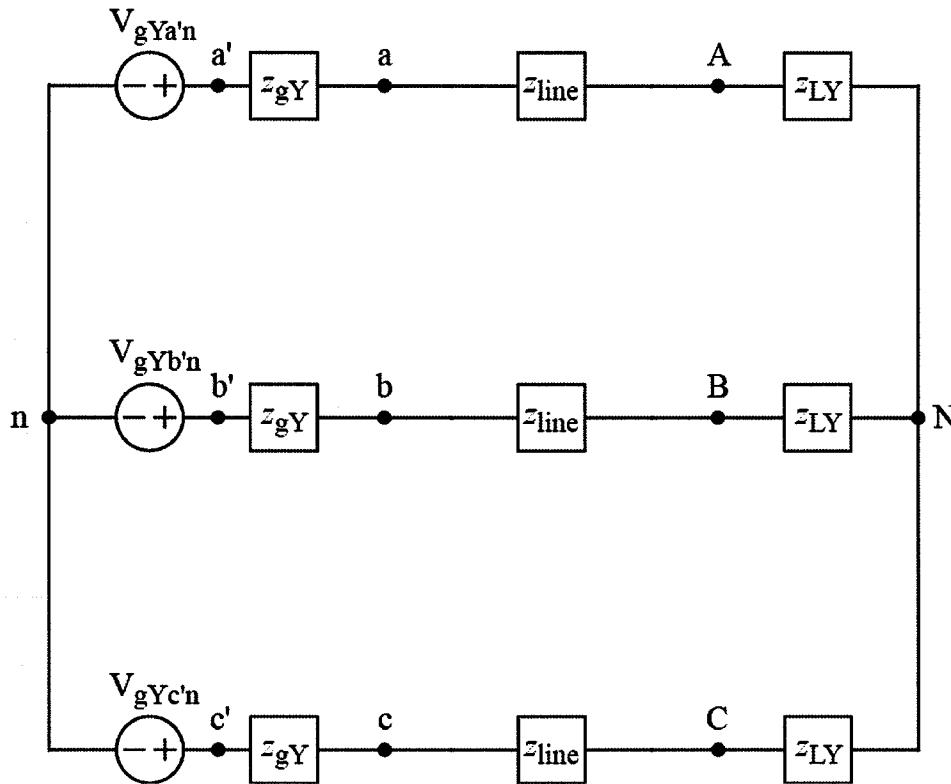


Ex:




$$V_{gYa'n} = 120\angle 0^\circ \text{ V} \quad z_{gY} = j0.3 \Omega$$

$$V_{gYb'n} = 120\angle +120^\circ \text{ V} \quad z_{line} = j0.6 \Omega$$

$$V_{gYc'n} = 120\angle -120^\circ \text{ V} \quad z_{LY} = 3 - j0.1 \Omega$$

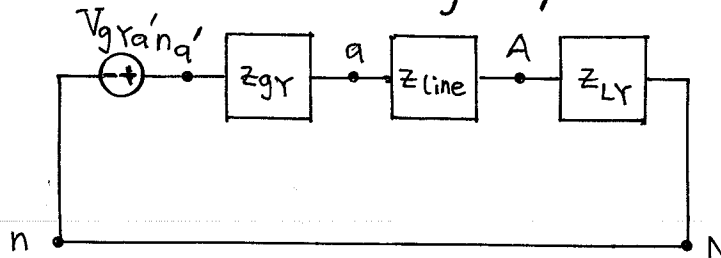- a) Draw the single-phase equivalent circuit.
- b) Calculate V_{aA} .

sol'n: a) This 3-phase circuit is already in a Y-Y configuration. Thus, the single phase model is obtained by adding a wire from n to N , (which has no effect on the circuit since the voltages and currents in a 3-phase circuit sum to zero). Then we use the added wire and the components in the a-phase to create the single-phase model.



$$V_{g a'n'} = 120 \angle 0^\circ \text{ V} \quad z_{gY} = j0.3 \Omega$$

$$z_{line} = j0.6 \Omega$$

$$z_{LY} = 3 - j0.1 \Omega$$

b) V_{aA} in the original circuit is outside of the generator and the load. Therefore V_{aA} is the same in the original circuit and in the single-phase model.

In the single-phase model, V_{aA} is given by a voltage-divider:

$$V_{aA} = V_{g a'n'} \cdot \frac{z_{line}}{z_{gY} + z_{line} + z_{LY}}$$

$$= \frac{120 \angle 0^\circ \text{ V} \cdot j0.6}{j0.3 + j0.6 + 3 - j0.1 \Omega}$$

$$\begin{aligned}V_{aA} &= 120 \angle 0^\circ \text{ V} \cdot \frac{0.6 \angle -90^\circ}{3 + j0.8} \\&= 120 \angle 0^\circ \text{ V} \cdot \frac{0.6 \angle -90^\circ}{3.1 \angle 14.9^\circ} \\&= \frac{120(0.6) \text{ V} \angle 0^\circ - 90^\circ - 14.9^\circ}{3.1}\end{aligned}$$

$$V_{aA} = 23.2 \angle -104.9^\circ \text{ V}$$