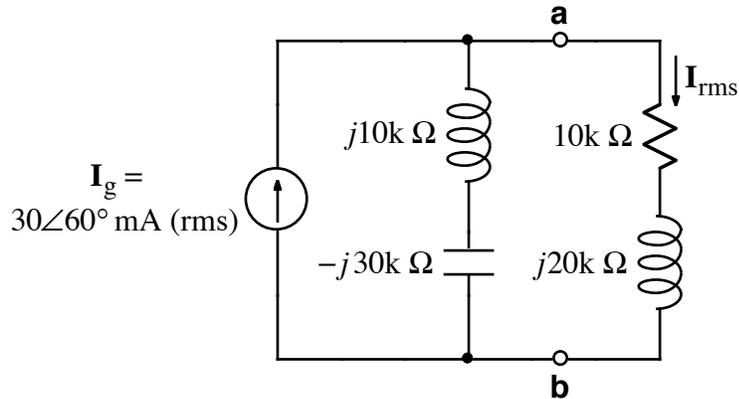


Ex:



- Calculate the value of rms voltage, \mathbf{I}_{rms} , flowing in the circuit to the right of terminals **a** and **b**.
- Calculate the complex power, S , for the circuit to the right of terminals **a** and **b**. Include appropriate units for S .

SOL'N: a) We use the current divider formula to find \mathbf{I}_{rms} :

$$\mathbf{I}_{\text{rms}} = \mathbf{I}_g \frac{j10k - j30k \Omega}{j10k - j30k + 10k + j20k \Omega} = 30\angle 60^\circ \text{ mA (rms)} \frac{-j20k}{10k}$$

or

$$\mathbf{I}_{\text{rms}} = 30\angle 60^\circ \text{ mA (rms)}(-j2) = 30\angle 60^\circ \cdot 2\angle -90^\circ \text{ mA (rms)}$$

or

$$\mathbf{I}_{\text{rms}} = 60\angle -30^\circ \text{ mA (rms)}$$

b) We can use the following convenient formula for S :

$$S = |\mathbf{I}_{\text{rms}}|^2 z = [60 \text{ mA (rms)}]^2 (10k + j20k \Omega)$$

or

$$S = 3.6k \text{ mm} \cdot (10k + j20k \Omega) = 36 + j72 \text{ VA}$$