
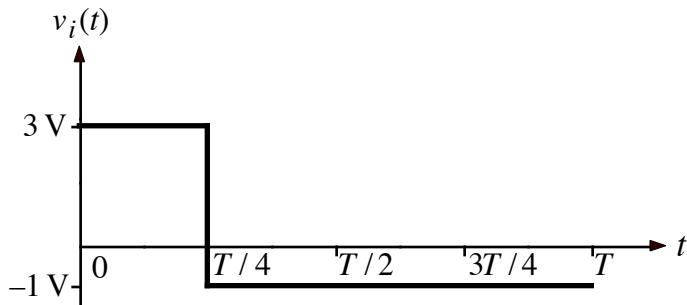


Ex:

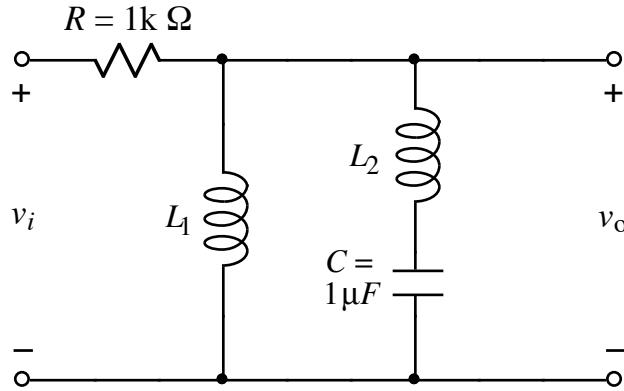

$T$  = one period of  $v_i(t) = 2\pi$  ms

$$v_i(t) = \begin{cases} 3 \text{ V} & 0 < t \leq T/4 \\ -1 \text{ V} & T/4 < t \leq T \end{cases}$$

- a) Find values of  $L_1 \neq 0$  and  $L_2 \neq 0$  for the above filter circuit such that the magnitude of the transfer function equals one for the fundamental and zero for the second harmonic of  $v_i(t)$ , also shown above.
- b) Find numerical values of coefficients  $a_v$ ,  $a_1$ , and  $b_1$  for the Fourier series for  $v_i(t)$ :

$$v_i(t) = a_v + \sum_{k=1}^{\infty} a_k \cos(k\omega_0 t) + b_k \sin(k\omega_0 t)$$

sol'n: a) For the circuit configuration given in this problem, we have  $|H|=0$  when  $L_2$  and  $C$  sum to  $0\text{-}\Omega$ , and we have  $|H|=1$  when  $L_1$  in parallel with  $L_2, C$  forms an open circuit.

$$\text{In other words, } j\omega L_2 + \frac{1}{j\omega C} = 0 @ 2\omega_0.$$

$$\text{Since } T = 2\pi \text{ ms}, \omega_0 = \frac{2\pi}{T} = \frac{2\pi}{2\pi \text{ ms}} = 1 \text{ k r/s.}$$

$$\text{So we want } j\omega L_2 + \frac{1}{j\omega C} = 0 @ 2k \text{ r/s}$$

$$\text{or } (2\omega_0)^2 = \frac{1}{L_2 C} = (2k)^2$$

$$\text{or } L_2 = \frac{1}{(2k)^2 \cdot C} = \frac{1}{(2k)^2 1\mu} H = \frac{1}{4} H$$

$$L_2 = 250 \text{ mH}$$

$$\begin{aligned} \text{At } \omega_0 \text{ we have } j\omega_0 L_2 + \frac{1}{j\omega_0 C} &= j1k \cdot \frac{1}{4} + \frac{1}{j1k 1\mu} \\ &= j250 - j1k \\ &= -j750 \Omega \end{aligned}$$

$$\text{We want } j\omega L_1 = j750 \Omega$$

$$\text{or } j1k L_1 = j750 \Omega$$

$$\text{or } L_1 = \frac{3}{4} H = 750 \text{ mH}$$

$$L_1 = 750 \text{ mH}$$

b) To find  $a_V$ , we note that the area on the left side is  $3V \cdot \frac{T}{4}$  and

the negative area on the right side is  $-1V \cdot \frac{3T}{4} = -3V \cdot \frac{T}{4}$ . So the areas


are equal but opposite and cancel out to give.

$$a_V = 0 V$$

(The formal calculation is  $a_V = \frac{1}{T} \int_0^T v_i(t) dt$ .)

To find  $a_1$ , we graphically analyze the area of the integral for the coefficient:
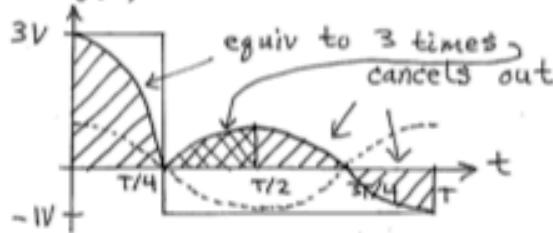
$$a_1 = \frac{2}{T} \int_0^T v_i(t) \cos(\omega_0 t) dt$$




The net area under the curve for  $v_i(t) \cos(\omega_0 t)$  is

$$\begin{aligned} & 4 \int_{T/4}^{T/2} -1 \cdot \cos(\omega_0 t) dt \quad (4 \text{ copies of } \text{--- region}) \\ &= -4 \left[ \frac{\sin(\omega_0 t)}{\omega_0} \right]_{T/4}^{T/2} \\ &= -4 \left( \frac{\sin \pi}{\omega_0} - \frac{\sin \pi/2}{\omega_0} \right) = +2 \frac{T}{\pi} \end{aligned}$$

$$\text{Thus } a_1 = \frac{2}{T} \cdot \frac{T}{\pi} \cdot 2 = \frac{4}{\pi} V$$

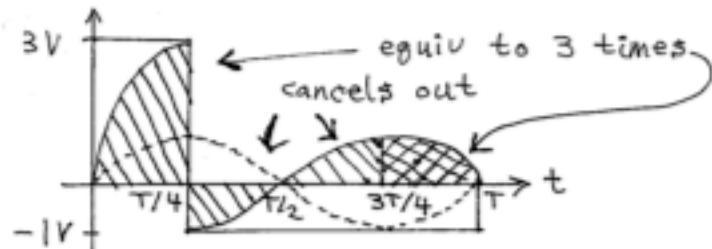For  $b_1$ , we find the area of  $v_i(t) \sin(\omega_0 t)$



We can calculate the area as 4 times the ~~\*\*\*~~ region on the right.  
But the area of the ~~\*\*\*~~ is the same as the ~~\*\*\*~~ region for  $a_1$ , above.

$$\text{So } b_1 = a_1 = \frac{4}{\pi} V.$$