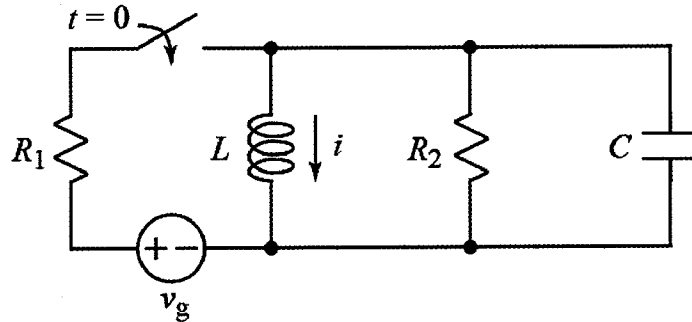


Ex:




After being open for a long time, the switch closes at $t = 0$.

$$v_g = 15 \text{ V} \quad R_1 = 5 \text{ k}\Omega \quad R_2 = 15 \text{ k}\Omega \quad L = 3.6 \text{ mH} \quad C = 100 \text{ pF}$$

- State whether $i(t)$ is under-damped, over-damped, or critically-damped.
- Write a numerical time-domain expression for $i(t)$, $t > 0$, the current through L . This expression must not contain any complex numbers.

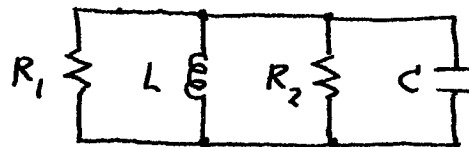sol'n: a) We compute the characteristic roots using the circuit for $t > 0$. We may also turn off pwr sources to see whether we have a series or parallel RLC circuit:



We may combine $R_1 \parallel R_2 = R$, and we have a parallel RLC.

$$s_{1/2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \quad \omega_0^2 = \frac{1}{LC}$$

$$\alpha = \frac{1}{2(5\text{k} \parallel 15\text{k})100\text{p}} = \frac{1}{(2)5\text{k}(1 \parallel 3)100\text{p}}$$

$$\alpha = \frac{1}{(2) 5k \left(\frac{3}{4}\right) 100p} \frac{r/s}{(3) 1000kp} = \frac{4}{3} \frac{r/s}{M} = \frac{4}{3} M r/s$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{(3.6m) 100p} = \frac{1}{0.36p}$$

$$\omega_0^2 = \frac{1}{0.6^2 \mu^2} = \left(\frac{5}{3} M r/s\right)^2$$

$$\sqrt{\alpha^2 - \omega_0^2} = \sqrt{\left(\frac{4}{3} M\right)^2 - \left(\frac{5}{3} M\right)^2} = \sqrt{-\left(\frac{3}{3} M\right)^2}$$

$$\sqrt{\alpha^2 - \omega_0^2} = j 1M r/s$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\frac{4}{3} M \pm j 1M r/s$$


Complex roots \Rightarrow underdamped

b) For our underdamped roots, our form of sol'n is

$$i(t > 0) = A_1 e^{-\alpha t} \cos(\omega_d t) + A_2 e^{-\alpha t} \sin(\omega_d t) + A_3$$

$$\text{where } \alpha = -\frac{4}{3} M r/s, \omega_d = 1M r/s$$

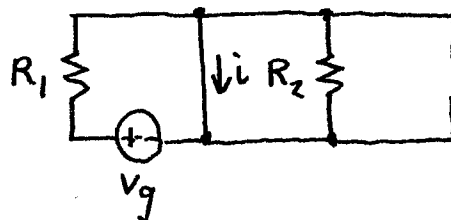We first find $A_3 = i(t \rightarrow \infty)$. As $t \rightarrow \infty$, we treat L as wire and C as open:




$$i = \frac{V_g}{R_1} = \frac{15V}{5k\Omega}$$

$$i = 3 mA = A_3$$

Now we match $i(t > 0)$ to initial conditions.
 We start at $t = 0^-$ to determine what
 L and C have as initial conditions.
 $L = \text{wire}, C = \text{open}$



$t = 0^-:$

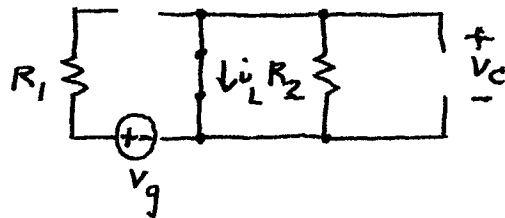

With no power source connected, we
 have $i_L(0^-) = 0 \text{ A}$ and $V_C(0^-) = 0 \text{ V}$.

We model the L and C as sources
 at $t = 0^+$.

$t = 0^+:$

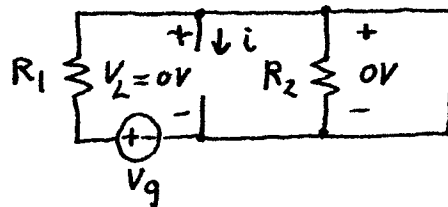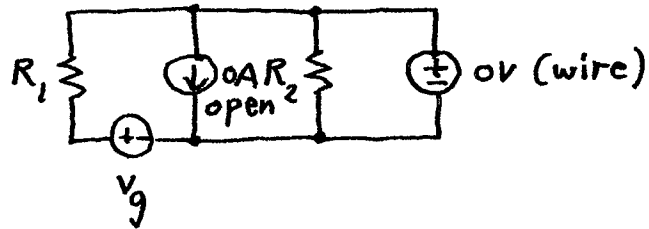

The wire (the C with 0 V) bypasses R_2 .

So we have $V_L = 0 \text{ V}$. Since the L is
 an open, we also have $i(0^+) = 0 \text{ A}$.

For our symbolic sol'n, we have

$$i(0^+) = A_1 + A_3$$

$$i(0^+) = A_1 + A_3 = A_1 + 3 \text{ mA} = 0 \text{ A}$$

$$\text{So } A_1 = -3 \text{ mA}$$

Now we find $\left. \frac{di}{dt} \right|_{t=0^+}$ by writing

$i(t)$ in terms of i_L and/or v_L .

In this case $i(t)$ is i_L .

$$i = i_L$$

We differentiate the eq'n in order to get $\frac{di}{dt} = \frac{v_L}{L}$, which is not a derivative.

$$\left. \frac{di_L}{dt} \right|_{t=0^+} = \left. \frac{v_L}{L} \right|_{t=0^+} = \frac{0V}{L} = 0 \text{ A/s}$$

Our symbolic derivative is

$$\left. \frac{di(0^+)}{dt} \right| = -\alpha A_1 + \omega_d A_2$$

$$\text{so } \left(-\frac{4}{3} \text{ Mr/s} \right) (-3 \text{ mA}) + (1 \text{ Mr/s}) A_2 = 0 \text{ A/s}$$

or

$$A_2 = \frac{-4 \text{ MmA}}{1 \text{ M}} = -4 \text{ mA}$$

so

$$i(t > 0) = -3 e^{-\frac{4}{3} M t} \cos(1 M t) \\ - 4 e^{-\frac{4}{3} M t} \sin(1 M t) \\ + 3 \text{ mA}$$