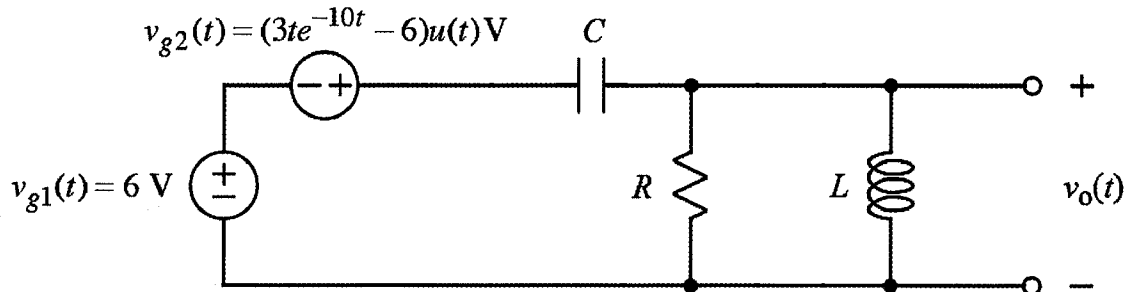


Ex:



Note: The 6 V in the $v_{g1}(t)$ source is always on.

$$C = 1 \mu\text{F} \quad R = 100 \Omega \quad L = 40 \text{ mH}$$

- Write the Laplace transform, $V_g(s)$, of $v_g(t) = v_{g1}(t) + v_{g2}(t)$.
- Draw the s -domain equivalent circuit, including source $V_g(s)$, components, initial conditions for C 's, and terminals for $V_o(s)$.
- Write an expression for $V_o(s)$. You may use the parallel operator (for parallel impedances) in your answer.
- Apply the initial value theorem to find $\lim_{t \rightarrow 0^+} v_o(t)$.

SOL'N: a) Note that $\mathcal{L}\{6\} = \mathcal{L}\{6u(t)\} = \frac{6}{s}$.


$$\mathcal{L}\{v_{g2}(t)\} = \mathcal{L}\{(3te^{-10t} - 6)u(t)\} \text{ V}$$

$$= \frac{3}{(s+10)^2} - \frac{6}{s} \text{ V}$$

$$V_g(s) = \frac{6}{s} + \frac{3}{(s+10)^2} - \frac{6}{s} \text{ V}$$

$$V_g(s) = \frac{3}{(s+10)^2} \text{ V}$$

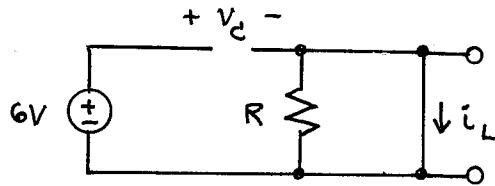- b) We find initial conditions at $t=0^-$.
 $L = \text{wire}$, $C = \text{open}$, $v_{g1} = 6V$, $v_{g2} = 0V$




Using an outside v -loop, we find that we must have $v_c = 6V$.


Because we have an open circuit, $i_L = 0A$.

$$v_c(0^-) = 6V, \quad i_L(0^-) = 0A$$

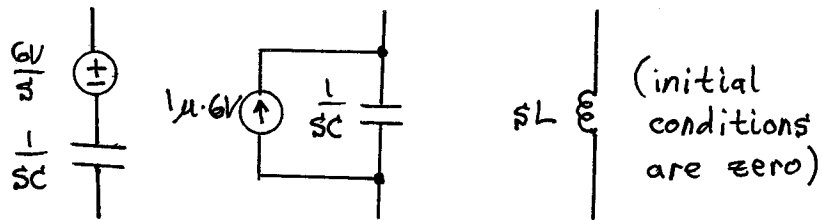Now we can draw the s -domain circuit. We have the following alternatives for initial conditions on the L and C :



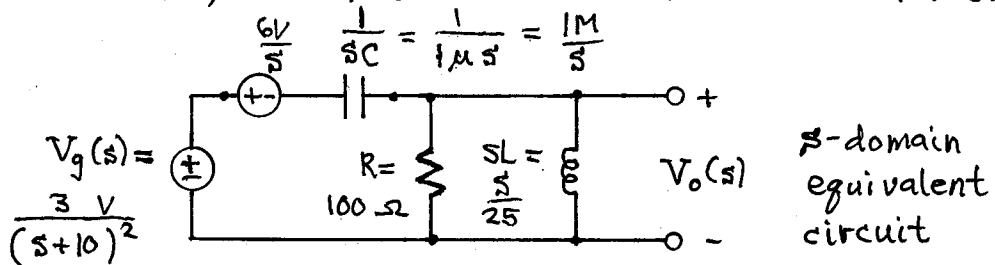Here, a series v -src will be used for C .



c) We sum voltage sources and use a v-divider.

$$V_0(s) = \left(\frac{3V}{(s+10)^2} - \frac{6V}{s} \right) \frac{R \parallel sL}{R \parallel sL + 1/sC}$$

d) Initial value theorem:

$$\lim_{t \rightarrow 0^+} v_0(t) = \lim_{s \rightarrow \infty} sV(s)$$

$$= \lim_{s \rightarrow \infty} s \left[\frac{3V}{(s+10)^2} - \frac{6V}{s} \right] \frac{R \parallel sL}{R \parallel sL + \frac{1}{sC}} V$$

$$= \lim_{s \rightarrow \infty} \left[\frac{3s}{(s+10)^2} - 6 \right] \frac{R \parallel sL}{R \parallel sL + \frac{1}{sC}} V$$

We may ignore all terms in a sum except the highest power of s .

$$= \lim_{s \rightarrow \infty} \left[\frac{3s}{s^2} - 6 \right] \frac{RLs}{R+Ls} V$$

$$= \lim_{s \rightarrow \infty} \left[\frac{3}{s} - 6 \right] \frac{RLs}{Ls} V$$

Small as $s \rightarrow \infty$

$$= \lim_{s \rightarrow \infty} -6V$$

$$\lim_{t \rightarrow 0^+} v_0(t) = -6V$$