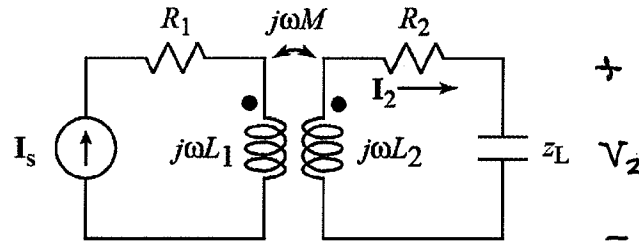



Ex:



$$I_s = 2\angle 45^\circ \text{ A} \quad R_1 = 10 \Omega \quad j\omega L_1 = j10 \Omega \quad j\omega M = j15 \Omega$$

$$R_2 = 30 \Omega \quad j\omega L_2 = j40 \Omega \quad z_L = -j10 \Omega$$

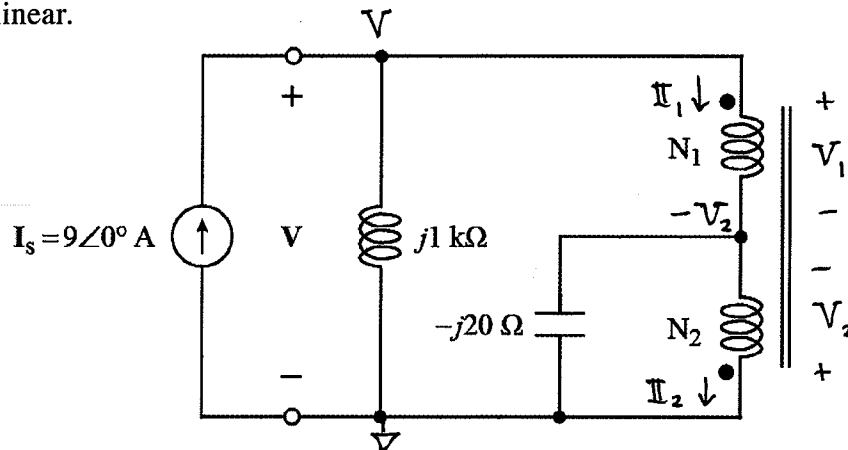- a) Calculate the numerical value of phasor current,  $I_2$ , flowing into the load impedance,  $z_L$ , on the secondary side of the transformer. Note: the transformer is linear.



- b) The turns ratio of the transformer is  $N_1/N_2 = 6$ . Calculate the numerical value of phasor voltage,  $V$ , shown in the diagram. Note: the transformer is ideal.

sol'n: a) We can use the idea of reflected impedance to find the current,  $I_1$ , flowing in the primary and then substitute for  $I_1$  in the voltage equation for the secondary. At least, that is what we could do in general. Here,  $I_1 = I_s$ , so we can move directly to the voltage equation for the secondary:

$$V_2 = I_1 j\omega M - I_2 (j\omega L_2 + R_2) = I_2 z_L$$

or

$$I_s j\omega M = I_2 (j\omega L_2 + R + z_L)$$

or

$$I_2 = \frac{I_s j\omega M}{R_2 + j\omega L_2 + z_L}$$

or

$$I_2 = \frac{2 \angle 45^\circ \cdot j 15 \Omega \text{ A}}{30 \Omega + j 40 \Omega - j 10 \Omega}$$

or

$$I_2 = 2 \angle 45^\circ \frac{j 15}{30 + j 30} \text{ A}$$

or

$$I_2 = 2 \angle 45^\circ \cdot \frac{15 \angle 90^\circ \text{ A}}{30\sqrt{2} \angle 45^\circ}$$

or

$$I_2 = \frac{1}{\sqrt{2}} \angle 90^\circ \text{ A} \quad \text{polar form}$$

$$I_2 = \frac{1}{2} + j \frac{1}{2} \text{ A} \quad \text{rectangular form}$$

b) We use the ideal transformer equations:

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

And we use Kirchoff's laws or other circuit-solving techniques. Here, node-voltage is used.

$$\text{node } V: -I_s + \frac{V}{j1k\Omega} + I_1 = 0 \text{ A} \quad (1)$$

$$\text{node } -V_2: -I_1 - \frac{V_2}{-j20\Omega} + I_2 = 0 \text{ A} \quad (2)$$

We need one more equation, in addition to the transformer equations. We turn to Kirchhoff's laws and find that we are able to write another equation for  $V$ .

$$V = -V_2 + V_1 \quad (\text{K-loop}) \quad (3)$$

Now we start eliminating variables using the transformer equations first.

$$V_1 = V_2 \frac{N_1}{N_2} \quad \text{and} \quad I_2 = I_1 \frac{N_1}{N_2}$$

Equation (3) becomes

$$V = -V_2 + V_2 \frac{N_1}{N_2} = V_2 \left( \frac{N_1}{N_2} - 1 \right)$$

or

$$V_2 = \frac{V}{\frac{N_1}{N_2} - 1}$$

Equation (2) becomes

$$-I_1 - \frac{V}{\left( \frac{N_1}{N_2} - 1 \right) (-j20 \Omega)} + I_1 \left( \frac{N_1}{N_2} \right) = 0 \text{ A}$$

or

$$I_1 \left( \frac{N_1}{N_2} - 1 \right) = \frac{V}{\left( \frac{N_1}{N_2} - 1 \right) (-j20 \Omega)}$$

or

$$I_1 = \frac{V}{\left( \frac{N_1}{N_2} - 1 \right)^2 (-j20 \Omega)}$$

Equation (1) becomes

$$-I_s + \frac{V}{j1k\Omega} + \frac{V}{\left(\frac{N_1}{N_2} - 1\right)^2 (-j20\Omega)} = 0A$$

or

$$V \left( \frac{1}{j1k\Omega} + \frac{1}{\left(\frac{N_1}{N_2} - 1\right)^2 (-j20\Omega)} \right) = I_s$$

or

$$V = \frac{I_s}{\frac{1}{j1k\Omega} + \frac{1}{\left(\frac{N_1}{N_2} - 1\right)^2 (-j20\Omega)}}$$

or

$$V = \frac{9 \angle 0^\circ A}{\frac{-j}{1k\Omega} + \frac{j}{5^2 (+20)\Omega}}$$

or

$$= \frac{9 A}{\frac{-j}{1k\Omega} + \frac{j2}{1k\Omega}}$$

or

$$= 9 A \cdot \frac{1k\Omega}{j}$$

or

$$V = -j9kV = 9kV \angle -90^\circ$$

Note: We could have solved this more quickly by observing earlier that we really have the following eqn.

$$V = I_s \cdot j1k\Omega \parallel \left[ \left( \frac{N_1}{N_2} - 1 \right)^2 (-j20\Omega) \right]$$

or

$$V = I_s \cdot j1k\Omega \parallel -j500\Omega = I_s \cdot j500 \cdot \frac{-2}{1} \Omega$$

or

$$V = I_s \cdot -j1k\Omega = -j9kV$$