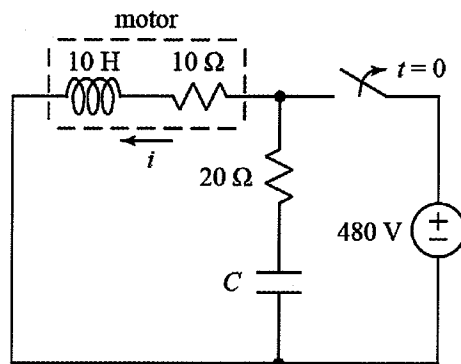


Ex:



After being closed for a long time, the switch opens at  $t = 0$ .

The above circuit represents a simplified circuit model of a motor and its power supply. The switch opens at time  $t = 0$  to turn off the motor, and resistor  $R_2$  and  $C$  provide a discharge path for current in the motor.

- Find the smallest **standard value** of  $C$  that makes the circuit over-damped after the switch is opened at  $t = 0$ . For standard values, assume the value of  $C$  is of form  $1 \cdot 10^n$  F or  $2 \cdot 10^n$  F or  $5 \cdot 10^n$  F where  $n$  is an integer.
- Using the  $C$  value from (a), find a numerical expression for the motor current,  $i(t)$ , for  $t > 0$ .

so(h: a) After  $t=0$ , we have a series RLC circuit.

$$\text{Characteristic roots are } s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L} \quad \text{and} \quad \omega_0^2 = \frac{1}{LC}$$

For over-damped roots we need  $\alpha^2 > \omega_0^2$ .

$$\alpha^2 = \left(\frac{R}{2L}\right)^2 = \left(\frac{30 \text{ r/s}}{2(10)}\right)^2 = \left(\frac{3}{2}\right)^2 (\text{r/s})^2 = 2.25 \text{ r/s}^2$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{10C}, \quad \text{or} \quad C = \frac{1}{10\omega_0^2}$$

$$\text{To achieve } \alpha^2 > \omega_0^2 \text{ we need } C \geq \frac{1}{10(2.25)} \text{ F.}$$

$$C \geq \frac{1}{10(2.25)} F = \frac{1}{22.5} F = 44.4 \text{ mF}$$


The smallest  $C \geq 44.4 \text{ mF}$  with a standard value is  $C = 50 \text{ mF}$ .

b) Using  $C = 50 \text{ mF}$ , we re-calculate characteristic roots.

$$\begin{aligned} s_{1,2} &= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -1.5 \pm \sqrt{2.25 - \frac{1}{10 \cdot 50 \text{m}}} \\ &= -1.5 \pm \sqrt{2.25 - 2} \\ &= -1.5 \pm \sqrt{0.25} \\ &= -1.5 \pm 0.5 \end{aligned}$$

$$s_{1,2} = -1 \text{ and } -2$$

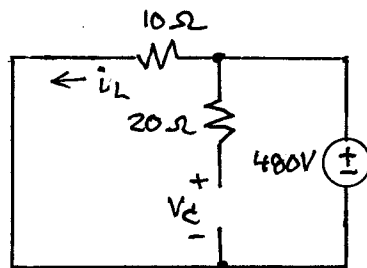We find initial conditions at  $t=0^-$ .  
Switch closed.  $L = \text{wire}$ ,  $C = \text{open}$



$$i_L = \frac{480\text{V}}{10\Omega} = 48\text{A}$$

$$V_C = 480\text{V} \text{ since } 20\Omega \text{ R has no current}$$

The form for the over-damped solution is

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + A_3$$


We will have  $A_3 = 0 \text{ A}$  since the circuit has no power supply on the left after  $t=0$ .

Now we find  $A_1$  and  $A_2$ .

$$i(0^+) = A_1 + A_2$$

$$\left. \frac{di}{dt} \right|_{t=0^+} = A_1 s_1 + A_2 s_2 = -A_1 - 2A_2$$

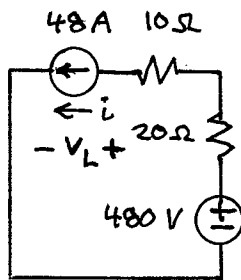our circuit at  $t=0^+$ :  $L = i_L$  source,  $C = v_C$  source



$$i(0^+) = 48 \text{ A}$$

$$\left. \frac{di}{dt} \right|_{t=0^+} = \frac{v_L(0^+)}{L}$$

$$v_L = 480 \text{ V} - 48 \text{ A} (10 \Omega + 20 \Omega) = -960 \text{ V}$$

$$\left. \frac{di}{dt} \right|_{t=0^+} = \frac{-960 \text{ V}}{10 \text{ H}} = -96 \text{ A/s}$$

Matching the circuit values to the symbolic solution, we have the following:

$$\begin{aligned} A_1 + A_2 &= 48 \text{ A} \\ -A_1 - 2A_2 &= -96 \text{ A/s} \end{aligned}$$

If we add the equations, we have

$$-A_2 = -48 \text{ A} \text{ or } A_2 = 48 \text{ A}$$

From the first eq'n, we see that we must have  $A_1 = 0 \text{ A}$

$$i(t > 0) = 48 e^{-2t} \text{ A}$$