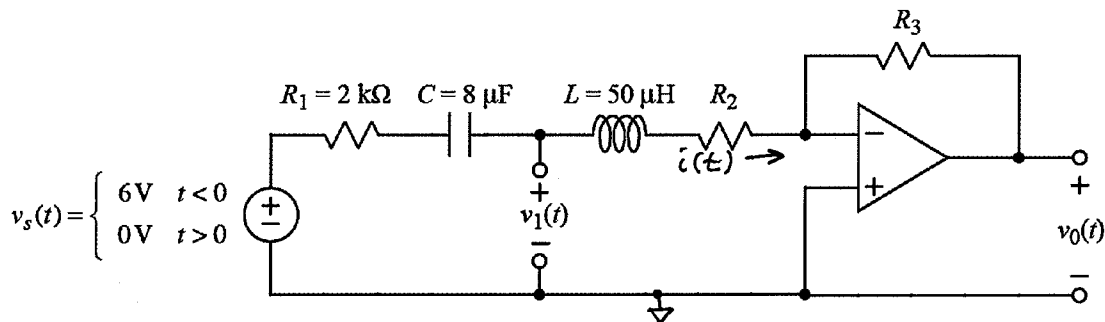


Ex:



The voltage source in the above circuit is off for $t > 0$.

- Find a symbolic expression for the Laplace-transformed output, $V_o(s)$, in terms of not more than R_1, R_2, R_3, L, C , and values of sources or constants.
- Choose a numerical value for R_2 to make


$$v_1(t) = v_m e^{-\alpha t} \cos(\beta t)$$

where v_m, α , and β are real-valued constants.

Sol'n: a) No current flows into the op-amp inputs. Thus, current flowing toward the $-$ input from the left will flow through R_3 (and into the op-amp then into the $+$ or $-$ power supply connections to the op-amp [which are not shown] then through the $+$ or $-$ power supply and back to the reference on the bottom rail [which was not shown]).

Since the op-amp has negative feedback, we expect that $v_- = v_+$ at the op-amp inputs. In other words, $v_- = v_+ = 0V$, and we have a virtual ground (or reference) at the $-$ input of the op-amp.

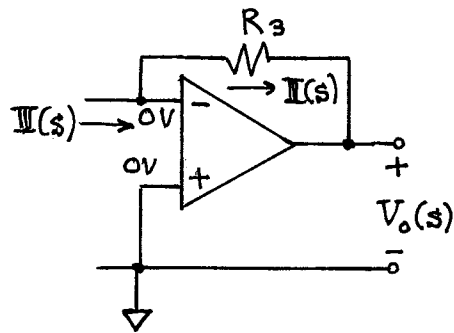We can find $V_o(s)$ from current, $I(s)$, flowing toward the $-$ input of the op-amp.




We have $V_o(s) = -I(s) R_3$.


To find $I(s)$, we may treat the - input as reference.

First, however, we find initial conditions for the L and C.

$t=0^-$: $v_s(t) = 6V$, C=open, L=wire

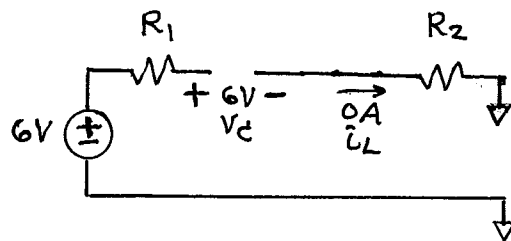

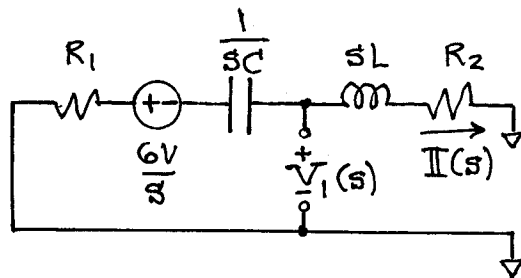We move to $t>0$ and include initial conditions on C. $V_s(t) = 0V = \text{wire}$ for $t>0$.



We have
$$I(s) = -\frac{6V}{s} \frac{1}{sL + R_1 + R_2 + \frac{1}{sC}}$$

$$\text{or } I(s) = \frac{-6V/L}{s^2 + \frac{R_1+R_2}{L}s + \frac{1}{LC}}$$

$$\text{So } V_o(s) = -I(s)R_3$$

$$V_o(s) = \frac{6V R_3/L}{s^2 + \frac{R_1+R_2}{L}s + \frac{1}{LC}}$$

b) $V_1(s)$ is the same as the V -drop across L and R_2 .

$$V_1(s) = I(s)(sL + R_2)$$

or

$$V_1(s) = \frac{-(6V/L)(sL + R_2)}{s^2 + \frac{R_1+R_2}{L}s + \frac{1}{LC}}$$

or

$$V_1(s) = -6V \frac{s + R_2/L}{s^2 + \frac{R_1+R_2}{L}s + \frac{1}{LC}}$$

From the form of $v_1(t)$ given in the problem, we have another form for $V_1(s)$:

$$V_1(s) = \mathcal{L} \{ v_m e^{-\alpha t} \cos(\beta t) \}$$

$$V_1(s) = v_m \frac{s + \alpha}{(s + \alpha)^2 + \beta^2}$$

$$V_1(s) = v_m \frac{s + \alpha}{s^2 + 2\alpha s + \alpha^2 + \beta^2}$$

Matching coefficients of the powers of s in the two forms of $V_1(s)$, we have the following equations:

$$R_2/L = \alpha, \quad \frac{R_1+R_2}{L} = 2\alpha, \quad \frac{1}{LC} = \alpha^2 + \beta^2$$

We have $\frac{R_2}{L} = \alpha = \frac{R_1 + R_2}{2L}$.

The solution is $R_2 = R_1 = 2k\Omega$.

$$R_2 = 2k\Omega$$

Now we consider whether this solution actually works. That is, we determine whether our solution is actually under-damped.

$$\alpha = \frac{R_2}{L} = \frac{2k\Omega}{50\mu H} = 40 \text{ M r/s}$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{50\mu H \cdot 8\mu F} = \frac{(1M)^2}{400}$$

$$\text{So } \alpha^2 - \omega_0^2 = 40^2 \text{ M}^2 - \frac{1 \text{ M}^2}{400} > 0.$$

Thus, we have an over-damped solution. Our characteristic roots will be real. We can't solve the problem!

$$\begin{aligned} s_{1,2} &= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \\ &= -\alpha \pm \alpha \sqrt{1 - \left(\frac{\omega_0}{\alpha}\right)^2} \\ &\doteq -\alpha \pm \alpha \left(1 - \frac{1}{2} \left(\frac{\omega_0}{\alpha}\right)^2\right) \text{ since } \omega_0 \ll \alpha \\ &\doteq -\frac{1}{2} \frac{\omega_0}{\alpha} \text{ and } -2\alpha \\ &\doteq -\frac{1}{2} \frac{1M}{20} \text{ and } -2(40M) \text{ r/s} \\ &\doteq -\frac{1}{1600} \text{ and } -80M \text{ r/s} \end{aligned}$$

We have one slow decay (that is probably very small in the solution) and one fast decay that is like a time constant $L/(R_1 + R_2)$.