
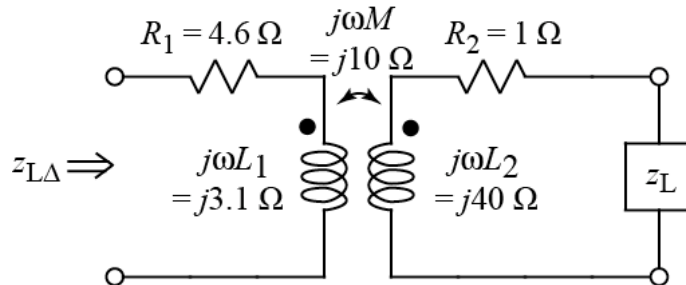


Ex:

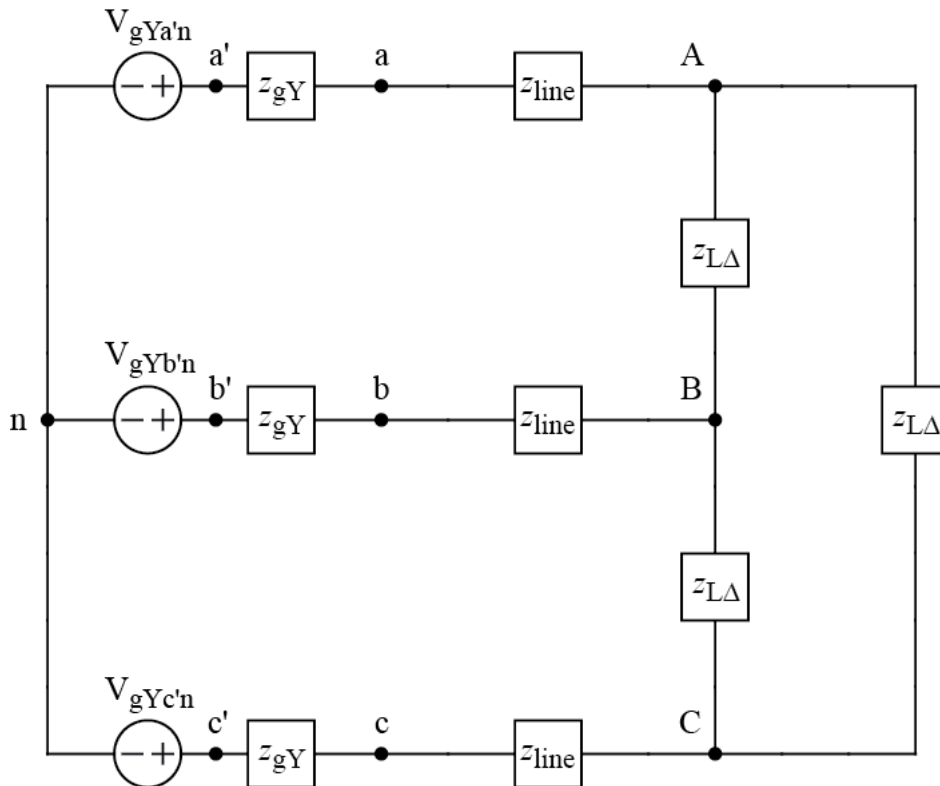

- a) Find the value of load impedance, z_L , that makes $z_{L\Delta} = 24.6 - j36.9 \Omega$. Note that $z_{L\Delta}$ is the equivalent impedance of the entire circuit.



$$V_{gYa'n} = 67 \angle 0^\circ \text{ V}$$

$$z_{gY} = 11.9 + j19.7 \Omega$$

$$V_{gYb'n} = 67 \angle -120^\circ \text{ V}$$


$$z_{line} = j6 \Omega$$

$$V_{gYc'n} = 67 \angle +120^\circ \text{ V}$$

$$z_{L\Delta} = 24.6 - j36.9 \Omega$$

- b) For the above 3-phase balanced circuit, find the numerical value of the phasor current \mathbf{I}_{CA} .
- c) For the above 3-phase balanced circuit, find the numerical value of the phasor voltage $\mathbf{V}_{b'a'}$.

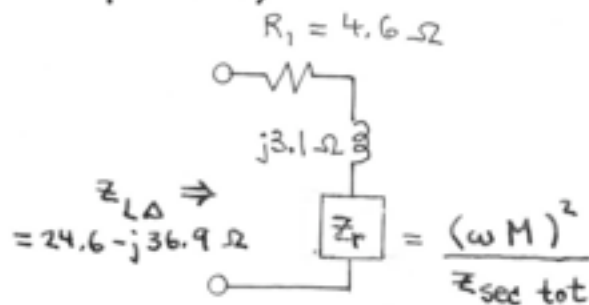- b) We replace the secondary with reflected impedance z_r in the primary.



$$4.6 + j3.1 + \left(z_r = \frac{(10 \Omega)^2}{j40 + 1 \Omega + z_L} \right) = 24.6 - j36.9 \Omega$$

$$\frac{-4.6 - j3.1 \Omega}{20 - j40 \Omega}$$

Inverting both sides, we have the following:

$$\frac{j40 + 1 \Omega + z_L}{100 \Omega^2} = \frac{1}{20 - j40 \Omega}$$

$$z_L = \frac{100 \Omega^2}{20 - j40 \Omega} - (1 + j40) \Omega$$

$$= 1 + 2i - 1 - j40 \Omega$$

$$z_L = -j38 \Omega$$


sol'n: a) We use a single-phase model to find V_{AN} .
From V_{AN} we can find V_{AB} , then V_{CA} , and then I_{CA} .

We only need to convert $z_{L\Delta}$ to z_{LY} :

$$z_{LY} = \frac{z_{L\Delta}}{3} = \frac{24.6 - j36.9 \Omega}{3}$$

$$z_{LY} = 8.2 - j12.3 \Omega$$


Single-phase model:

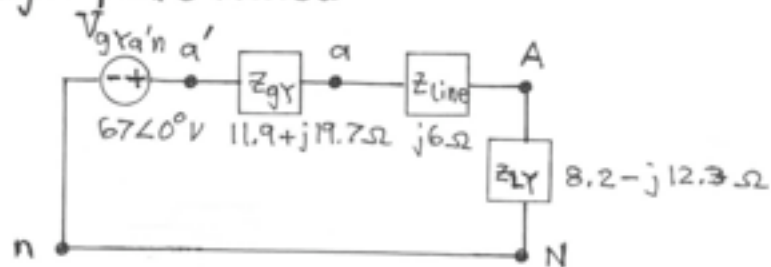

$$\begin{aligned}
 V_{AN} &= V_{gYa'n} \cdot \frac{Z_{LY}}{Z_{gY} + Z_{line} + Z_{LY}} \\
 &= 67\angle 0^\circ V \frac{8.2 - j12.3 \Omega}{11.9 + j19.7 + j6 + 8.2 - j12.3 \Omega} \\
 &= 67\angle 0^\circ V \frac{8.2 - j12.3 \Omega}{20.1 + j13.4 \Omega} \\
 &\doteq 67\angle 0^\circ V \cdot 0.612\angle -90^\circ
 \end{aligned}$$

$$V_{AN} = 41\angle -90^\circ V$$

We use a phasor diagram to find V_{AB} .

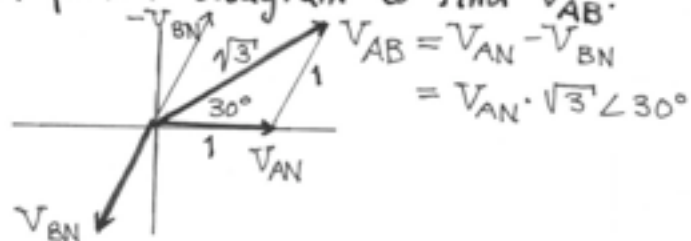

$$V_{AB} = 41\angle -90^\circ V \cdot \sqrt{3}\angle 30^\circ$$

$$V_{AB} \doteq 71\angle -60^\circ V$$

We shift $+120^\circ$ to get V_{cA} :

$$V_{CA} = V_{AB} \cdot 1 \angle 120^\circ$$

$$V_{CA} \doteq 71 \angle 60^\circ \text{ V}$$

Using Z_{Δ} and V_{CA} , we find I_{CA} :

$$I_{CA} = \frac{V_{CA}}{Z_{\Delta}} \doteq \frac{71 \angle 60^\circ \text{ V}}{24.6 - j36.9 \Omega}$$

$$\doteq \frac{71 \angle 60^\circ \text{ V}}{44.35 \angle -56.3^\circ \Omega}$$

$$I_{CA} \doteq 1.6 \angle 116.3^\circ \text{ A}$$

c) Since $V_{AB} = V_{AN} \sqrt{3} \angle 30^\circ$, we have the same relationship for the generator side:

$$V_{a'b'} = V_{a'n} \sqrt{3} \angle 30^\circ$$

or

$$V_{a'b'} = 67 \angle 0^\circ \cdot \sqrt{3} \angle 30^\circ \doteq 116 \angle 30^\circ$$

Reversing the indices to b'a' means changing the sign, which is equivalent to adding or subtracting 180° .

$$V_{b'a'} \doteq 116 \angle 210^\circ = 116 \angle -150^\circ$$