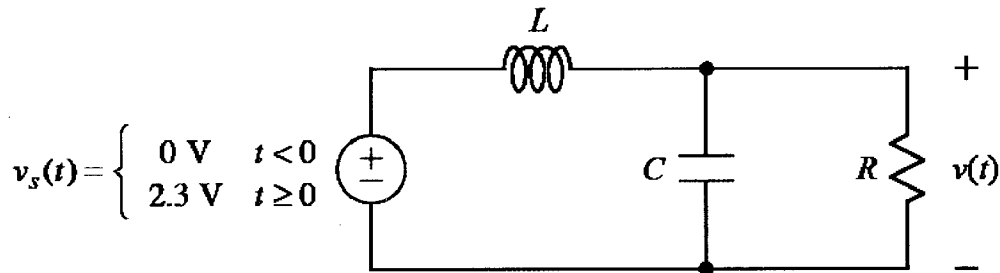


Ex:



The above circuit models a digital logic gate driving another digital logic gate (modeled as R and C) via a long path of metal on-chip (modeled as L).

$$L = 10 \text{ pH} \quad C = 0.4 \text{ pF} \quad R = 1 \text{ G}\Omega$$

Find the shape of $v(t)$ versus time. That is, make a rough sketch of $v(t)$ based on the characteristic roots and final value of $v(t)$.

sol'n: We have a parallel RLC, which may be seen by turning off the v -src, which becomes a wire.

$$\text{Thus, } \alpha = \frac{1}{2RC} = \frac{1}{2(1\text{G})(0.4\text{p})} = \frac{1}{0.8\text{m}} \text{ /s}$$

$$\alpha = 1.25 \text{ k/s}$$

Characteristic roots:

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\text{where } \omega_0^2 = \frac{1}{LC} = \frac{1}{10\text{p}(0.4\text{p})} \text{ r}^2/\text{s}^2$$

$$\text{or } \omega_0^2 = \left(\frac{1}{2\text{p}}\right)^2 \text{ r}^2/\text{s}^2$$

$$\text{or } \omega_0^2 = (500\text{M})^2$$

$$\text{Thus, } s_{1,2} = -1.25 \text{ k} \pm \sqrt{(1.25\text{k})^2 - (500\text{M})^2}$$

Since $\omega_0 \gg \alpha$, the circuit is very underdamped.

Our damping frequency is

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \approx \sqrt{\omega_0^2} \text{ since } \omega_0 \gg \alpha$$

or

$$\omega_d \approx \omega_0 = (500M)^2$$

So our roots are $s_{1,2} \approx -1.25 \pm j500M$ r/s.

Our roots are complex, so the sol'n oscillates at frequency $\omega_d = 500M$.

The frequency of oscillation is much higher than α , so the sol'n will oscillate many times before they decay away as $e^{-\alpha t}$. The sol'n form shows the oscillation and decay:


$$v(t) = A_1 e^{-\alpha t} \cos(\omega_d t) + A_2 e^{-\alpha t} \sin(\omega_d t) + A_3$$

Finally, we find A_3 , which is the final value of $v(t)$.

$$A_3 = v(t \rightarrow \infty)$$


As $t \rightarrow \infty$, the circuit stabilizes, and the L acts like a wire and C acts like an open.

$t \rightarrow \infty$:

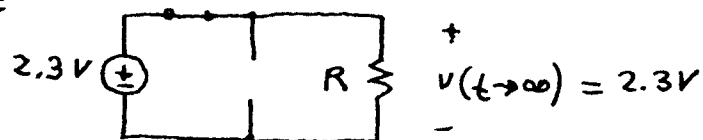

The R must drop the 2.3V.

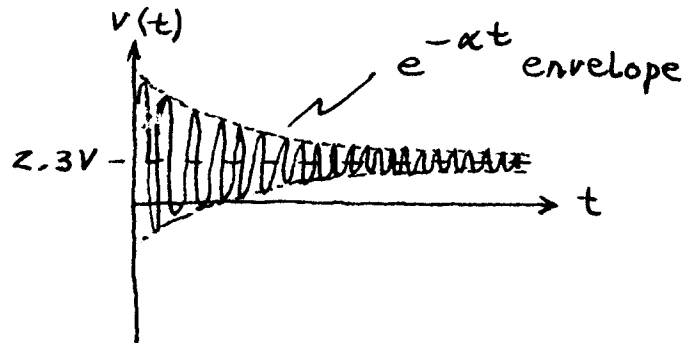Our sketch of the sol'n captures the qualitative nature of the sol'n, but it will not capture the initial value of $v(t)$, and it will not capture the size of the oscillations.



Note: the oscillations are actually much more rapid than shown.