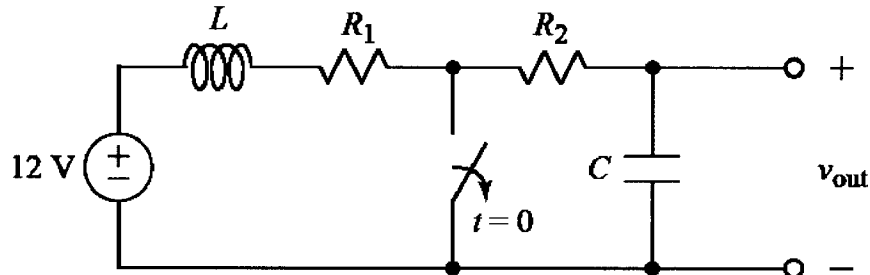


Ex:



A 12 V power supply drives a long wire, (modeled as  $L$  and  $R_1$ ), followed by a short wire,  $R_2$ , and a smoothing capacitor,  $C$ . There is a safety switch, located before the smoothing capacitor, to turn off the output at the remote end. The switch is closed for a long time before opening at  $t = 0$ .

$$L = 2 \mu\text{H} \quad R_1 = 2.0 \Omega \quad R_2 = 0.1 \Omega \quad C = 200 \mu\text{F}$$

- Find the characteristic roots,  $s_1$  and  $s_2$ , for the above circuit.
- Find  $v_{out}$  for  $t > 0$ .

sol'n: For  $t > 0$ , the switch is open and the two  $R$ 's may be combined as  $R = R_1 + R_2$ .

To determine whether we have a series or parallel RLC, we turn off any sources, (a  $V$ -src becomes a wire, and an  $i$ -src becomes an open). Here, we turn off the 12V source and find that we have a series RLC.

$$\begin{aligned} \text{Thus, } \alpha &= \frac{R}{2L} = \frac{R_1 + R_2}{2L} = \frac{2\Omega + 0.1\Omega}{2(2\mu\text{H})} \\ \alpha &= \frac{2.1}{4\mu} / \text{s} = 525 \text{ k/s} \end{aligned}$$

$$\begin{aligned} \text{As always, } \omega_0^2 &= \frac{1}{LC} = \frac{1}{2\mu \cdot 200\mu} / \text{s}^2 = \left(\frac{1}{20\mu}\right)^2 \\ \omega_0^2 &= (50\text{k})^2 / \text{s}^2 \end{aligned}$$

Our characteristic roots are

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$s_{1,2} = -525k \pm \sqrt{(525k)^2 - (50k)^2} / s$$

The circuit is overdamped and has one root close to zero (because  $50k \ll 525k$ ).

While we could just use a calculator, it is instructive to use an approximation method that will work even when  $\alpha^2 \gg \omega_0^2$ .

We first write the  $\sqrt{\quad}$  in the form  $\sqrt{1-x}$  where  $0 < x \ll 1$ .

$$s_{1,2} = -525k \pm 525k \sqrt{1 - \left(\frac{50}{525}\right)^2}$$

The next step is to use a truncated Taylor series to write an approximation.

$$f(x) = f(0) + \left. \frac{df(x)}{dx} \right|_{x=0} \cdot x + \dots$$

for  $f(x) = \sqrt{1-x}$

$$\begin{aligned} \text{We have } \left. \frac{df(x)}{dx} \right|_{x=0} &= \left. \frac{1}{2} (1-x)^{-1/2} (-1) \right|_{x=0} \\ &= -\frac{1}{2} \end{aligned}$$

Since  $f(0) = \sqrt{1-0} = 1$  we have

$$\sqrt{1-x} = 1 - \frac{1}{2}x + \dots$$

We might be tempted to use  $\sqrt{1-x} \approx 1$ , but this approximation would be too coarse. It would lead us to conclude that one characteristic root is zero, which would imply a sol'n that never decays. Furthermore, we would be unable to match initial conditions for both  $L$  and  $C$ , owing to having too few terms in our sol'n. ( $A_2 e^{0t} = A_2$  could be absorbed by the  $A_3$  term, see below)

So we use  $\sqrt{1-x} \approx 1 - \frac{1}{2}x$ , dropping the smaller, higher order terms in  $x^2, x^3$ , etc. These terms will be very small since  $x$  is small.

$$s_{1,2} \approx -525k \pm 525k \left(1 - \frac{1}{2} \left(\frac{50}{525}\right)^2\right)$$

$$s_1 \approx -525k + 525k(0.995) \quad 0.004535$$

$$\text{or } s_1 \approx -525k(1 - 0.995) = -525k(0.0045)$$

$$\text{or } s_1 \approx -2.4k \text{ r/s}$$

$$\text{and } s_2 \approx -525k - 525k(0.995)$$

$$s_2 \approx -525k(2) = -1.05M \text{ r/s}$$

Note: We may use the approximation  $\sqrt{1-x} \approx 1$  for  $s_2$  because our error will be small percentage-wise relative to the size of  $s_2$ .

Summary:  $s_1 \approx -2.4k \text{ r/s}$   $s_2 \approx -1.05M \text{ r/s}$

We have two real and distinct roots: under-damped.

b) For the underdamped case our sol'n is

$$v_{out}(t > 0) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + A_3$$


Because  $e^{s_1 t}$  and  $e^{s_2 t}$  are decaying exponentials, as  $t \rightarrow \infty$  we have  $v_{out} \rightarrow A_3$ .

$$\text{So } A_3 = v_{out}(t \rightarrow \infty)$$

In our circuit model for  $t \rightarrow \infty$ , we assume  $i$ 's and  $v$ 's stabilize. Since  $i$ 's and  $v$ 's are not changing, we have

$$v_L = L \frac{di}{dt} = L \cdot 0 = 0 \Rightarrow L \text{ acts like a wire (carries } i \text{ with no } v\text{-drop)}$$
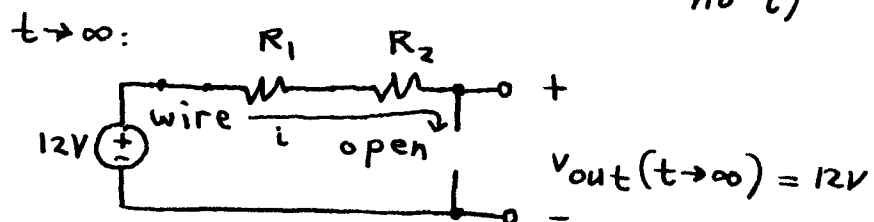
$$i_C = C \frac{dv}{dt} = C \cdot 0 = 0 \Rightarrow C \text{ acts like an open (} v\text{-drop but no } i\text{'}$$



Because of the open  $C$ , the current flowing around the circuit is zero. This means the voltage drops across  $R_1$  and  $R_2$  are zero by Ohm's law. Consequently, we have a 12V drop across  $C$ , meaning

$$A_3 = v_{out}(t \rightarrow \infty) = 12V$$

To find  $A_1$  and  $A_2$ , we use initial conditions.


$$\begin{aligned}
 v_{out}(t=0^+) &= A_1 e^{s_1 t} + A_2 e^{s_2 t} + A_3 \Big|_{t=0^+} \\
 &= A_1 e^{0^+} + A_2 e^{0^+} + 12V \\
 &= A_1 + A_2 + 12V, \text{ since } e^{0^+} = 1
 \end{aligned}$$

From our circuit, we determine the value of  $v_{out}(0^+)$ . To do so, we need to know what the L and C are doing. Fortunately,  $i_L$  and  $v_C$  are energy variables:  $w_L = \frac{1}{2} L i_L^2$  and  $w_C = \frac{1}{2} C v_C^2$ .

Energy cannot change instantly, so

$$i_L(0^+) = i_L(0^-) \text{ and } v_C(0^+) = v_C(0^-).$$

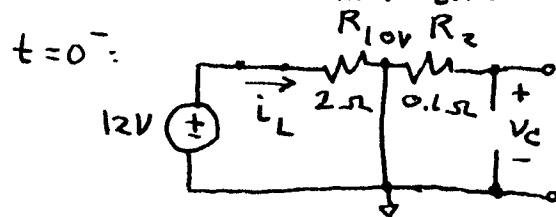
At  $t=0^-$ , we may assume the circuit has stabilized, and we may treat the L as a wire and the C as an open.




Note: We only find  $i_L$  and  $v_C$  at  $t=0^-$  since any other  $i$  or  $v$  may change when the switch moves.

The switch in the middle allows us to separate the circuit into two sides, as it creates two circuits in parallel across a  $v$ -src. In this case, the  $v$ -src is 0V for the short circuit formed by the switch.

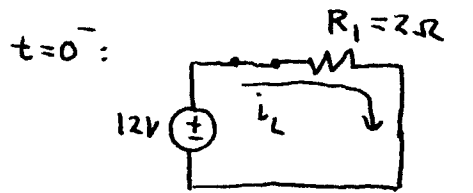We can also say we have 0V between  $R_1$  &  $R_2$  as our node voltage.




$$i_L = \frac{12V}{2\Omega} = 6A$$

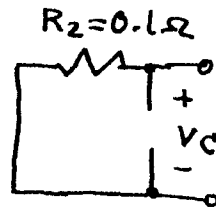

$$v_C = 0^+$$

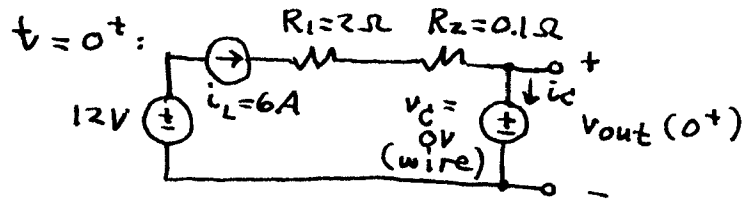At  $t=0^+$ , we can model the L and C as sources, since  $i_L(0^+) = i_L(0^-)$ ,  $v_C(0^+) = v_C(0^-)$ , and any component whose  $i$  or  $v$  is known may be replaced by a source with that  $i$  or  $v$  value.



Since  $v_{out} = v_C$ , we have  $v_{out}(0^+) = 0V$ .

$$\text{Thus, } A_1 + A_2 + 12V = 0V$$

We need one more eq'n in order to have two eq'ns in two unknowns that we can solve for  $A_1$  and  $A_2$ .

What we need is a sol'n for  $v_{out}(t)$  that matches the initial conditions for L and C. Our  $v_{out}(0^+)$  matches the initial conditions for C, but we need it to also give the correct  $i_L$ .

We observe that  $i_L = i_C = C \frac{dv_C}{dt} = C \frac{dv_{out}}{dt}$

$$\text{so we have } \left. \frac{dv_{out}}{dt} \right|_{t=0^+} = \frac{i_C(0^+)}{C} = \frac{6A}{200\mu F} = 30kV/s$$

Our sol'n form for  $v_{out}(t)$  gives

$$\left. \frac{d}{dt} v_{out}(t) \right|_{t=0^+} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t} \Big|_{t=0^+}$$

$$= A_1 s_1 + A_2 s_2$$

So we have  $A_1 s_1 + A_2 s_2 = 30 \text{ kV/s}$ .  
and, from before,  $A_1 + A_2 + A_3 = 0V$ ,  $A_3 = 12V$ .

Solving the 2<sup>nd</sup> eq'n gives

$$A_2 = -12V - A_1$$

Substituting this into the first eq'n gives

$$A_1 s_1 + (-12V - A_1) s_2 = 30 \text{ kV/s}$$

or

$$A_1 (s_1 - s_2) = 12V s_2 + 30 \text{ kV/s}$$

We can get a more accurate answer  
by analyzing  $s_1 - s_2$ :

$$s_1 - s_2 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} - (-\alpha - \sqrt{\alpha^2 - \omega_0^2})$$

$$= 2\sqrt{\alpha^2 - \omega_0^2} \approx 2(525 \text{ k})(0.995) \text{ r/s}$$

$$s_1 - s_2 \approx 1.05 \text{ M}(0.995) \text{ r/s} \quad \text{small } (< 1\% \text{ err if ignored})$$

So  $A_1 \approx \frac{12V(-1.05 \text{ M r/s}) + 30 \text{ k r/s}}{(1.05 \text{ M})(0.995) \text{ r/s}}$

$$A_1 \approx -12.06V$$

From earlier,  $A_1 + A_2 + 12V = 0V$  so  $A_2 = 0.06V$ .

$$\text{Thus, } v_{out}(t > 0) = -12.06V e^{-2.4 \text{ k/s} t} + 0.06 e^{-1.05 \text{ M/s} t} + 12V$$

Alternative view:

In the above discussion, the sol'n was matched to initial conditions for the L and C explicitly. It turns out the key to finding coefficients  $A_1$  and  $A_2$  is always to determine the value of  $dv/dt$  (or  $di/dt$ ) from the circuit and match it to the symbolic sol'n.

The problem is that one must find the derivative of the sol'n before knowing the sol'n! This seeming contradiction is resolved by observing that the component eq'ns for L and C relate derivatives to non-derivatives.

$$v_L = L \frac{di_L}{dt} \quad i_C = C \frac{dv_C}{dt}$$

Using these eq'ns is the way we find the derivative of our sol'n. If we are solving for  $i$  or  $v_C$ , our task is simple: we need only find  $v_L$  or  $i_C$ :


$$\left. \frac{di_L}{dt} \right|_{0^+} = \frac{v_L(0^+)}{L}, \quad \left. \frac{dv_C}{dt} \right|_{0^+} = \frac{i_C}{C}$$

If, however, we have an arbitrary  $i$  or  $v$ , the idea is to write that  $i$  or  $v$  in terms of  $i_L$  and  $v_C$ , (plus component or source values). Then, we can differentiate to get  $di/dt$  or  $dv/dt$  in terms of  $di_L/dt$  and or  $dv_C/dt$ .



There are some subtleties to be observed here: 1) the expression for  $i$  or  $v$  in terms of  $i_L$  and  $v_C$  must be valid over  $t > 0$ , not just at  $t = 0^+$ ; and 2) the expression for  $i$  or  $v$  must be derivative-free, otherwise it will contain 2<sup>nd</sup> derivatives when differentiated. Condition (1) is necessary in order for the derivative to be valid, and condition (2) is necessary to avoid creating terms which we are unable to evaluate.

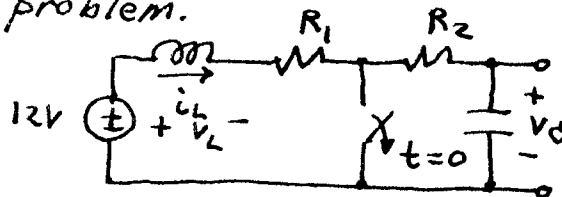ex: Suppose we were asked to find  $v_L(t)$  for  $t > 0$  in this problem.



We want to write  $v_L$  in terms of  $i_L$  and/or  $v_C$ . We turn to Kirchhoff's and Ohm's Laws.


Using a  $v$ -loop and the fact that  $i_L$  flows thru  $R_1$  and  $R_2$ , we have

$$\text{so } v_L = 12V - i_L(R_1 + R_2) - v_C$$

$$\frac{dv_L}{dt} \Big|_{0^+} = \frac{di_L}{dt} \Big|_{0^+} (R_1 + R_2) - \frac{dv_C}{dt} \Big|_{0^+}$$


$$\text{or } \frac{dv_L}{dt} \Big|_{0^+} = \frac{v_L(0^+)}{L} (R_1 + R_2) - \frac{i_C(0^+)}{C}$$

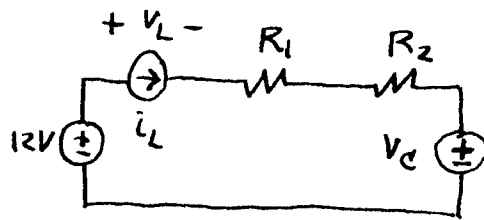A visual aid to finding the eqn is to replace the  $L$  and  $C$  with sources:



Using superposition, we find  $v_L$ :


case I: 12V,  $i_L$  off,  $v_C$  off

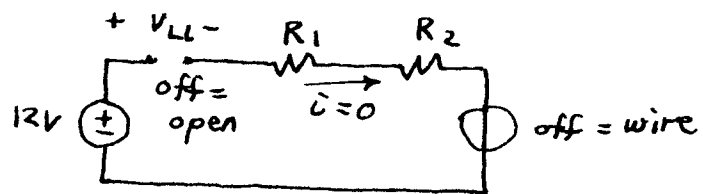

Since no current flows, there is no drop across the  $R$ 's, and all the voltage is dropped across the gap at  $v_{L1}$ .

$$v_{L1} = 12V$$

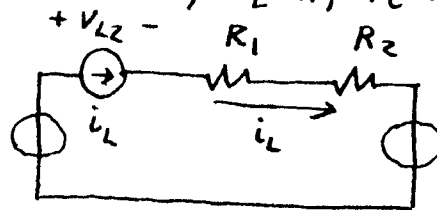
case II: 12V off,  $i_L$  on,  $v_C$  off



$$-v_{L2} - i_L R_1 - i_L R_2 = 0V$$

$$v_{L2} = -i_L (R_1 + R_2)$$

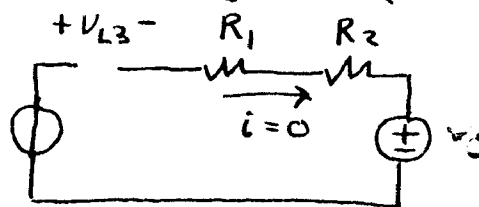case III: 12V off,  $i_L$  off,  $v_C$  on



Since no current flows, there is no  $v$ -drop across the  $R$ 's and  $v_L$  must be  $-v_C$  so that the  $v$ -drops around the loop sum to zero.

$$v_{L3} = -v_C$$

Combining results, we have

$$v_L = v_{L1} + v_{L2} + v_{L3} = i_L (R_1 + R_2) - v_C$$

This result is the eq'n stated earlier, as promised. We then take  $d/dt$  of this entire eq'n, as explained earlier.