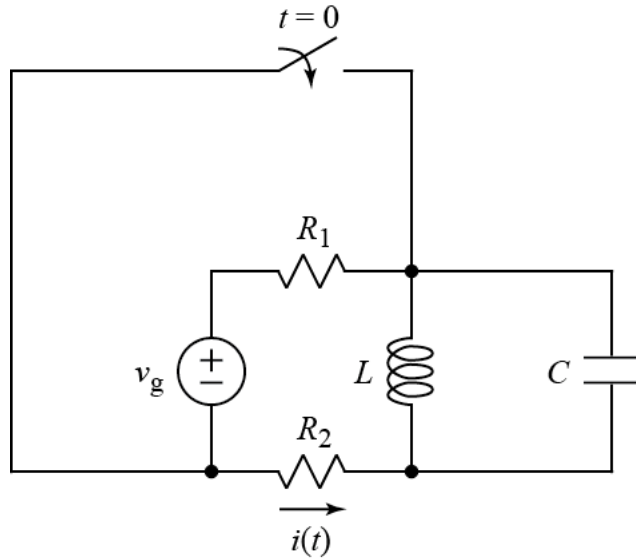


Ex:



After being open for a long time, the switch closes at  $t = 0$ .

- a) Give expressions for the following in terms of no more than  $v_g$ ,  $R_1$ ,  $R_2$ ,  $L$ , and  $C$ :


$$i(t = 0^+) \quad \text{and} \quad \left. \frac{di(t)}{dt} \right|_{t=0^+}$$

- b) Find the numerical value of  $R_2$  given the following information:

$$R_1 = 150 \, \Omega \quad L = 40 \, \text{mH} \quad C = 3.2 \, \mu\text{F}$$

$$\alpha = 1250 \, \text{r/s} \quad \omega_d = 2500 \, \text{r/s}$$

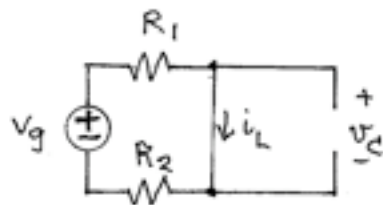SOL'N: a) We start with the circuit at  $t = 0^-$  to determine the state of the  $L$  and  $C$ . At  $t = 0^-$ ,  $L = \text{wire}$ ,  $C = \text{open}$




$$v_C(0^-) = 0V \text{ (shorted by } L)$$

$$i_L(0^-) = \frac{v_g}{R_1 + R_2}$$

At  $t=0^+$ , the switch is closed and  $i_L(0^+) = i_L(0^-)$  and  $v_C(0^+) = v_C(0^-)$ .

$V_g$  and  $R_1$  are shorted out by the switch. This short divides the circuit into two halves that we may solve independently. The one we are interested in consists of  $R_2$ ,  $L$ , and  $C$ .

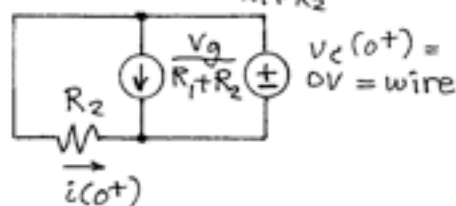$t=0^+$ :  $i_L(0^+) = \frac{V_g}{R_1+R_2}$  = current source



Because the  $C$  acts like a wire, all the current from the  $L$  will flow thru the  $C$ . So the current in  $R_2$  is zero. (Another way to see this is to observe that  $R_2$  has  $0V = v_C$  across it, and by Ohm's law  $i(0^+) = 0V/R_2 = 0A$ .)

So  $i(0^+) = 0A$ .

For  $\frac{di}{dt}\bigg|_{t=0^+}$ , we first write  $i(t)$

in terms of  $i_L$  and/or  $v_C$ .

We observe that  $v_C$  is across  $R_2$ :

$$i(t) = v_C / R_2$$

Now we differentiate the entire eq'n:

$$\frac{di(t)}{dt} = \frac{1}{R_2} \frac{dv_C}{dt} = \frac{1}{R_2} \frac{i_C}{C}$$

(We have used  $i_C = C \frac{dv_C}{dt}$  rearranged.)

We evaluate  $i_C$  at  $t=0^+$ . We noted earlier that all the current from the L goes thru C. If we follow the direction of the current arrow for the L down, over, and up thru the C, we see that


$$i_C(0^+) = -i_L(0^+) = -\frac{V_g}{R_1 + R_2}$$

$$\text{Thus, } \left. \frac{di(t)}{dt} \right|_{t=0^+} = \frac{1}{R_2 C} i_C(0^+)$$

or

$$\left. \frac{di(t)}{dt} \right|_{t=0^+} = \frac{-V_g}{R_2 C (R_1 + R_2)}$$

b) We use the circuit for  $t > 0$ .

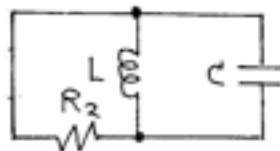

We have a parallel RLC.

$$\alpha = \frac{1}{2R_2 C}, \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}, \quad \omega_0^2 = \frac{1}{LC}$$

$$\text{Use } \alpha: R_2 = \frac{1}{2\alpha C} = \frac{1}{2(1250)3.2\mu} = 125 \Omega$$