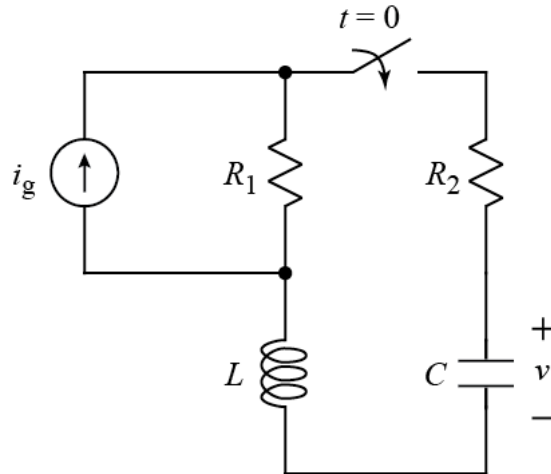


Ex:



After being open for a long time, the switch closes at $t = 0$.

$$i_g = 0.2 \text{ A} \quad R_1 = 50 \, \Omega \quad R_2 = 12.5 \, \Omega \quad L = 10 \text{ mH} \quad C = 16 \, \mu\text{F}$$

- State whether $v(t)$ is under-damped, over-damped, or critically-damped.
- Write a numerical time-domain expression for $v(t)$, $t > 0$, the voltage across C . This expression must not contain any complex numbers.

SOL'N: a) We use the circuit for $t > 0$ to find the characteristic roots. If we convert i_g and R_1 into a Thevenin equivalent, we see that R_1 and R_2 are in series. Since L and C are in series, we have a series RLC.

$$\alpha = \frac{R}{2L} = \frac{50 + 12.5 \, \Omega}{2(10 \text{ mH})} = 3.125 \text{ k/s}$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{10 \text{ mH} \cdot 16 \, \mu\text{F}} = \frac{1 \text{ Gr/s}^2}{160} = \left(\frac{10 \text{ kr/s}}{4}\right)^2$$

$$s_{1,2} = -3.125 \pm \sqrt{3.125^2 - 2.5^2} \text{ kr/s} = -5 \text{ kr/s}, -1.25 \text{ kr/s}$$


overdamped (real roots)

b) Our form of solution for the overdamped case is

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + A_3.$$

$$A_3 = v(t \rightarrow \infty)$$

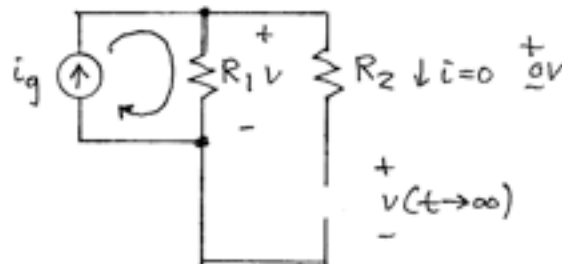For $t \rightarrow \infty$, we use $L = \text{wire}$, $C = \text{open}$



$v(t \rightarrow \infty)$ equals the voltage across

R_1 since no current flows in R_2 (so $0V$ across R_2) owing to C being an open circuit.

i_g can only flow around the upper left loop. By Ohm's law, the v -drop across R_1 is $i_g R_1$.

$$\therefore v(t \rightarrow \infty) = i_g R_1 = A_3$$

$$\text{or } A_3 = 0.2A \cdot 50\Omega = 10V$$

Now we match our solution to circuit values at $t=0^+$:

$$v(0^+) = A_1 + A_2 + A_3 \quad \left. \frac{dv}{dt} \right|_{t=0^+} = s_1 A_1 + s_2 A_2$$

We consider $t=0^-$ to determine initial values for L and C :


$t=0^-$: L =wire, C =open, switch open

Since the switch is open, no current will flow in L , so we must have $i_L(0^-) = i_L(0^+) = 0A$.

We are given $v(0^+) = 0V$.

At $t=0^+$, we treat L as i -src and C as v -src.

$t=0^+$:

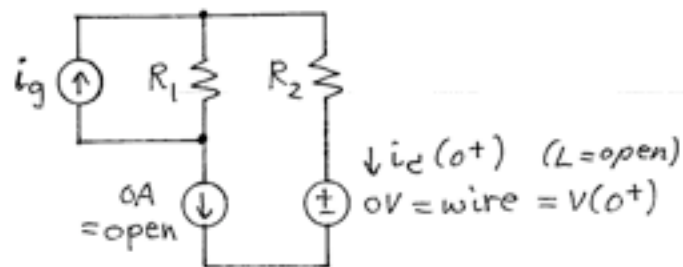

$$v(0^+) = 0V = A_1 + A_2 + A_3 = A_1 + A_2 + 10V$$

$$\left. \frac{dv}{dt} \right|_{t=0^+} = \left. \frac{i_c}{C} \right|_{t=0^+} = 0 = \underbrace{s_1}_{-5k} A_1 + \underbrace{s_2}_{-1.25k} A_2$$

From 2nd eq'n, $A_2 = -4A_1$.
Substitute into 1st eq'n:

$$A_1 - 4A_1 + 10V = 0V, \quad A_1 = \frac{10V}{3}, \quad A_2 = \frac{-40V}{3}$$

$$v(t) = \frac{10}{3} e^{-5k/s \cdot t} - \frac{40}{3} e^{-1.25k/s \cdot t} + 10V$$