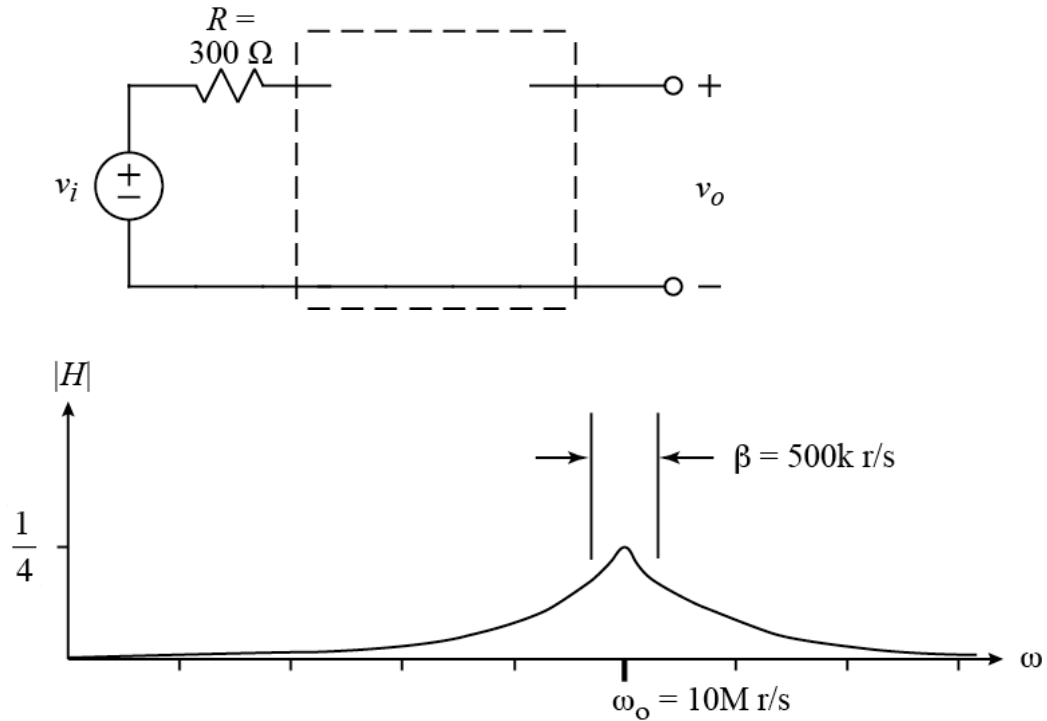


1.




Given the resistor connected as shown and using not more than one each R , L , and C in the dashed-line box, design a circuit to go in the dashed-line box that will produce the **band-pass** $|H(j\omega)|$ vs. ω shown above. That is:

$$\max_{\omega} |H(j\omega)| = \frac{1}{4} \text{ and occurs at } \omega_0 = 10 \text{ M r/s}$$

The bandwidth, β , of the filter is 500 k r/s .

$$|H(j\omega)| = 0 \text{ at } \omega = 0 \quad \text{and} \quad \lim_{\omega \rightarrow \infty} |H(j\omega)| = 0$$

2.

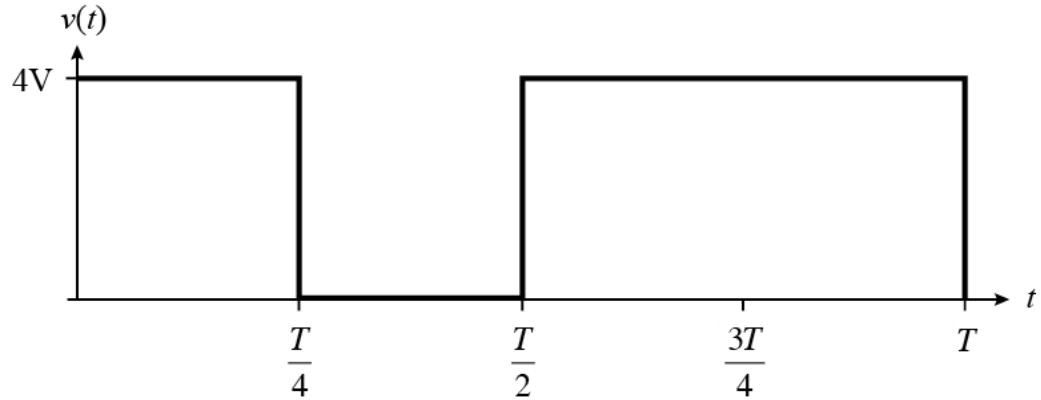

One period, T , of a function $v(t)$ is shown above. The formula for $v(t)$ is

$$v(t) = \begin{cases} 4 \text{ V} & 0 < t < T/4 \\ 0 \text{ V} & T/4 < t < T/2 \\ 4 \text{ V} & T/2 < t < T \end{cases}$$

Find the numerical value of the following coefficients of the Fourier series for $v(t)$:


a) a_v

b) a_2

3.

Find the value of b_2 and b_4 for the Fourier series in problem 2.

4.

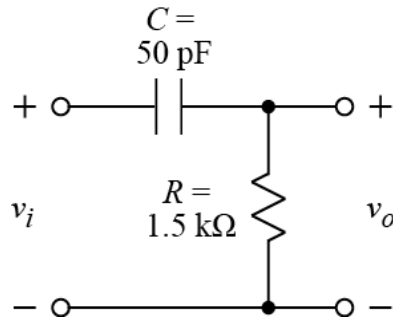

$$v_i(t) = -4 + 2 \sum_{k=1}^{\infty} \frac{1}{k^2 + 1} \sin(k\omega_0 t) \text{ V}$$

For the above circuit, determine the transfer function $H(j\omega) = V_o/V_i$.

5.

Assume the circuit in problem 4, has the following input signal:

$$v_i(t) = -4 + 2 \sum_{k=1}^{\infty} \frac{1}{k^2 + 1} \sin(k\omega_0 t) \text{ V}$$

Note: $\omega_0 = \frac{10}{3} \text{ M r/s}$ for the Fourier series.

Write the time-domain expression of the third harmonic (i.e., $k = 3$) of $v_o(t)$.