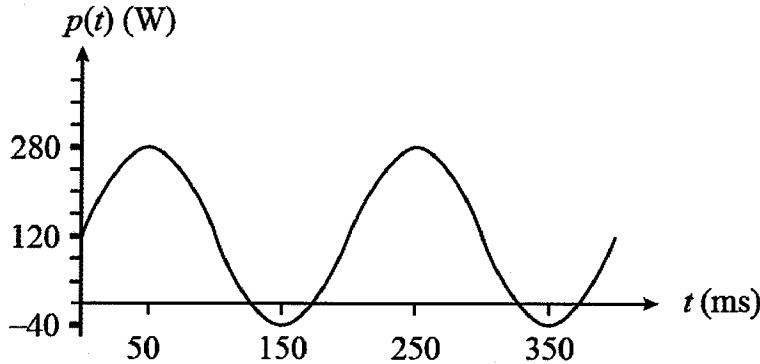


Ex:



Use the waveform of power versus time shown above to answer the following questions:

- Determine the value of ω .
- Calculate complex power $S = P + jQ$.
- Can the phasor values of V and I be determined uniquely from the waveform? If so, find V and I .

sol'n: a) The power waveform as shown isn't necessarily phase-shifted so that the phase-shift of the current, $i(t)$, is zero. (In fact, the phase shift of the current cannot be zero, as will be seen later on.)

Consider the power waveform when the angle of the current is not zero:

$$P(t) = v(t)i(t)$$

$$\text{"} = V_m \cos(\omega t + \theta_v) i_m \cos(\omega t + \theta_i)$$

$$P(t) = \frac{V_m i_m}{2} \cos(2\omega t + \theta_v + \theta_i) \quad \text{AC pwr}$$

$$+ \frac{V_m i_m}{2} \cos(\theta_v - \theta_i) \quad \text{DC pwr}$$

We compare this to the $p(t)$, which we will call $p_1(t)$, that we obtain when we assume $\theta_i = 0$:

$$p_1(t) = \frac{v_{mim}}{2} \cos(2\omega t + \theta_v - \theta_i) \quad \text{AC pwr}$$

$$+ \frac{v_{mim}}{2} \cos(\theta_v - \theta_i) \quad \text{DC pwr}$$

The key difference is that $p_1(t)$ has angle $\theta_v - \theta_i$, whereas $p(t)$ has angle $\theta_v + \theta_i$.

This discrepancy involves only the phase shift. The frequency of $p(t)$ is still 2ω .

We now find ω .

The period of $p(t)$ is $T = 250\text{ms} - 50\text{ms}$
or $T = 200\text{ ms}$.

$$\text{So } 2\omega = \frac{2\pi}{T} \quad \text{or} \quad \omega = \frac{\pi}{T} = \frac{\pi}{200\text{ms}}$$

$$\text{or} \quad \omega = 5\pi \text{ rad/s}$$

- b) The complex power, S , is the phasor of the AC part of $p_1(t)$, (not the phasor of the AC part of $p(t)$).

We have only $p(t)$ not $p_1(t)$, but the DC offset of $p(t)$ and $p_1(t)$ is the same:

$$P = \frac{v_{mim}}{2} \cos(\theta_v - \theta_i) = 120 \text{ W}$$

(from graph
of $p(t)$)

The magnitude of the AC pwr part of $p(t)$ and $p_1(t)$ is also the same, and the magnitude of the AC pwr is $|S| = \sqrt{P^2 + Q^2}$.

From the graph, the magnitude of the sinusoidal part of $p_1(t)$ is

$$|S| = 280W - 120W = 160W.$$

Now we can solve for Q .

$$160W = \sqrt{(120W)^2 + Q^2}$$

or

$$160^2 W^2 = 120^2 W^2 + Q^2$$

or

$$256(100)W^2 - 144(100)W^2 + Q^2$$

or

$$112(100)W^2 = Q^2$$

or

$$Q = \pm \sqrt{112} \cdot 10 \text{ VAR}$$

or

$$Q = \pm 105.8 \text{ VAR}$$

Note: we write Watts in different ways so we can tell which pwr quantity we are looking at, if all we see is a number. We use the following units:

P (W), Q (VAR), S (VA)

VAR stands for volt-amps reactive

c) Now we try to determine V and II.

We observe that $|S| = \frac{v_m i_m}{2} = 160W$

and $P = \frac{v_m i_m}{2} \cos(\theta_{v-i}) = 120W$.

$$\text{So } \frac{P}{Q} = \cos(\theta_{v-i})$$

and

$$\theta_{v-i} = \cos^{-1}\left(\frac{P}{Q}\right) = \cos^{-1}\left(\frac{3}{4}\right)$$

$$\theta_{v-i} = 41.4^\circ = \theta_v - \theta_i$$

If we look at $p(t)$ at time $t=0$, we have

$$\begin{aligned} p(0) &= \frac{v_m i_m}{2} \cos(\theta_v + \theta_i) \\ &\quad + \frac{v_m i_m}{2} \cos(\theta_v - \theta_i) \\ &= \frac{v_m i_m}{2} \cos(\theta_v + \theta_i) \\ &\quad + P \\ &= P = 120W \text{ (from graph)} \end{aligned}$$

$$\text{So } \frac{v_m i_m}{2} \cos(\theta_v + \theta_i) = 0$$

This means $\theta_v + \theta_i = \pm 90^\circ$. Looking at $p(t)$, we see a waveform that looks like $\sin(2\omega t)$ rather than $-\sin(2\omega t)$ starting from $t=0$.

$$\text{So } \theta_v + \theta_i = -90^\circ$$

$$\text{and } \theta_v - \theta_i = 41.4^\circ.$$

Summing eq's, we have

$$2\theta_V = -90^\circ + 41.4^\circ = -48.6^\circ$$

or

$$\theta_V = -24.3^\circ$$

It follows that $\theta_i = -65.7^\circ$.

$$\text{We have } |S| = \frac{v_m i_m}{2} = 160W$$

or $v_m i_m = 320 W$.

Nowhere in our eq's do we see anything but $v_m i_m$. Thus, we have no way of uniquely determining v_m and i_m .

$$V = v_m \angle -24.3^\circ$$

$$I = i_m \angle -65.7^\circ$$

and $v_m i_m = 320 W$

Note: $\frac{v_m}{i_m} = |z|$, so we could find

v_m and i_m if we knew z .