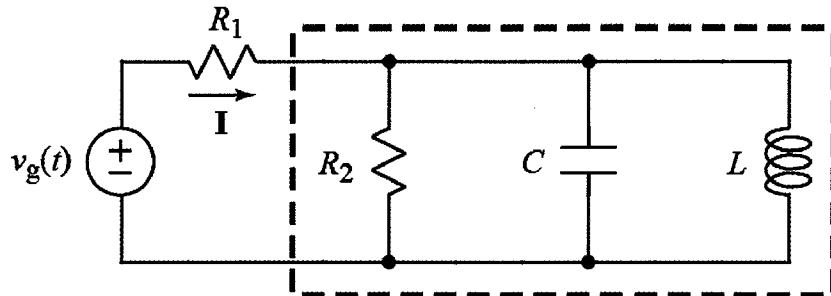


Ex:



$$v_g(t) = 5 \cos(2\pi M t) V$$

$$R_1 = 0.1 \Omega \quad R_2 = 1 \Omega$$

$$C = 1 \mu F \quad L = 125 \text{ nH}$$

- a) Calculate I.
- b) Calculate the complex power, S, for the components inside the box.

sol'n: a) We use phasor currents and voltages, and impedances.

$$V_g = P [v_g(t) = 5 \cos(2\pi M t) V]$$

$$V_g = 5 \angle 0^\circ V$$

$$\frac{1}{j\omega C} = \frac{1}{j2\pi M(1\mu)} = -j \frac{1}{2} \Omega$$

$$j\omega L = j2\pi M(125n) \Omega = j \frac{1}{4} \Omega$$

Now we calculate  $z_{\text{box}}$ , starting with the reactive components, L and C. (The idea is to keep imaginary quantities together and real quantities together.)

$$\frac{1}{j\omega C} \parallel j\omega L = \frac{1}{\frac{1}{j\omega C} + \frac{1}{j\omega L}} = \frac{1}{j\omega C + -j \frac{1}{\omega L}}$$

$$\frac{1}{j\omega C} \parallel j\omega L = \frac{1}{jz - j^4 \Omega} = \frac{1}{-j^2 \Omega}$$

$$" = j \frac{1}{2} \Omega$$

$$Z_{box} = 1 \Omega \parallel j \frac{1}{2} \Omega = \frac{1}{\frac{1}{1 \Omega} + \frac{1}{j \frac{1}{2}}}$$

$$" = \frac{1}{1 - j^2} \Omega \cdot \frac{1 + j^2}{1 + j^2}$$

$$" = \frac{1 + j^2}{5} \Omega = 0.2 + j 0.4 \Omega$$

The current is equal to  $V_g$  divided by the total impedance in the circuit.

$$I = \frac{V_g}{0.1 \Omega + 0.2 + j 0.4 \Omega} = \frac{5 \angle 0^\circ V}{0.3 + j 0.4 \Omega}$$

$$" = \frac{5 \angle 0^\circ V}{0.5 \angle 53^\circ \Omega}$$

$$I = 10 \angle -53^\circ A$$

b) We have various formulae for  $S$ , based on a basic eqn and Ohm's law,  $V = IZ$ :

$$S = \frac{V I^*}{2} = \frac{|I|^2 Z}{2} = \frac{|V|^2}{2 Z^*}$$

where \* means complex conjugate.

Here, we use  $S^* = \frac{|I|^2}{2} Z_{box}$ .

$$S = \frac{10^2}{2} \cdot (0.2 + j 0.4) VA = 10 + j 20 VA$$