
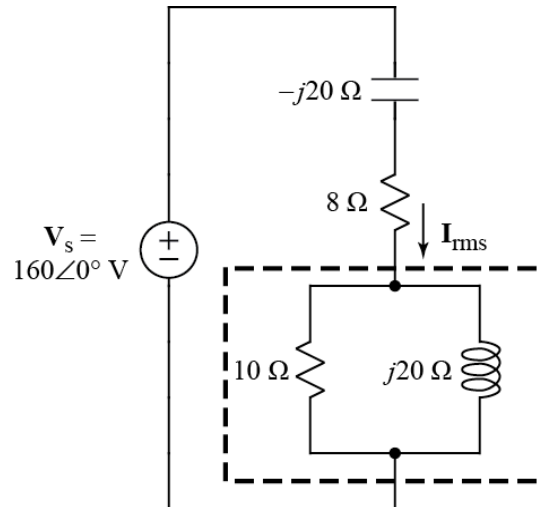


1.

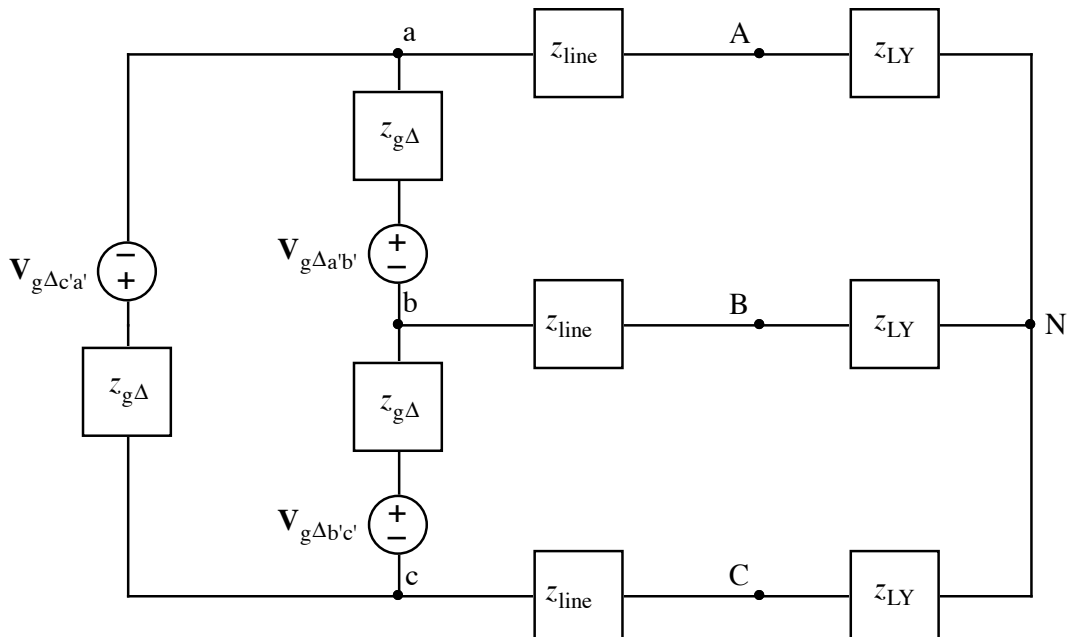

- Calculate the value of rms current, I_{rms} , flowing down through the dashed box.
- Calculate the complex power, S , for the circuitry inside the dashed box.

2.



$$V_{g\Delta a'b'} = 168\angle 0^\circ \text{ V} \quad z_{g\Delta} = 0.90 + j1.62 \ \Omega$$

$$V_{g\Delta b'c'} = 168\angle +120^\circ \text{ V} \quad z_{\text{line}} = 0.51 + j4.92 \ \Omega$$


$$V_{g\Delta c'a'} = 168\angle -120^\circ \text{ V} \quad z_{LY} = 7.92 - j1.58 \ \Omega$$

Draw a single-phase equivalent circuit.

3.


Calculate the voltage drop V_{BC} from B to C.

4.

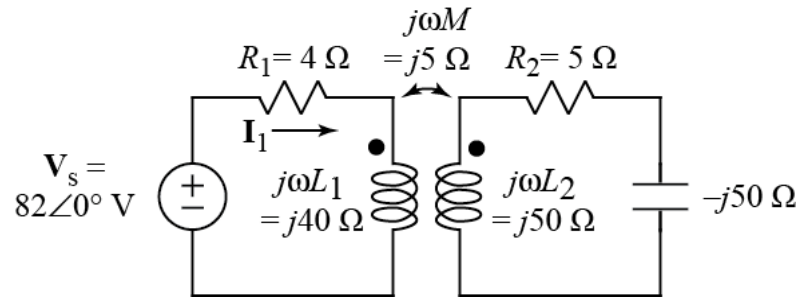

Calculate the numerical value of phasor current, I_1 , flowing into the primary side of the transformer. Note: the transformer is linear.

5.

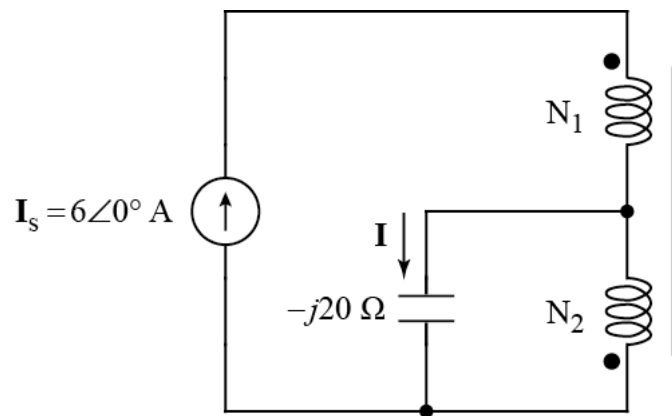

The turns ratio of the transformer is $N_1/N_2 = 6$. Calculate the numerical value of phasor current, I , flowing down through the capacitor. Note: the transformer is ideal.