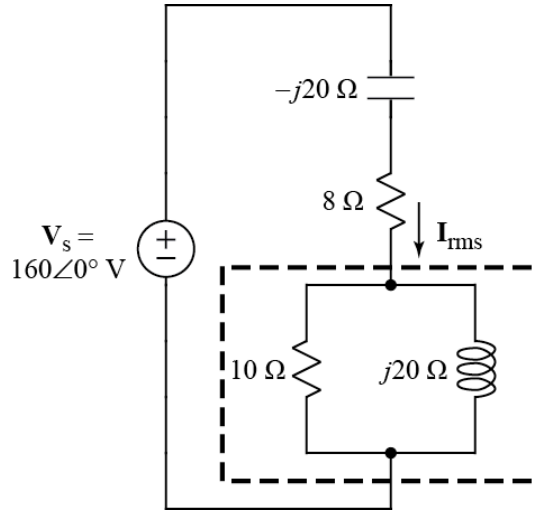


Ex:



- Calculate the value of rms current, I_{rms} , flowing down through the dashed box.
- Calculate the complex power, S , for the circuitry inside the dashed box.

$$\text{sol'n: a)} \quad I_{rms} = \frac{V_s}{\sqrt{2}} \frac{1}{z_{tot}} = \frac{160 \angle 0^\circ \text{ V}}{\sqrt{2}} \frac{1}{z_{tot}}$$

We divide V_s by $\sqrt{2}$ to convert to rms.

$$z_{tot} = -j20 \Omega + 8 \Omega + 10 \Omega \parallel j20 \Omega$$

$$\text{where } 10 \Omega \parallel j20 \Omega = 10 \Omega \cdot \parallel j2$$

$$= 10 \Omega \frac{j2}{1+j2} \frac{1-j2}{1-j2} = \frac{10 \Omega (4+j2)}{5}$$

$$= 2(4+j2) \Omega = 8 + j4 \Omega$$

$$z_{tot} = -j20 \Omega + 8 \Omega + 8 \Omega + j4 \Omega = 16 - j16 \Omega$$

$$I_{rms} = \frac{160 \angle 0^\circ \text{ V}_{rms}}{\sqrt{2}} \frac{1}{16 - j16 \Omega}$$

$$= \frac{160}{\sqrt{2}} \frac{1}{16\sqrt{2} \angle -45^\circ} \text{ A}_{rms}$$

$$= \frac{160}{32} \angle 45^\circ \text{ A}_{rms}$$

$$I_{rms} = 5 \angle 45^\circ \text{ A}_{rms}$$

$$\begin{aligned} \text{b) } S &= |I_{\text{rms}}|^2 Z \\ &= 5^2 \cdot (8 + j4) \text{ VA} \\ S &= 200 + j100 \text{ VA} \end{aligned}$$