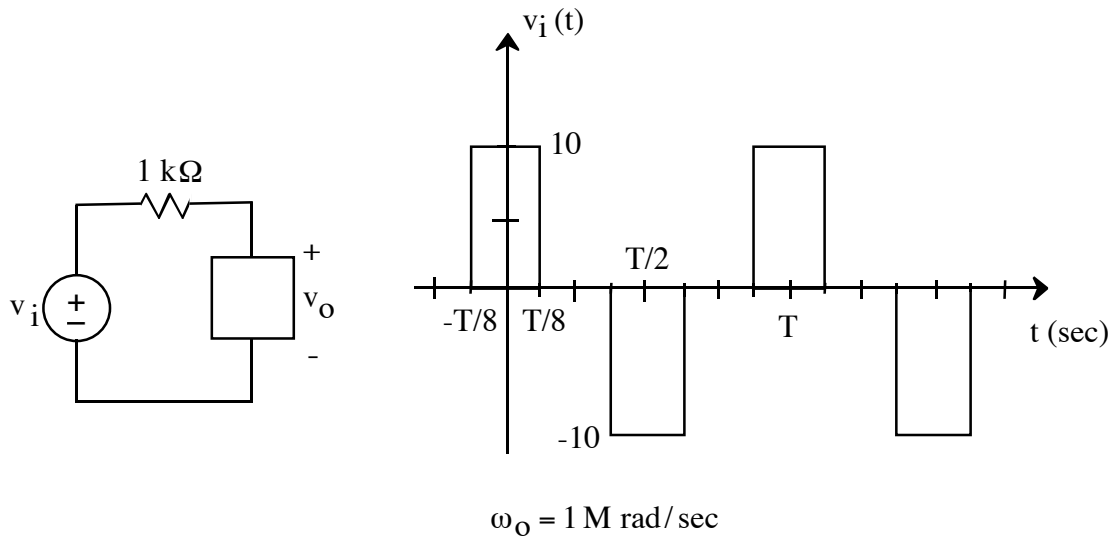


2. (50 points)



- a. Determine the coefficients of the Fourier series,  $a_v$ ,  $a_n$ , and  $b_n$ , for the periodic waveform  $v_i(t)$ . Also, use these Fourier coefficients to find the coefficients of the first five terms of the Fourier series written in terms of inverse phasors:

$$v_1(t) = a_v + \sum_{n=1}^{\infty} A_n \cos(n\omega_0 t + \theta_n)$$

Note any symmetry properties of the waveform that you use to determine coefficients.

- b. The circuit on the left is a filter with output  $v_o(t)$ . Design a circuit to be placed in the box such that the filter rejects the fundamental frequency of  $v_i(t)$  and has a bandwidth of 10,000 rad/sec. Specify the component values. Show how the components are connected in the circuit.

ans: a)  $a_v = 0$

$$a_n = \begin{cases} \frac{40}{\pi n} \sin \frac{\pi n}{4} & n \text{ odd} \\ 0 & n \text{ even} \end{cases}$$


$$b_n = 0 \text{ for all } n$$

$$A_1 = \frac{20\sqrt{2}}{\pi}, \theta_1 = 0^\circ \quad A_2 = 0, \theta_2 = 0^\circ \quad A_3 = \frac{20\sqrt{2}}{3\pi}, \theta_3 = 0^\circ$$

$$A_4 = 0, \theta_4 = 0^\circ \quad A_5 = \frac{-4\sqrt{2}}{\pi}, \theta_5 = 0^\circ$$

Symmetries used: even function, half wave (shift-flip symmetry), and quarter wave symmetry.

b)

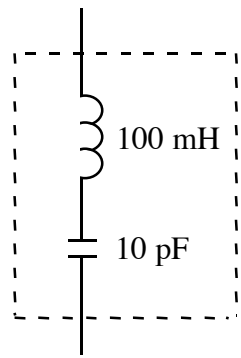

sol'n: (a)  $a_v =$  ave value of  $v_i(t) = 0$  since equal positive and negative areas are under the  $v_i(t)$  curve.

$v_i(t)$  is symmetric around vertical axis so  $v_i(t)$  is an even function. This means we need only even functions—cosine terms—in our Fourier series.


$\therefore b_n = 0$  for all  $n$  (no  $\sin(n\omega_0 t)$  terms in Fourier series)

If we shift  $v_i(t)$  one-half period and flip it upside down, we have  $v_i(t)$  again. Thus, we have half-wave symmetry or, as refer to it, shift-flip symmetry.

$\therefore a_n = 0$  for  $n$  even ( $b_n = 0$  for  $n$  even, too, but we already know  $b_n = 0$  all  $n$ )

For the question of quarter wave symmetry, we look for symmetry around  $T/4$  and  $3T/4$ . What we find is that  $v_i(t)$  is odd around  $T/4$  and  $3T/4$ . In other words, if the vertical axis for  $T = 0$  were shifted to  $T/4$  or  $3T/4$ ,  $v_i(t)$  would be an odd function. If we superimpose the  $\cos(n\omega_0 t)$  term for  $n = 1$  on  $v_i(t)$  and consider the signs of the product  $v_i(t)\cos(n\omega_0 t)$ , as shown below, we discover that we can calculate  $a_1$  by quadrupling the integral from 0 to  $T/4$  in the formula for  $a_1$ :
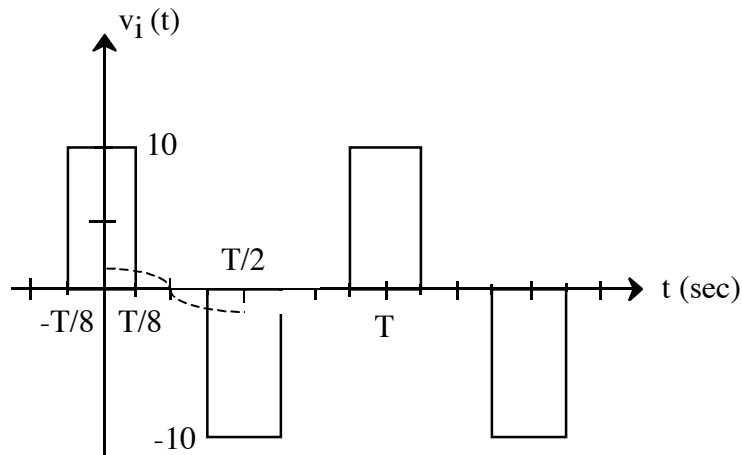
$$a_1 = 4 \cdot \frac{2}{T} \int_0^{T/4} v_i(t) \cos(1 \cdot \omega_o t) dt$$



$$\omega_o = 1 \text{ M rad/sec}$$

The same will hold true for every odd numbered  $n$ .

Now we define  $v_i(t)$  from 0 to  $T/4$ :

$$v_i(t) = \begin{cases} 10 & 0 \leq t \leq T/8 \\ 0 & T/8 < t \leq T/4 \end{cases}$$

Thus,

$$a_n = \frac{8}{T} \left[ \int_0^{T/8} 10 \cos(n\omega_o t) dt + \underbrace{\int_{T/8}^{T/4} 0 \cdot \cos(n\omega_o t) dt}_{\int 0 dt = 0} \right]$$

or

$$a_n = \frac{8}{T} \int_0^{T/8} 10 \cos(n\omega_o t) dt$$

$$= \frac{8}{T} \frac{10 \sin(n\omega_o t)}{n\omega_o} \Big|_0^{T/8}$$

Now substitute:

$$\omega_o \equiv \frac{2\pi}{T}$$

$$\begin{aligned}
 a_n &= \frac{8}{T} \left. \frac{10 \sin n \frac{2\pi}{T} t}{n \frac{2\pi}{T}} \right|_0^{T/8} \\
 &= \frac{40}{\pi n} \sin \left[ \frac{2\pi n}{T} \cdot \frac{T}{8} - \sin 0 \right] \\
 a_n &= \frac{40}{\pi n} \sin \left( \frac{\pi n}{4} \right) \quad \text{for } n \text{ odd}
 \end{aligned}$$

If we compute the values of  $\sin(\pi n/4)$  for  $n = 0, 1, \dots$  we get  $0, 1/\sqrt{2}, 1, 1/\sqrt{2}, 0, -1/\sqrt{2}, -1/\sqrt{2}, 0$ , in a repeating pattern.

Therefore,  $a_n$  coefficients for  $n$  odd up to the fifth harmonic are:

$$a_1 = \frac{\sqrt{2}}{2} \cdot \frac{40}{\pi}, \quad a_3 = \frac{\sqrt{2}}{2} \cdot \frac{40}{3\pi}, \quad a_5 = \frac{-\sqrt{2}}{2} \cdot \frac{40}{5\pi}$$

Now we convert to phasor form,  $a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t)$ . The time-domain rectangular representation of the  $n$ th term of the Fourier series is

$$a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t)$$

Recalling that the phasor for pure  $\cos()$  is 1 and for pure  $\sin()$  is  $-j$ , the phasor for the  $n$ th term of the Fourier series is

$$a_n \text{ (or } a_n \angle 0^\circ) + -jb_n \text{ (or } b_n \angle -90^\circ)$$

Thus, our phasor is  $a_n - jb_n$ . Incidentally, if we convert to polar form,  $A_n \angle \theta_n$ , we have:

$$A_n = \sqrt{a_n^2 + b_n^2}$$

$$\theta_n = \tan^{-1} \left( \frac{-b_n}{a_n} \right)$$

Here, however, all  $b_n = 0$ . So we have  $A_n = a_n$ ,  $\theta_n = 0^\circ$ . In other words, we have only  $\cos()$  terms, and the phase angle for  $\cos()$  terms is zero since they are real.

$$A_1 = a_1 = \frac{20\sqrt{2}}{\pi}, \quad \theta_1 = 0^\circ$$

$$A_3 = a_3 = \frac{20\sqrt{2}}{3\pi}, \quad \theta_3 = 0^\circ$$

$$A_5 = a_5 = \frac{-20\sqrt{2}}{5\pi}, \quad \theta_5 = 0^\circ$$

**Note:** You may find it easier to derive symmetry results by drawing  $v_i(t)$  and the  $\cos(\ )$  or  $\sin(\ )$  waveforms on a plot and multiplying them point by point (a rough sketch will do). The area under the curve corresponds to

$$\int_0^T v_i(t) \cos(\ ) \quad \text{or} \quad \int_0^T v_i(t) \sin(\ )$$

If the positive and negative areas under the product curves cancel,  $a_n$  (or  $b_n$ ) = 0.

**sol'n: (b)** We want a band reject filter with center frequency =  $\omega_o = 1\text{M rad/s}$ , (see diagram in problem statement), and bandwidth  $\beta = 10\text{k rad/s}$  (see problem statement).

Note: By coincidence, in this problem  $\omega_o$  for the Fourier series (which is determined by the value of the period,  $T$ ), happens to be the same as the center frequency,  $\omega_o$ , of the filter (which is determined the values of  $R$ ,  $L$ , and  $C$ ). This need not always be the case.

Our transfer function is  $H(s) \equiv V_o(s)/V_i(s)$ .

We use V-divider formula for  $V_o(s)$  in terms of  $V_i(s)$ , letting  $z_L$  denote the impedance in the box.


$$V_o(s) = V_i(s) \cdot \frac{z_L}{1\text{ k}\Omega + z_L}$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{z_L}{1\text{ k}\Omega + z_L}$$

We need  $z_L = 0$  at  $\omega = 1\text{M}$  to get

$$\frac{V_o(s = j\omega = j1\text{Mr/s})}{V_i(s = j\omega = j1\text{Mr/s})} = 0$$

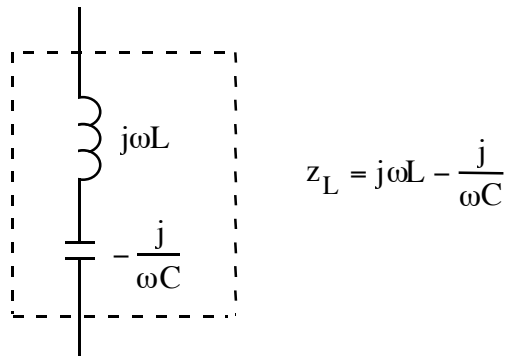We use an  $L$  in series with a  $C$  to get  $z$  cancellation:



To get cancellation,  $\omega L = 1/\omega C$  at  $\omega = 1\text{M}$  or

$$LC = \frac{1}{\omega^2} = \frac{1}{(1\text{M})^2} = 1 \text{ ps}$$

We have RLC in series, and for a series RLC band-reject filter, we have  $\beta = R/L$ . For  $\beta = 10\text{k rad/s}$  and  $R = 1 \text{ k}\Omega$ , we get

$$L = R/\beta = 0.1 \text{ H.}$$

Knowing L, we can now solve for C:

$$C = \frac{1}{L\omega^2} = \frac{1}{0.1\text{H}(1\text{M/s})^2}$$

$$\therefore C = 10 \text{ pF}$$