
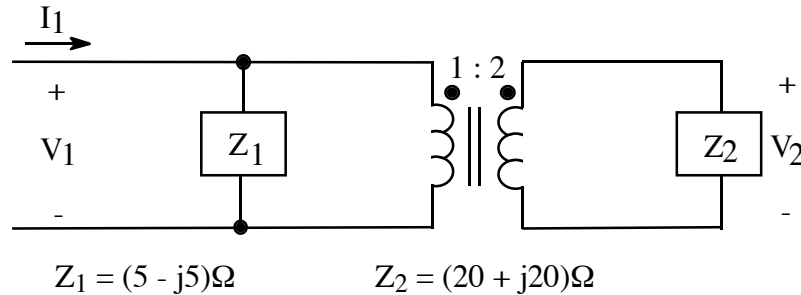


4. (50 points)

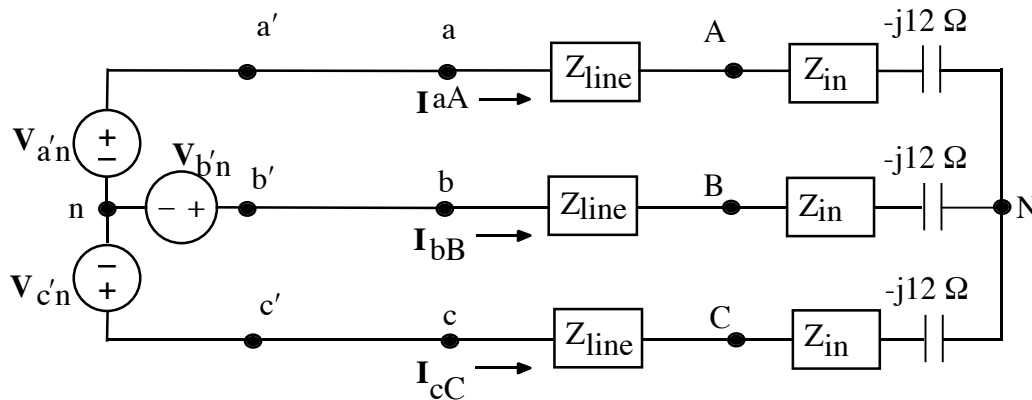

- a. Find the input impedance, $z_{in} = \mathbf{V}_1/\mathbf{I}_1$, for the above circuit.
- b. Using z_{in} from (a), find a numerical expression for \mathbf{V}_{AB} in the circuit below.



Balanced three-phase system.


$$\mathbf{V}_{a'n} = 52 \angle 0^\circ \text{ V}$$

$$\mathbf{V}_{b'n} = 52 \angle -120^\circ \text{ V}$$

$$z_{line} = j12 \Omega$$

ans: a) $z_{in} = 5 \Omega$ b) $\mathbf{V}_{AB} \approx 234 \angle -37.38^\circ \text{ V}$

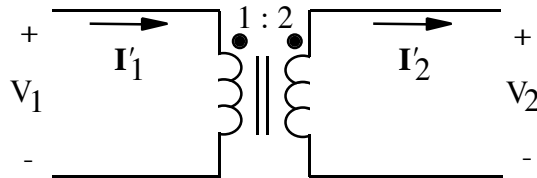sol'n: (a) Transformer is ideal. To distinguish currents in the transformer itself from other currents, we use a prime to denote the transformer currents. The current flowing into the dot on the primary side is \mathbf{I}'_1 , and the current flowing out of the dot on the secondary side is \mathbf{I}'_2 :




$$\frac{V_1}{V_2} = \frac{N_1}{N_2} \quad \frac{I'_1}{I'_2} = \frac{N_2}{N_1}$$

Using the above model, we can derive the formula (or we can just look up the formula) for secondary impedance reflected into the primary:

$$z_r = \left(\frac{N_1}{N_2} \right)^2 z_2$$

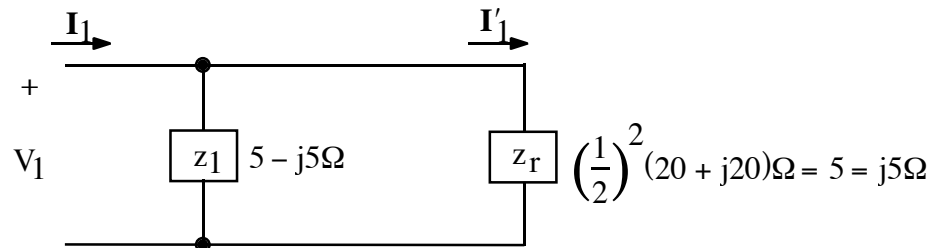
Our model, given $N_1/N_2 = 1/2$ turns ratio, is:



$$z = z_1 \parallel z_r = (5 - j5) \parallel (5 + j5)\Omega$$

$$z = \frac{(5 - j5)(5 + j5)}{5 - j5 + 5 + j5} = \frac{5^2 + 5^2}{10} = 5\Omega$$

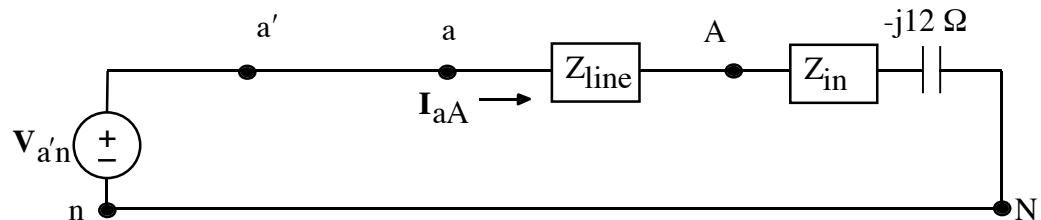sol'n: (b) Our first step is to convert our circuit to a Y – Y form so we can use a single-phase equivalent model. In this problem, the circuit is already in Y – Y form and we may draw the single-phase equivalent directly:




We find V_{AN} and then calculate V_{AB} using phasor diagrams. We obtain V_{AN} from the voltage divider formula:

$$V_{AN} = V_{a'n} \frac{z_{in} - j12\Omega}{z_{line} + z_{in} - j12\Omega}$$

$$V_{AN} = 52\angle 0^\circ V \frac{5\Omega - j12\Omega}{j12\Omega + 5\Omega - j12\Omega} = 52\angle 0^\circ V \frac{5\Omega - j12\Omega}{5\Omega}$$

$$V_{AN} = 52\angle 0^\circ V \frac{13\angle -67.38^\circ \Omega}{5\Omega}$$

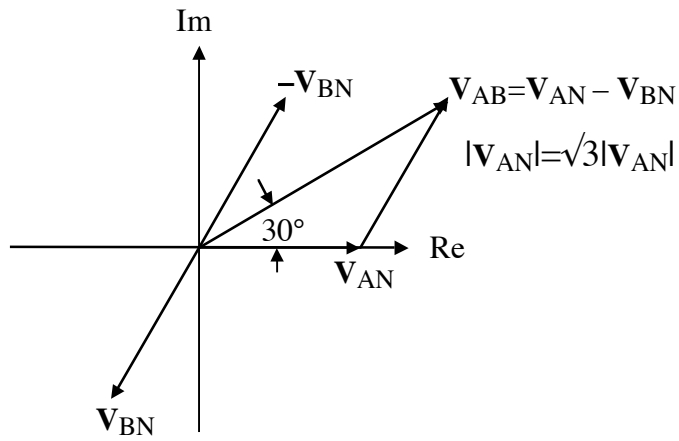We use a phasor diagram to relate V_{AN} to V_{AB} . The diagram shows the relationship between V_{AN} and V_{AB} , and we assume V_{AN} has phase angle zero so we can find the relative phase angle of V_{AB} .



From the diagram, we deduce that

$$\mathbf{V}_{AB} = \mathbf{V}_{AN} \cdot \sqrt{3} \angle 30^\circ$$

Plugging in the value of \mathbf{V}_{AN} gives the numerical value of \mathbf{V}_{AB} .

$$\mathbf{V}_{AB} = 52 \angle 0^\circ \text{V} \frac{13 \angle -67.38^\circ \Omega}{5 \Omega} \sqrt{3} \angle 30^\circ = \frac{52 \cdot 13 \cdot \sqrt{3}}{5} \angle -37.38^\circ \text{V}$$

$$\mathbf{V}_{AB} \approx 234 \angle -37.38^\circ \text{V}$$