
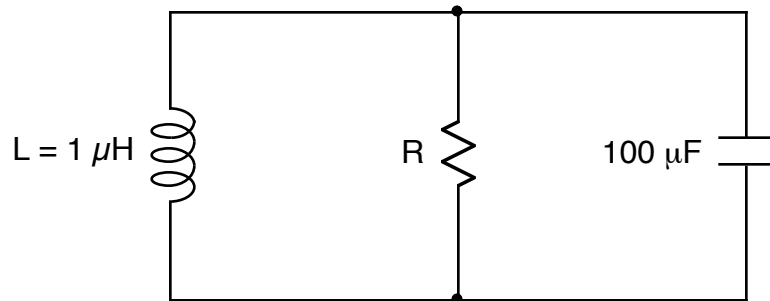


1.

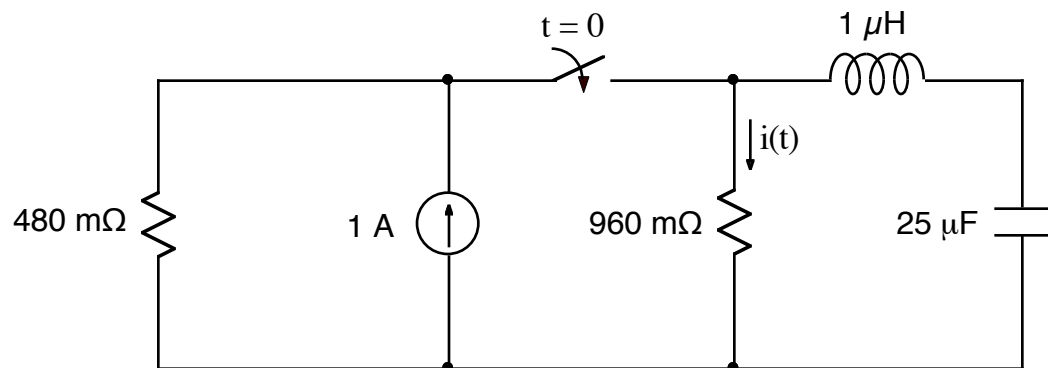

- If $R = 40 \text{ m}\Omega$, find the characteristic roots, s_1 and s_2 , for the above circuit.
- If $R = 40 \text{ m}\Omega$, find the value of L that makes the circuit critically damped.
- If $L = 1 \mu\text{H}$, find the damping frequency, ω_d , for the value of R that gives a damping frequency of $\alpha = 10 \text{ krad/s}$.

2.



After being open for a long time, the switch closes at $t = 0$.

Find $i(t)$ for $t > 0$.