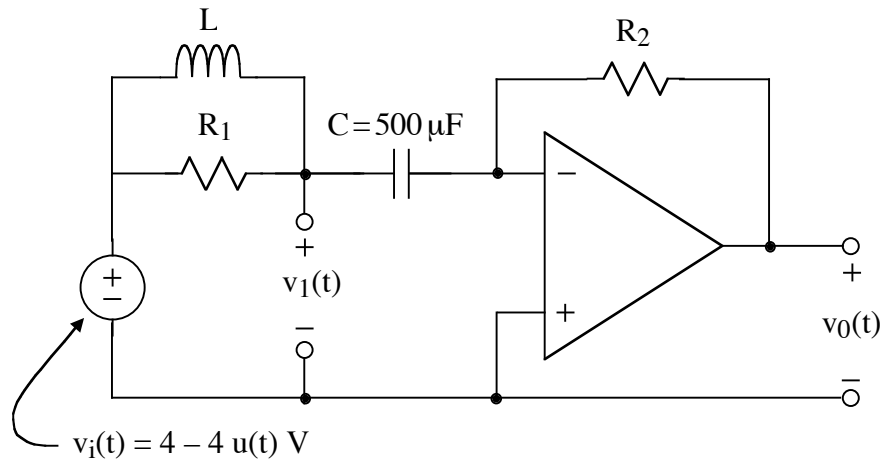



1.



- Find a symbolic expression for $V_o(s)$ in terms of not more than R_1 , R_2 , L , C , and constants.
- Choose numerical values for R_1 and L to make


$$v_1(t) = v_m e^{-\alpha t} \cos(\beta t + \varphi)$$
 where $\alpha = \beta = 100 \text{ rad/s}$ and v_m and φ are constants.

2.

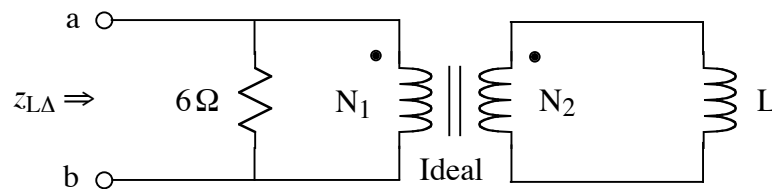

Given $N_1/N_2 = 2$ and $\omega = 100 \text{ rad/s}$, find a numerical value for L to make $z_{L\Delta} = 3 + j3 \Omega$.

3.

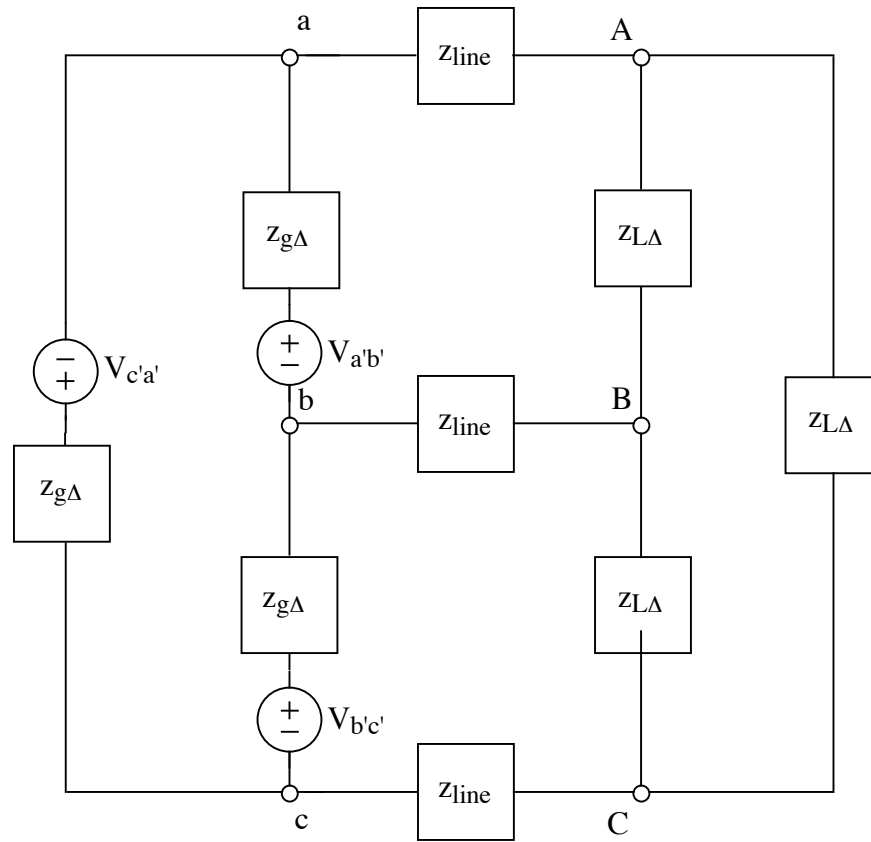

$$V_{a'b'} = 142 \angle 0^\circ \text{ V} \quad z_{g\Delta} = 24 + j33 \, \Omega$$

$$V_{b'c'} = 142 \angle -120^\circ \text{ V} \quad z_{line} = j28 \, \Omega$$

$$V_{c'a'} = 142 \angle 120^\circ \text{ V} \quad z_{L\Delta} = 3 + j3 \, \Omega$$

Find the numerical value of the current, I_{bB} .