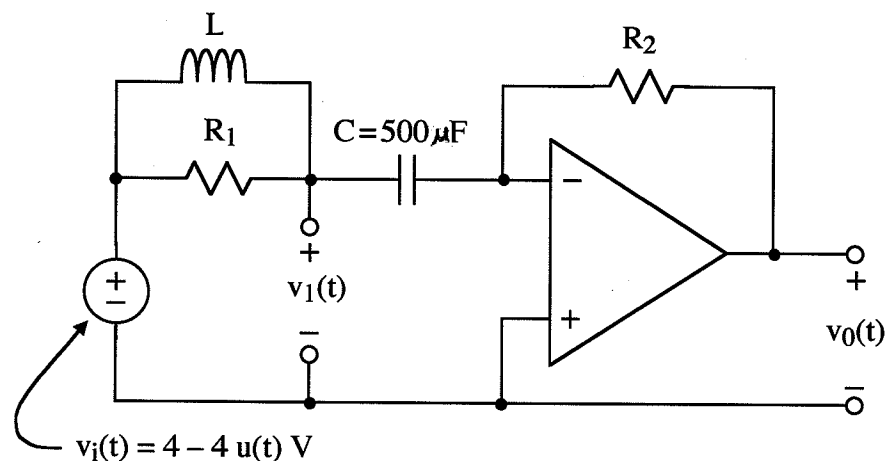


Ex:




Find a symbolic expression for $V_o(s)$ in terms of not more than R_1 , R_2 , L , C , and constants.

Sol'n: To find the Laplace transformed circuit elements, we first find initial conditions for L and C : $i_L(0^-)$ and $v_C(0^-)$.

For a long time before $t=0$, $v_i(t) = 4V$.

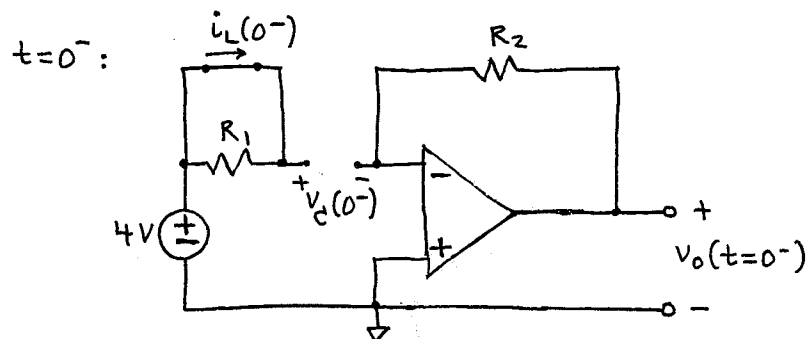For this DC input, the circuit will reach an equilibrium with constant currents and voltages. Thus, derivatives di_L/dt and dv_C/dt equal zero. This, in turn, means $v_L = 0$ and $i_C = 0$. So $L = \text{wire}$ and $C = \text{open}$.



The op-amp has negative feedback that acts to keep $V_- \doteq V_+$. Thus, we have 0V at the inputs of the op-amp.

If we consider a voltage passing through the 4V source, $L = \text{wire}$, $C = \text{open}$, and across the op-amp inputs = 0V drop, we have

$$V_C(0^-) = 4V.$$

Since $C = \text{open}$, we also have

$$i_L(0^-) = 0A.$$

Now we Laplace transform the input voltage to obtain a model for the s-domain.

$$\begin{aligned}\mathcal{L}\{4 - 4u(t)\} &= \mathcal{L}\{4\} - \mathcal{L}\{4u(t)\} \\ &= \frac{4}{s} - \frac{4}{s} \\ &= 0\end{aligned}$$


Thus, $V_i(s) = 0V$ which is wire.

Using a parallel current source for initial conditions on the L , we have $0/s = 0A = \text{open}$. Thus, we may leave out this source.

Using a series voltage source for initial conditions on C , we would have $4V/s$. Since we have a virtual reference at V_- , however, C is effectively in parallel with R_1 and C .

Thus, we use a parallel current source for initial conditions on C . The value of the current source is $Cv_c(0^-) = C \cdot 4V$. The direction of current is chosen to place charge instantly on C that will yield $4V$ at time 0^+ across C . (Note that, in the time-domain, $C \cdot 4V$ corresponds to $C \cdot 4V \cdot \delta(t)$.)

s-domain model:

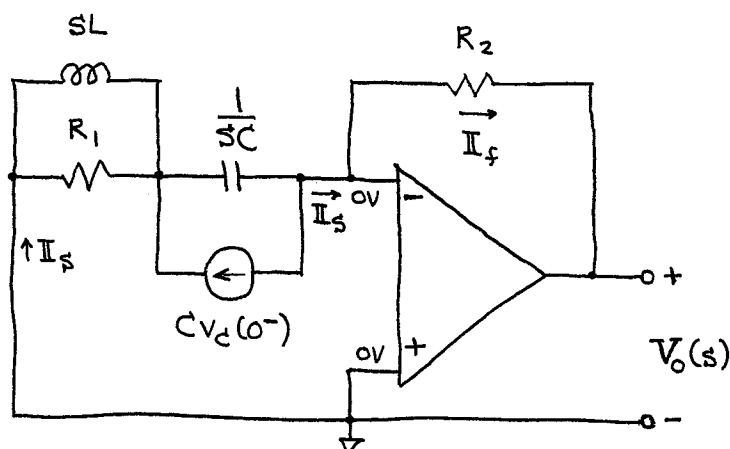

To solve this op-amp circuit, we observe that $V_+ = 0V$ and $V_- = V_+ = 0V$.

Since no current flows into the op-amp, we also have I_s flowing toward the - input from the left is the same as current I_f flowing in R_2 . We write equations for I_s and I_f using $V_- = 0V$. Then we set $I_s = I_f$ and solve for $V_o(s)$.

We observe that I_s is the current flowing in R_1 and sL , and we use a current divider eq'n.

$$I_s = -C v_c(0^-) \frac{1/sC}{1/sC + R_1 \parallel sL}$$

$$= -C v_c(0^-) \frac{1}{1 + sC \cdot R_1 \parallel sL}$$

$$= -C v_c(0^-) \frac{1 + R_1/sL}{1 + \frac{R_1}{sL} + sR_1C}$$

$$= -C v_c(0^-) \frac{sL + R_1}{sL + R_1 + s^2 R_1 LC}$$

$$I_s = -\cancel{C} v_c(0^-) \frac{1}{R_1 \cancel{C}} \cdot \frac{s + R_1/L}{s^2 + \frac{1}{R_1 C} s + \frac{1}{LC}}$$

$$\text{or } I_s = -\frac{4V}{R_1} \frac{s + R_1/L}{s^2 + \frac{1}{R_1 C} s + \frac{1}{LC}}$$

For I_f , we have

$$I_f = \frac{0V - V_o(s)}{R_2} = -\frac{V_o(s)}{R_2}$$

Equating I_s and I_f and solving for $V_o(s)$ yields

$$V_o(s) = -R_2 I_s$$

$$V_o(s) = 4V \cdot \frac{R_2}{R_1} \cdot \frac{s + R_1/L}{s^2 + \frac{1}{R_1 C} s + \frac{1}{LC}}$$