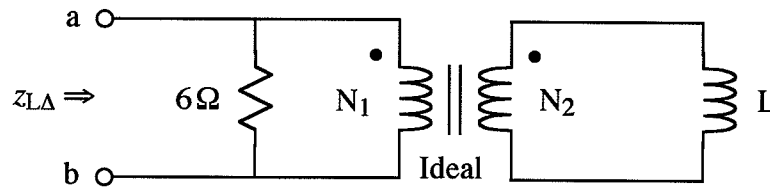


Ex:




Given $N_1/N_2 = 2$ and $\omega = 100 \text{ rad/s}$, find a numerical value for L to make $z_{LA} = 3 + j3 \Omega$.

sol'n: We use the idea of reflected impedance.

We replace the transformer and the secondary's impedance, z_L , with z_r :

$$z_r = \left(\frac{N_1}{N_2} \right)^2 j\omega L = 2^2 \cdot j100 \text{ r/s } L$$

circuit model:

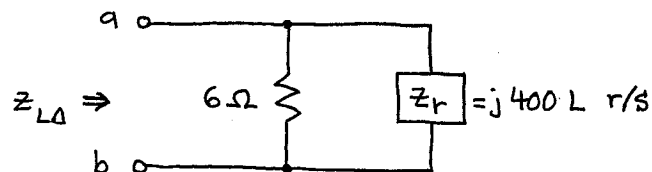

We are given $z_{LA} = 3 + j3 \Omega = 3(1+j) \Omega$.

Since we have parallel impedances, it simplifies matters if we use conductance:

$$\frac{1}{z_{LA}} = \frac{1}{3(1+j) \Omega} = \frac{1}{6 \Omega} + \frac{1}{j400 L \text{ r/s}}$$

"

$$\frac{1}{z_{LA}} = \frac{1-j}{\underbrace{3(1+j)(1-j)}_2 \Omega} = \frac{1}{6 \Omega} + \frac{-j}{400 L \text{ r/s}}$$

$$\frac{1}{Z_{LA}} = \frac{1}{6\Omega} - \frac{j}{6\Omega} = \frac{1}{6\Omega} - \frac{j}{400L \text{ r/s}}$$

$$\text{We have } 400L \text{ r/s} = 6\Omega$$

$$\text{or } L = \frac{6\Omega}{400 \text{ r/s}}$$

$$\text{or } L = 15 \text{ mH}$$