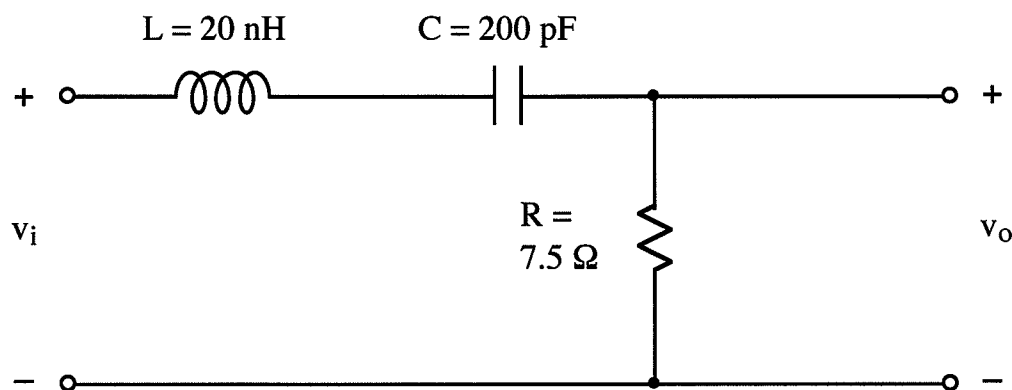


3.



For the band-pass filter shown above, calculate the following quantities:

- a) ω_o
- b) f_o
- c) ω_{C1} and ω_{C2}
- d) β and Q

sol'n: a) For this standard form of filter, the center frequency is $\omega_o = 1/\sqrt{LC}$.

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{20\text{n} \cdot 200\text{p}} = \left(\frac{1}{2\text{n}}\right)^2$$

Note: ω_o is where $|H(s)| = \text{min or max}$.
We accept that min or max of $|H(s)|$ occurs where $\omega = \omega_o$. We could prove this by finding $H(s)$.

$$\omega_o = \frac{1\text{r/s}}{2\text{n}} = \frac{1}{2} \text{ G r/s or } 500 \text{ M r/s}$$


b) $f_0 = \frac{\omega_0}{2\pi}$ since $\omega = 2\pi f$ in general

$$f_0 = \frac{500 \text{ M Hz}}{2\pi} = 79.6 \text{ kHz}$$

c) We could use standard formulas for ω_{c1} and ω_{c2} , but the derivation is instructive.

$\omega_{c1,2}$ occur where $|H(s)| = \frac{1}{\sqrt{2}} \max_{\omega} |H(s)|$.

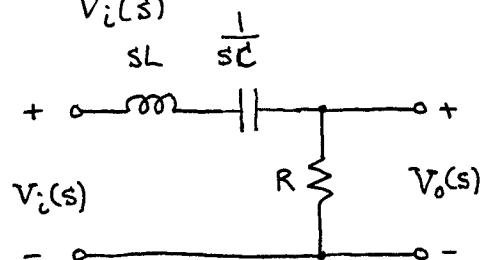$H(s) \equiv \frac{V_o(s)}{V_i(s)}$ for frequency domain model:



$$H(s) = \frac{R}{R + sL + \frac{1}{sC}} = \frac{1}{1 + sL + \frac{1}{sC}} \cdot \frac{1}{R}$$

$$H(j\omega) = \frac{1}{1 + j\omega L + \frac{1}{j\omega C}} \cdot \frac{1}{R} = \frac{1}{1 + j\left(\omega L - \frac{1}{\omega C}\right)} \cdot \frac{1}{R}$$

At ω_0 we have $\omega L - \frac{1}{\omega C} = 0$ and $|H| = 1$.

This is the maximum value $|H|$ can have; this is the only frequency where the imaginary part of H is zero.

It follows that $\omega_{c1,2}$ solve $|H| = \frac{1}{\sqrt{2}} \cdot 1 = \frac{1}{\sqrt{2}}$.

$$|H(j\omega_c)| = \frac{1}{\left| \frac{1 + j\left(\omega_c L - \frac{1}{\omega_c C}\right)}{R} \right|} = \frac{1}{\sqrt{2}}$$

$$\text{or } \left| \frac{1 + j\left(\omega_c L - \frac{1}{\omega_c C}\right)}{R} \right| = \sqrt{2}$$

$$\text{The sol'n is } \frac{\omega_c L - \frac{1}{\omega_c C}}{R} = \pm 1$$

$$\text{or } \frac{L\omega_c^2 - \frac{1}{C}}{R} = \pm \omega_c$$

$$\text{or } L\omega_c^2 - \frac{1}{C} = \pm R\omega_c$$

$$\text{or } \omega_c^2 - \frac{1}{LC} \mp \frac{R}{L}\omega_c = 0$$

$$\text{or } \omega_c = \pm \frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

Since ω_c 's > 0 and $\sqrt{\quad}$ term $> \frac{R}{2L}$, we use

$$\omega_{c1,2} = \pm \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

Now for the numbers:

$$\frac{R}{2L} = \frac{7.5\Omega}{2 \cdot 20 \text{ nH}} = \frac{7.5 \cdot 25}{40 \text{ n}} = 187.5 \text{ Mr/s}$$

$$\sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} = \sqrt{(187.5M)^2 + (500M)^2} \text{ r/s}$$

$$= 534 M \text{ r/s}$$

$$\text{Thus } \omega_{c1,2} = \pm 187.5 M + 534 M \text{ r/s}$$

$$\omega_{c1} = 346.5 M \text{ r/s}$$

$$\omega_{c2} = 721.5 M \text{ r/s}$$

$$d) \text{ Bandwidth } \beta = \omega_{c2} - \omega_{c1} = \frac{R}{L} = \frac{7.5}{20n} \text{ r/s}$$

$$\beta = \frac{7.5 \cdot 50}{20n \cdot 50} = 375 M \text{ r/s}$$

$$\text{Quality factor } Q = \frac{\omega_o}{\beta} = \frac{500 M \text{ r/s}}{375 M \text{ r/s}} = \frac{4}{3}$$