HOMEWORK #4



1.



After being open for a long time, the switch closes at t = 0.

The inductor carries no current at time $t = 0^{-}$.

Using not more than one each R, L, and C, design a circuit to go in the dashed-line box that will produce the $|H(j\omega)|$ vs. ω shown above, that is:

$$|H(j\omega)| = 0 \text{ at } \omega = 0$$

 $|H(j\omega)| = \frac{4}{9\sqrt{2}} \text{ at } \omega = 400 \text{ k rad/s}$
 $|H(j\omega)| = \frac{4}{9} \text{ as } \omega \rightarrow \infty$





One period, T, of a function v(t) is shown above. The formula for v(t) is

$$v(t) = \begin{cases} -12V & 0 < t < T/8 \\ -6V & T/8 < t < 3T/8 \\ -12V & 3T/8 < t < T/2 \\ 12V & T/2 < t < 5T/8 \\ 18V & 5T/8 < t < 7T/8 \\ 12V & 7T/8 < t < T \end{cases}$$

Find the numerical value of the following coefficients of the Fourier series for v(t):

- 2. a_v
- 3. a₁
- 4. a) b₁
 - b) b₂

5.



where

$$a_k = -\frac{1}{\pi^2 k^2}$$
$$b_k = \frac{\cos\left(\frac{\pi}{2}k\right)}{k}$$

Write the time-domain expression of the fifth harmonic (i.e., k = 5) of $v_0(t)$. Note: $\omega_0 = 5M$ rad/s.