
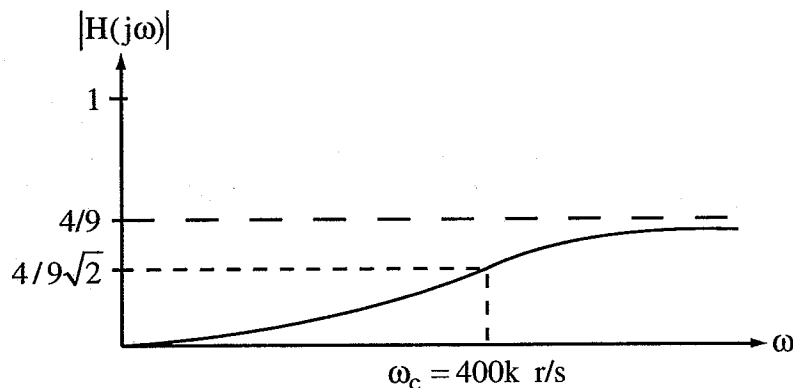


1. (30 points)

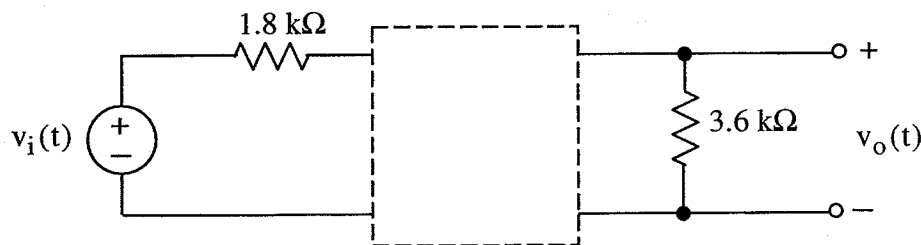

Using not more than one each R, L, and C, design a circuit to go in the dashed-line box that will produce the $|H(j\omega)|$ vs. ω shown above, that is:


$$|H(j\omega)| = 0 \text{ at } \omega = 0$$

$$|H(j\omega)| = \frac{4}{9\sqrt{2}} \text{ at } \omega = 400\text{k rad/s}$$

$$|H(j\omega)| = \frac{4}{9} \text{ as } \omega \rightarrow \infty$$

sol'n: At least two sol'ns are possible.

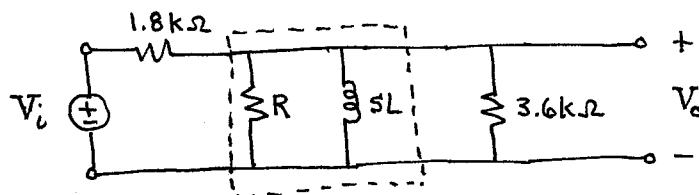I) Use an R and L in parallel across output:



The L shorts out for $\omega = 0 \Rightarrow V_o = 0, |H(j0)| = 0$.

As $\omega \rightarrow \infty$, $|H(j\infty)| \equiv \frac{V_o}{V_i} = \frac{R \parallel 3.6\text{k}\Omega}{R \parallel 3.6\text{k}\Omega + 1.8\text{k}\Omega}$ must be $\frac{4}{9}$,
(since L acts like open circuit).

An easy way to do the algebra to find R is to use ratios: $\frac{4}{9} = \frac{4}{4+5} = \frac{R \parallel 3.6 \text{ k}\Omega}{R \parallel 3.6 \text{ k}\Omega + 1.8 \text{ k}\Omega}$.


$$\text{Thus, } \frac{R \parallel 3.6 \text{ k}\Omega}{1.8 \text{ k}\Omega} = \frac{4}{5}, \quad R \parallel 3.6 \text{ k}\Omega = 1.8 \text{ k}\Omega \cdot \frac{4}{5}$$

$$\text{Factor out } 1.8 \text{ k}\Omega: \frac{R}{1.8 \text{ k}\Omega} \parallel 2 = \frac{4}{5} \quad \text{or} \quad R' \parallel 2 = \frac{4}{5}$$

$$\text{Now use conductance: } \frac{1}{R'} + \frac{1}{2} = \frac{5}{4} \quad \text{or} \quad \frac{1}{R'} = \frac{3}{4}$$

$$\text{Thus, } R' = \frac{4}{3} \Rightarrow \frac{R}{1.8 \text{ k}\Omega} = \frac{4}{3}, \quad R = \frac{4}{3}(1.8 \text{ k}\Omega) = 2.4 \text{ k}\Omega.$$

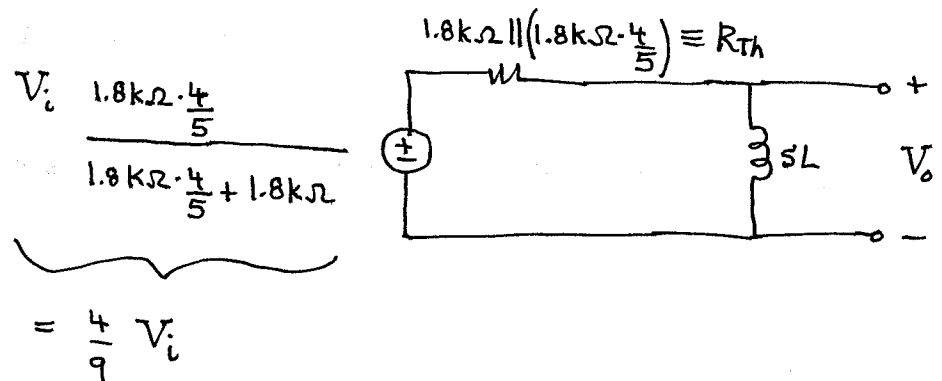To find ω_c , use a Thevenin equivalent for all the R 's and V_i . From above, $R \parallel 3.6 \text{ k}\Omega = 1.8 \text{ k}\Omega \cdot \frac{4}{5}$.



This is now in standard form, so $\omega_c = \frac{R_{Th}}{L} = 400 \text{ kr/s}$.

$$L = \frac{R_{Th}}{400 \text{ kr/s}}$$

$$R_{Th} = 1.8 \text{ k}\Omega \parallel \frac{4}{5} = 1.8 \text{ k}\Omega \cdot \frac{4}{5} \cdot \frac{1}{1 + \frac{4}{5}}$$


$$R_{Th} = 1.8 \text{ k}\Omega \cdot \frac{4}{9} = 0.8 \text{ k}\Omega$$

$$L = \frac{0.8 \text{ k}\Omega}{400 \text{ kr/s}} = \frac{0.8 (2.5)}{1 \text{ k}} \frac{\text{k}\Omega}{\text{r/s}} = 2 \text{ mH}$$

$$R = 2.4 \text{ k}\Omega$$

$$L = 2 \text{ mH}$$

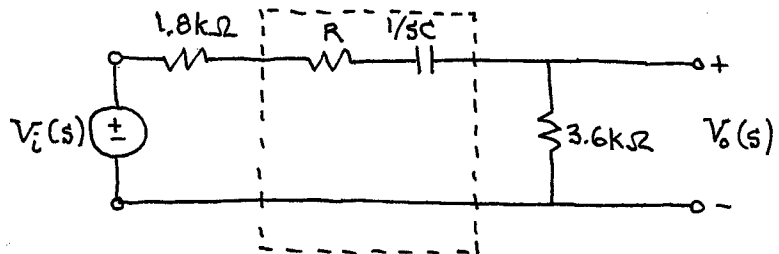II) Use an R and C in series with $1.8\text{ k}\Omega$.



For $\omega = 0$, the C acts like an open circuit. This gives $V_o(s=j0) = 0$ and $|H(s=j0)| = 0$.


For $\omega \rightarrow \infty$, the C acts like a wire and $|H(j\omega)| = \frac{3.6\text{ k}\Omega}{1.8\text{ k}\Omega + R + 3.6\text{ k}\Omega}$ must be $\frac{4}{9}$.

$$\text{or } |H(j\omega)| = \frac{4(0.9\text{ k}\Omega)}{9(0.9\text{ k}\Omega)} = \frac{3.6\text{ k}\Omega}{8.1\text{ k}\Omega}$$

Thus, $1.8\text{ k}\Omega + R + 3.6\text{ k}\Omega = 8.1\text{ k}\Omega$.

$$R = 2.7\text{ k}\Omega$$

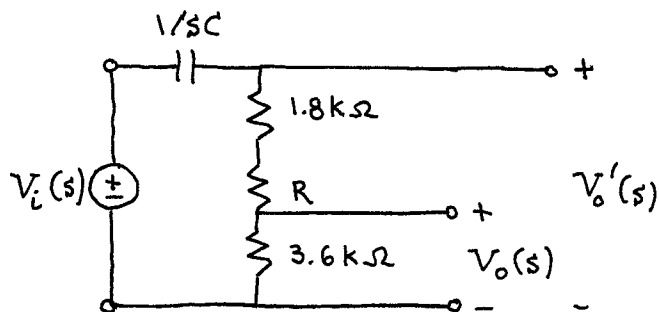To find ω_c , rearrange components to put R's together, (without changing $H(s)$).



In this configuration we have a standard RC filter multiplied by a voltage divider.

$$H(s) = \frac{3.6 \text{ k}\Omega}{3.6 \text{ k}\Omega + 1.8 \text{ k}\Omega + R} \cdot \frac{3.6 \text{ k}\Omega + 1.8 \text{ k}\Omega + R}{3.6 \text{ k}\Omega + 1.8 \text{ k}\Omega + R + \frac{1}{sC}}$$

$$= \frac{3.6 \text{ k}\Omega}{8.1 \text{ k}\Omega + \frac{1}{sC}} = \frac{sC \cdot 3.6 \text{ k}\Omega}{1 + sC \cdot 8.1 \text{ k}\Omega}$$

A better form of $H(s)$ for finding ω_c is $H(s) = \frac{4}{9} \cdot \frac{R'}{R' + \frac{1}{sC}}$ where $R' = 8.1 \text{ k}\Omega$.

$$\text{or } H(s) = \frac{4}{9} \cdot \frac{sR'C}{1 + sR'C}$$

$$\omega_c \text{ is where } |H(j\omega_c)| = \frac{1}{\sqrt{2}} \max_{\omega} |H(j\omega)|$$

$$\text{or } |H(j\omega_c)| = \frac{1}{\sqrt{2}} \cdot \frac{4}{9}$$

$$\text{or } \frac{|sR'C|}{|1 + sR'C|} = \frac{1}{\sqrt{2}}$$

$$\text{The sol'n is } s = j\omega_c = j \frac{1}{R'C}, \text{ as this}$$

$$\text{gives } |sR'C| = |j \frac{1}{R'C} R'C| = |j| = 1$$

$$\text{and } |1 + sR'C| = |1 + j \frac{1}{R'C} R'C| = |1 + j| = \sqrt{2}$$

$$\text{So } \omega_c = \frac{1}{R'C} \text{ and } C = \frac{1}{R'\omega_c} = \frac{1}{8.1 \text{ k}\Omega \cdot 400 \text{ kr/s}}$$

$$C = 309 \text{ pF}$$