ECE 2270 F 06



Im

1. a) Find 
$$\mathcal{L}\left\{\int_0^t e^{-6\tau} u(6\tau) d\tau\right\}$$
.

b) Find 
$$f(t)$$
 if  $F(s) = \frac{6s + 27}{s^2 + 4s + 29}$ 

c) Find 
$$\lim_{t \to \infty} f(t)$$
 if  $F(s) = \frac{3}{s[(s+4)^2 + 36]}$ 

d) Plot the poles and zeros of F(s) in the *s* plane.



2.



- a) Write the Laplace transform,  $V_{g1}(s)$ , of  $v_{g1}(t)$ .
- b) Draw the s-domain equivalent circuit, including sources  $V_{g1}(s)$  and  $V_{g2}(s)$ , components, initial conditions for L, and terminals for  $V_0(s)$ . Note that the 30 V source is on for all time.
- c) Write an expression for  $V_0(s)$ . You may write parallel impedances using the  $\parallel$  operator without having to simplify them.
- d) Apply the initial value theorem to find  $\lim_{t\to 0^+} v_o(t)$ .

3. Find the inverse Laplace transform for each of the following expressions:

$$i_{g}(t) = 3e^{-10t}\cos(3t) \text{ A}$$

**Note:** The initial voltage on the capacitor is  $v_{\rm C}(t = 0^-) = 3 {\rm V}$ .

- a) Write the Laplace transform  $I_g(s)$  of  $i_g(t)$ .
- b) Write the Laplace transform  $V_0(s)$  of  $v_0(t)$ . Be sure to include the effects of the initial voltage on the C.
- c) Write a numerical time-domain expression for  $v_0(t)$  where t > 0. Hint: plug in numbers and look for terms that cancel before computing partial fractions.