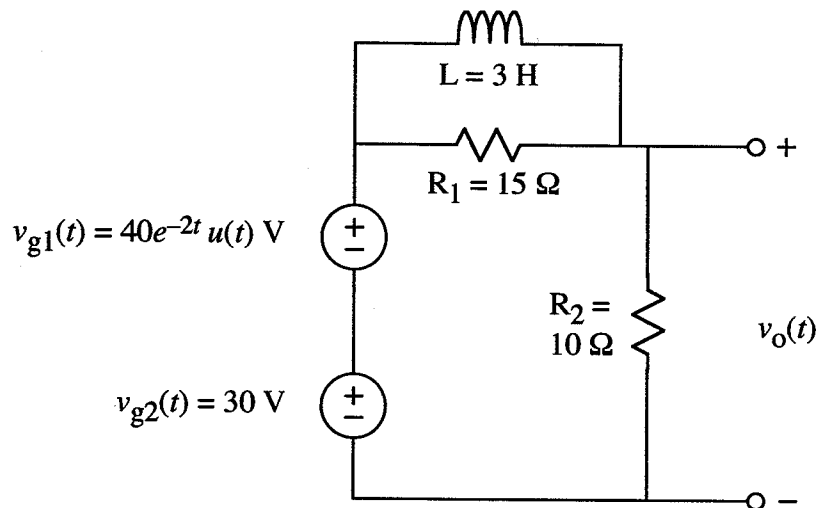


Ex:



- Write the Laplace transform, $V_{g1}(s)$, of $v_{g1}(t)$.
- Draw the s-domain equivalent circuit, including sources $V_{g1}(s)$ and $V_{g2}(s)$, components, initial conditions for L , and terminals for $V_o(s)$. Note that the 30 V source is on for all time.
- Write an expression for $V_o(s)$. You may write parallel impedances using the $\parallel$ operator without having to simplify them.
- Apply the initial value theorem to find $\lim_{t \rightarrow 0^+} v_o(t)$.


Sol'n: a) From a table of Laplace transforms we have

$$\mathcal{L}\{v_{g1}(t)\} = \mathcal{L}\{40e^{-2t}u(t)\text{V}\} = \frac{40 \text{ V}}{s+2}$$

Note: we append units of V to our answer, although our expression has units V·sec owing to integration over time when we take the Laplace transform. s has units of 1/sec and the 2 in the denominator has units of 1/sec in e^{-2t} . Thus, our answer should technically be $\frac{40 \text{ V}}{s+2/\text{sec}}$.

- b) We first find the initial conditions for the L. At $t=0^-$, the L acts like a wire, and only the v_{g2} source has a nonzero value.

$t=0^-$ circuit model:

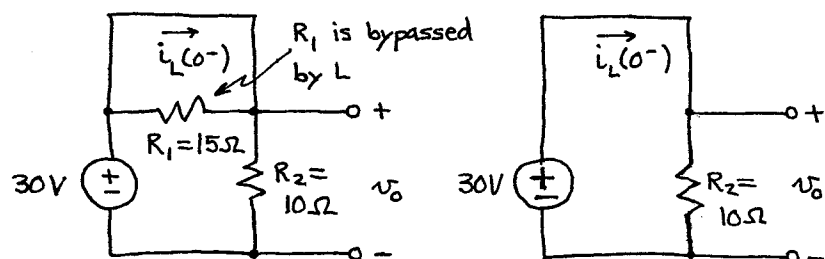


Our circuit simplifies

$$i_L(0^-) = \frac{30V}{R_2} = \frac{30V}{10\Omega}$$

$$i_L(0^-) = 3A$$

Although we may model the initial conditions on L as a series voltage source or a parallel current source, a parallel current source is convenient owing to the R in parallel with L.

$$i_L(0^-)/s = 3/s \text{ A}$$

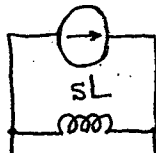


From part (a) we have $\mathcal{L}\{v_{g1}(t)\} = \frac{40V}{s+2}$.

For $v_{g2}(t)$, we have $\mathcal{L}\{v_{g2}(t)\} = \mathcal{L}\{30V\}$.


We treat 30V as $30V u(t)$. Thus, $\mathcal{L}\{v_{g2}(t)\} = \frac{30V}{s}$.

s-domain model:

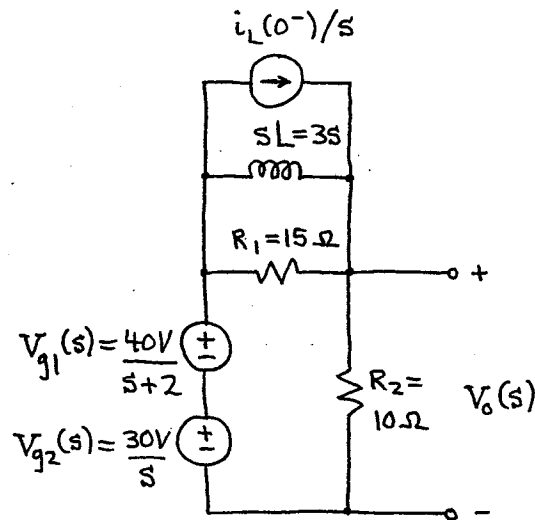


c) We may use superposition to find $V_o(s)$.
We have two circuits:

circuit I:

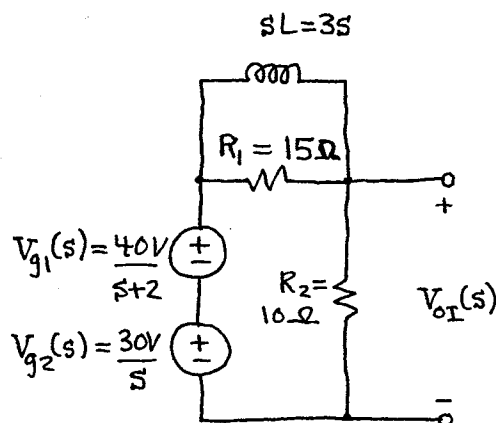

circuit I is V-divider

circuit II:

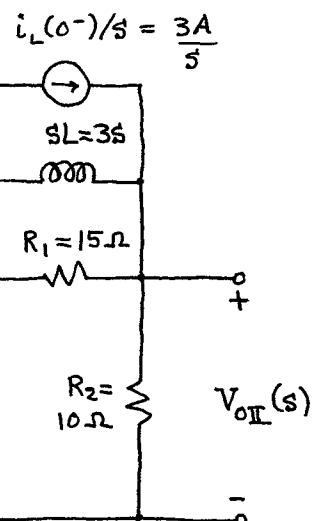

circuit II is solved by Ohm's law

We write down $V_{oI}(s)$ and $V_{oII}(s)$ by inspection:

$$V_{oI}(s) = \left(\frac{40V}{s+2} + \frac{30V}{s} \right) \frac{R_2}{R_2 + R_1 \parallel sL}$$

$$V_{oII}(s) = \frac{i_L(0^-)}{s} \cdot R_2 \parallel R_1 \parallel sL$$

$$V_o(s) = V_{oI}(s) + V_{oII}(s) \quad (\text{we sum the } V's)$$

$$\text{or } V_o(s) = \left(\frac{40V}{s+2} + \frac{30V}{s} \right) \frac{R_2}{R_2 + R_1 \parallel sL} + \frac{i_L(0^-)}{s} R_2 \parallel R_1 \parallel sL$$

We may simplify the expression to a ratio of polynomials. We begin by finding an expression for $R \parallel sL$.

$$\text{We write } R \parallel sL \text{ as } sLR \cdot \frac{1}{sL} \parallel \frac{1}{R} = \frac{sLR}{sL + R} = \frac{sR}{s + R/L}$$

$$\text{Note: we are using the identity } \frac{1}{a} \parallel \frac{1}{b} = \frac{1}{a+b}.$$

$$\text{Thus, } R_2 \parallel R_1 \parallel sL = \frac{sL \cdot R_1 \parallel R_2}{sL + R_1 \parallel R_2} \quad \text{where } R_1 \parallel R_2 = 10\Omega \parallel 15\Omega$$

$$= 5\Omega \cdot 2 \parallel 3$$

$$= \frac{5 \cdot 6\Omega}{5} = 6\Omega$$

$$= \frac{s R_1 \parallel R_2}{s + \frac{R_1 \parallel R_2}{L}}$$

$$= \frac{s \cdot 6\Omega}{s + \frac{6\Omega}{3H}}$$

$$R_2 \parallel R_1 \parallel sL = \frac{s \cdot 6\Omega}{s+2}$$

Now we substitute $R_1 \parallel sL = \frac{sR_1}{s + R_1/L}$ in the 1st term.

$$\frac{R_2}{R_2 + R_1 \parallel sL} = \frac{R_2}{R_2 + \frac{sR_1}{s + R_1/L}} = \frac{R_2(s + R_1/L)}{R_2(s + R_1/L) + sR_1}$$

$$= \frac{R_2}{R_1 + R_2} \frac{s + R_1/L}{s + \frac{R_1 \parallel R_2}{L}}$$

$$= \frac{10 \Omega}{10 + 15 \Omega} \frac{s + 15 \Omega / 3 \text{ H}}{s + 6 \Omega / 3 \text{ H}}$$

$$\frac{R_2}{R_2 + R_1 \parallel sL} = \frac{2}{5} \frac{s+5}{s+2}$$

Plugging in values, we find $V_o(s)$:

$$V_o(s) = \left(\frac{40 \text{ V}}{s+2} + \frac{30 \text{ V}}{s} \right) \frac{2}{5} \frac{s+5}{s+2} + \frac{3 \text{ A} \cdot 6 \Omega \cdot s}{s(s+2)}$$

$$V_o(s) = \frac{[40Vs + 30(s+2)](2/5)(s+5) + 18Vs(s+2)}{s(s+2)^2}$$

$$= \frac{28s^2 + 84s + 120 + 18s^2 + 36s}{s(s+2)^2} \text{ V}$$

$$V_o(s) = \frac{46s^2 + 120s + 120}{s(s+2)^2} \text{ V}$$

d) By the initial value theorem $\lim_{t \rightarrow 0^+} v_o(t) = \lim_{s \rightarrow \infty} sV_o(s)$.

We only use the highest power of s in the numerator and denominator as these dominate as $s \rightarrow \infty$.

$$\lim_{t \rightarrow 0^+} v_o(t) = \lim_{s \rightarrow \infty} s \cdot \frac{46 s^2}{s \cdot s^2} V = 46 V$$

Note: We may also apply the initial value theorem to the unsimplified $V_o(s)$.

We observe that $\lim_{s \rightarrow \infty} R \parallel sL = R \parallel \infty = R$.

$$\lim_{s \rightarrow \infty} sV_o(s) = \lim_{s \rightarrow \infty} s \left(\frac{40V}{s+2} + \frac{30V}{s} \right) \frac{R_2}{R_1+R_2} + \frac{s i_L(0^-) R_2 \parallel R_1}{s}$$

↑
ignore 2 since $2 \ll s \rightarrow \infty$

$$= 70V \cdot \frac{R_2}{R_1+R_2} + i_L(0^-) R_2 \parallel R_1$$

$$= 70V \cdot \frac{10\Omega}{10+15\Omega} + 3A \cdot 6\Omega$$

$$= 28V + 18V$$

$$\lim_{t \rightarrow 0^+} v_o(t) = 46V \quad \checkmark$$