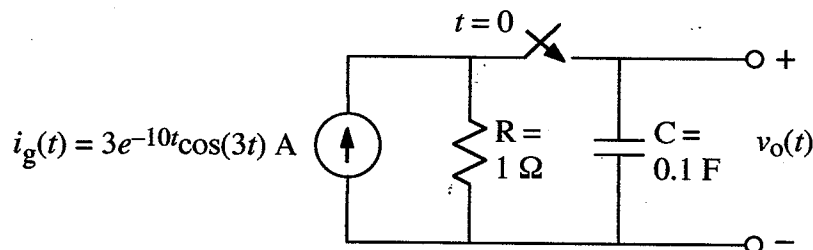


EX:




Note: The initial voltage on the capacitor is $v_C(t=0^-) = 3$ V measured with + on top.

- Write the Laplace transform $I_g(s)$ of $i_g(t)$.
- Write the Laplace transform $V_o(s)$ of $v_o(t)$. Be sure to include the effects of the initial voltage on the C.
- Write a numerical time-domain expression for $v_o(t)$ where $t > 0$. Hint: plug in numbers and look for terms that cancel before computing partial fractions.

Sol'n: a) From a table of Laplace transforms:

$$\mathcal{L}\{i_g(t)\} = \mathcal{L}\{3e^{-10t} \cos(3t) A\} = \frac{3(s+10)}{(s+10)^2 + 3^2} A$$

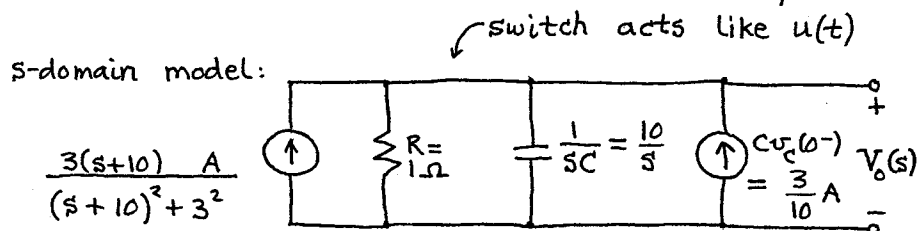- It is convenient to use a parallel current source for initial conditions on the Capacitor.



The output voltage is the total current times the total parallel resistance.

$$V_o(s) = \left(\frac{3(s+10) A}{(s+10)^2 + 3^2} + \frac{3}{10} A \right) R \parallel \frac{1}{sC}$$

Simplifying further, we have

$$R \parallel \frac{1}{sC} = R \cdot \left(\frac{1}{1} \parallel \frac{1}{sRC} \right) = \frac{R}{1 + sRC} = \frac{1 \Omega}{1 + \frac{s}{10}} = \frac{10 \Omega}{s+10}$$

$$\therefore V_o(s) = \left(\frac{3(s+10) A}{(s+10)^2 + 3^2} + \frac{3}{10} A \right) \frac{10 \Omega}{s+10}$$

$$= \frac{30V}{(s+10)^2 + 3^2} + \frac{3V}{s+10}$$

$$V_o(s) = \frac{10V \cdot 3}{(s+10)^2 + 3^2} + 3V \cdot \frac{1}{s+10}$$

c) The above form for $V_o(s)$ is

$$V_o(s) = \frac{10V\omega}{(s+a)^2 + \omega^2} + 3V \cdot \frac{1}{s+a} \quad \text{where } a=10 \quad \omega=3$$

Using a table, we inverse transform $V_o(s)$ by inspection:

$$v_o(t) = [10V e^{-10t} \sin(3t) + 3V e^{-10t}] u(t)$$