

Ex:



Note:  $\omega = 10$  r/s.

Do the following for the impedance to the right of the a, b terminals:

- a) Calculate complex power S = P + jQ.
- b) Calculate average (or DC) power.
- c) Calculate maximum instantaneous power.
- d) Sketch the power waveform, p(t).
- SOL'N: a) We first create an s-domain model. We have the following impedance values:

$$\frac{1}{j\omega C_1} = \frac{1}{j10r/s \cdot 200\mu F} = -j500 \ \Omega \qquad \frac{1}{j\omega C_2} = \frac{1}{j10r/s \cdot 5mF} = -j20 \ \Omega$$
$$j\omega L = j10r/s \cdot 3H = j30 \ \Omega$$

Our s-domain model:



STATISTICS STUDENT'S OR t-DISTRIBUTION Derivation (cont.)

Now we calculate the impedance to the right of **a**, **b**.

$$z = -j500 \parallel (80 + -j20 \parallel j30) \Omega$$

or

$$z = 10 \cdot (-j50 \parallel (8 + -j2 \parallel j3)) \Omega$$

or

 $z = 10 \cdot (-j50 \parallel (8 + \frac{6}{j})) \Omega$ 

or

$$z = 10 \cdot (-j50 \parallel (8 - j6)) \Omega$$

or

$$z = 20 \cdot (-j25 \parallel (4 - j3)) \Omega$$

or

 $z = 20 \cdot \left( 25 \cdot \frac{-3 - j4}{4 - j28} \right) \Omega$ 

or

$$z = 5 \cdot \left(25 \cdot \frac{-3 - j4}{1 - j7} \cdot \frac{1 + j7}{1 + j7}\right) \Omega$$

or

$$z = 5 \cdot \left(25 \cdot \frac{25 - j25}{50}\right) \Omega$$

or

$$z = \frac{125 - j125}{2} \ \Omega$$

One formula for complex power involves only current and impedance:

$$S = \frac{1}{2}\boldsymbol{V}\boldsymbol{I}^* = \frac{1}{2}\boldsymbol{I}\boldsymbol{z}\cdot\boldsymbol{I}^* = \frac{1}{2}|\boldsymbol{I}|^2\boldsymbol{z}$$

Using values from the problem, we find the numerical value of *S*:

$$S = \frac{1}{2}4^2 \frac{125 - j125}{2} \text{ VA} = 500 - j500 \text{ VA}$$

b) The average DC power is equal to the real part of S = P + jQ, which is P:

P = 500 W

- **NOTE:** The value of *P* is, by coincidence, both the average power and the magnitude of the cosine portion of the AC part of the power waveform.
- **NOTE:** The units we use when writing P are Watts. The units we use when writing S are VA. This equals Watts, but we write it in this alternate way so we can distinguish which quantity we are talking about when we see only a numerical value.
- c) The power waveform is equal to a DC value of P plus a sinusoid whose phasor is S. It follows that the peak instantaneous value of power,  $p_{max}(t)$ , is equal to P plus the magnitude of S:

$$p_{\max}(t) = P + |S| = P + \sqrt{P^2 + Q^2} = 500 + \sqrt{500^2 + 500^2} W$$

or

 $p_{\max}(t) = 500 + 500\sqrt{2} \text{ W}$ 

d) From the description in (c), we have the AC signal represented by *S* riding on top of the DC signal of height *P*. The AC signal is best represented in polar form when making a sketch:

$$\mathcal{L}^{-1}\{S = 500 - j500 \text{ VA}\} = \mathcal{L}^{-1}\{S = 500\sqrt{2}\mathcal{L} - 45^{\circ} \text{ VA}\}\$$
  
= 500\sqrt{2}\cos(2\cdot 10t - 45^{\circ}) W

Adding the AC waveform to the DC offset, we have the following waveform for p(t).

$$p(t) = 500 + 500\sqrt{2}\cos(20t - 45^\circ)$$
 W

**NOTE:** The AC part of the power has frequency  $2\omega$ . This arises from the trigonometric identity for the product of cosines.

STATISTICS STUDENT'S OR t-DISTRIBUTION Derivation (cont.)

For  $2\omega = 20$ , we have the following period:

$$T = \frac{1}{f} = \frac{2\pi}{2\omega} = \frac{2\pi}{20 \text{ r/s}} \approx 0.314 \text{ s} = 314 \text{ ms}$$

