

Ex:



- a) Calculate  $\mathbf{I}_{rms}$ . Note:  $\omega = 5 \text{ kr/s}$ .
- b) Calculate the complex power, S, for the components inside the box.
- SOL'N: a) We first create an *s*-domain model. We have the following impedance values:

$$\frac{1}{j\omega C} = \frac{1}{j5 \text{ k r/s} \cdot 2 \ \mu\text{F}} = -j100 \ \Omega$$
$$j\omega L = j5 \text{ k r/s} \cdot 20 \ \text{mH} = j100 \ \Omega$$

Our *s*-domain model, with the rms value of the voltage source:



We use Ohm's law to calculate  $I_{rms}$ :

$$\mathbf{I}_{\rm rms} = \frac{\mathbf{V}_{\rm rms}}{z_{\rm tot}} = \frac{5/\sqrt{2} \,\, \mathrm{V}_{\rm rms}}{-j100 + 700 \,\, \text{II} \,\, j100 \,\, \Omega} = \frac{5/\sqrt{2} \,\, \mathrm{V}_{\rm rms}}{100 \left(-j + \frac{j7}{7+j}\right) \Omega}$$

STATISTICS STUDENT'S OR t-DISTRIBUTION Derivation (cont.)

or

$$\mathbf{I}_{\rm rms} = \frac{5/\sqrt{2} \, V_{\rm rms}}{100 \left(-j\frac{7+j}{7+j} + \frac{j7}{7+j}\right) \Omega} = \frac{5/\sqrt{2}}{100\frac{1}{7+j}} \, A_{\rm rms}$$

or

$$\mathbf{I}_{\text{rms}} = \frac{50}{\sqrt{2}}(7+j) \text{ mA}_{\text{rms}} = \frac{50}{\sqrt{2}}\sqrt{50}\angle \tan^{-1}\left(\frac{1}{7}\right) \text{ mA}_{\text{rms}}$$

or

$$\mathbf{I}_{\text{rms}} = 50\sqrt{25}\angle 8.13^{\circ} \text{ mA}_{\text{rms}}$$

b) We use the rms formulas for *S*:

$$S = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = \mathbf{I}_{\text{rms}} z \mathbf{I}_{\text{rms}}^* = |\mathbf{I}_{\text{rms}}|^2 z$$

Using numerical values, we have the following:

$$S = (50\sqrt{25} \text{ m})^2 \cdot 100 \cdot 7 \parallel j = \frac{25}{20^2} \cdot 100 \cdot \frac{j7}{7+j} \text{ VA}$$

or

$$S = \frac{25}{4} \cdot \frac{j7}{7+j} \cdot \frac{7-j}{7-j} = \frac{25}{4} \cdot \frac{7(1+j7)}{50} = \frac{7(1+j7)}{8} \text{ VA}$$

In polar form, we have the following:

$$S = \frac{7\sqrt{50}}{8} \tan^{-1} \left(\frac{7}{1}\right) = \frac{7\sqrt{50}}{8} \angle 81.7^{\circ} \text{ VA}$$

**NOTE:** Since S is a power quantity, there is no factor of  $\sqrt{2}$  for rms after we have calculated S. A factor of 1/2 has, however, been embedded in the final answer via the product of rms quantities.