
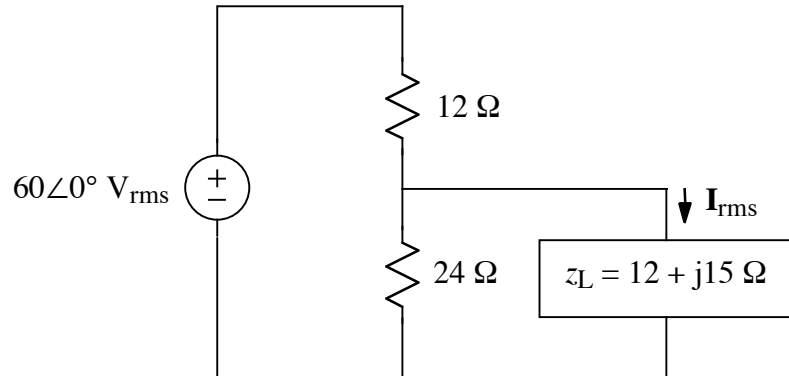


1.

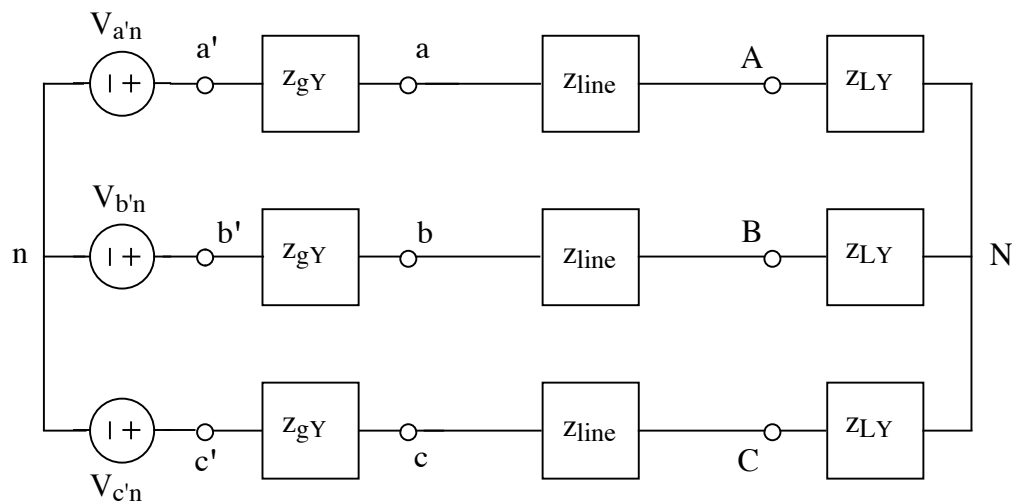

- Calculate the value of rms current, I_{rms} , flowing through z_L .
- Calculate the complex power, S , for z_L . Include appropriate units.


2.




$$\begin{aligned} V_{a'n} &= 82\angle 0^\circ \text{ V} & z_{gY} &= 0.1 \Omega \\ V_{b'n} &= 82\angle 120^\circ \text{ V} & z_{\text{line}} &= 39 + j5 \Omega \\ V_{c'n} &= 82\angle -120^\circ \text{ V} & z_{LY} &= 0.9 + j4 \Omega \end{aligned}$$

- Draw a single-phase equivalent circuit.
- Calculate V_{AB} .

3.

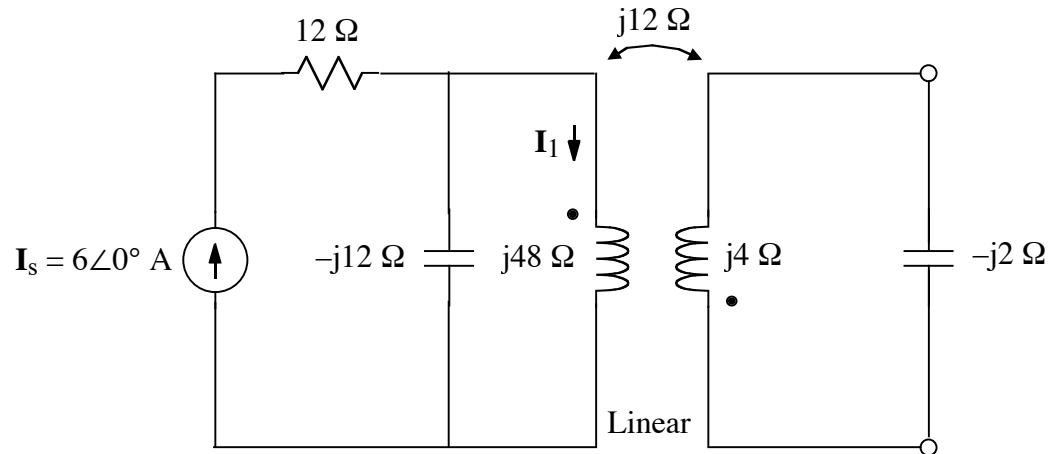

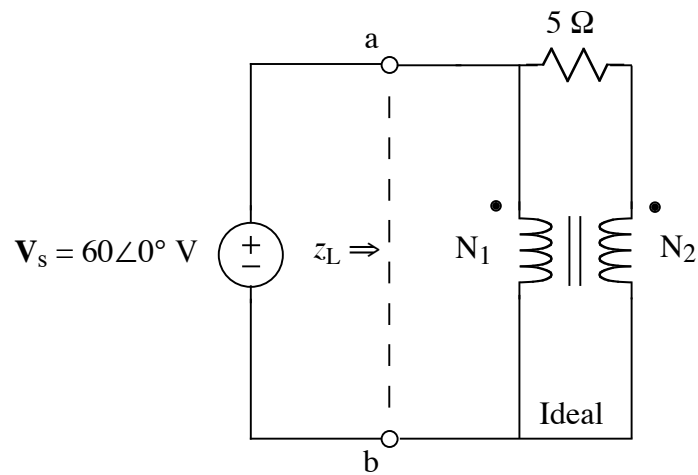- a) Calculate the numerical value of phasor current $\mathbf{I}_1$.



- b) Given $N_1/N_2 = 9$, calculate the impedance, z_L , seen by the voltage source in the above transformer circuit.